

CDA 4253 FPGA System Design

Optimization Techniques

Hao Zheng
Comp S ci & Eng
Univ of South Florida

Extracted from
Advanced FPGA Design
by Steve Kilts

Optimization for Performance

Performance Definitions

- **Throughput:** the number of inputs processed per unit time.
- **Latency:** the amount of time for an input to be processed.
- Maximizing throughput and minimizing latency in conflict.
- Both require timing optimization:
 - Reduce delay of the *critical path*.

Achieving High Throughput: Pipelining

- Divide data processing into stages
- Process different data inputs in different stages simultaneously.

```
xpower = 1;  
for (i = 0; i < 3; i++)  
    xpower = x * xpower;
```

Throughput: 1 data / 3 cycles = 0.33 data / cycle .

Latency: 3 cycles.

Critical path delay: 1 multiplier delay

```
-- Non-pipelined version  
process (clk) begin  
    if rising_edge(clk) then  
        if start='1' then  
            cnt <= 3;  
        end if;  
        if cnt > 0 then  
            cnt <= cnt - 1;  
            xpower <= xpower * x;  
        elsif cnt = 0 then  
            done <= '1';  
        end if;  
    end process;
```

Achieving High Throughput: Pipelining

```
xpower = 1;  
for (i = 0; i < 3; i++)  
    xpower = x * xpower;
```

Throughput: 1 data / cycle


Latency: 3 cycles + register delays.

Critical path delay: 1 multiplier delay


```
-- Pipelined version  
process (clk, rst) begin  
    if rising_edge(clk) then  
        if start='1' then -- stage 1  
            x1 <= x;  
            xpower1 <= x;  
            done1 <= start;  
        end if;  
        -- stage 2  
        x2 <= x1;  
        xpower2 <= xpower1 * x1;  
        done2 <= done1;  
        -- stage 3  
        xpower <= xpower2 * x2;  
        done <= done2;  
    end if;  
end process;
```

Comparison

Iterative implementation

 


Pipelined implementation

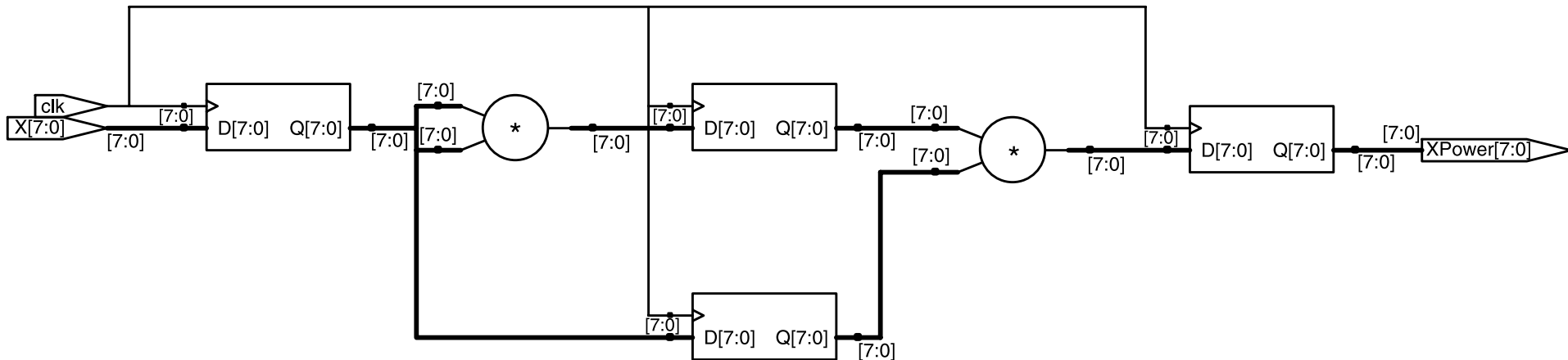


Achieving High Throughput: Pipelining

- Loop unrolling

 


Achieving High Throughput: Pipelining

- Loop unrolling

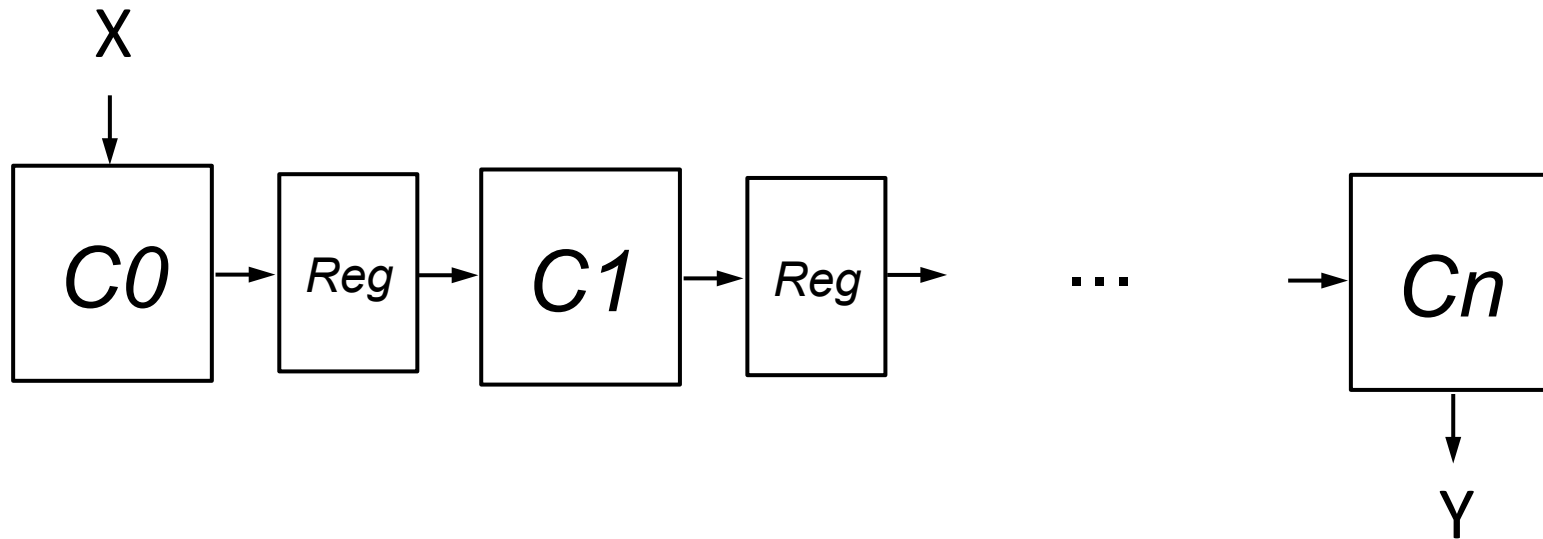


Achieving High Throughput: Pipelining

 - Divide data processing into stages
- Process different data inputs in different stages simultaneously.



Achieving High Throughput: Pipelining

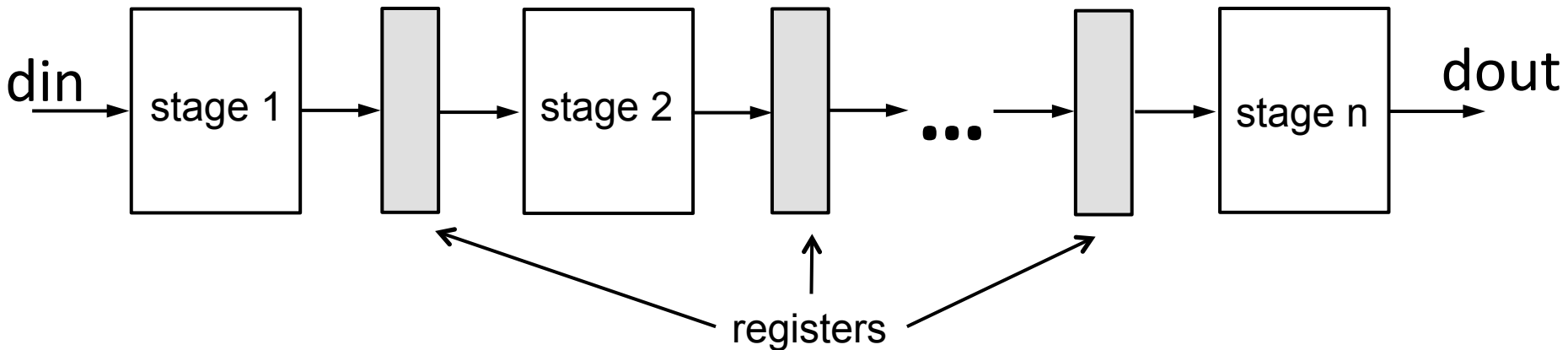
- Divide data processing into stages
- Process different data inputs in different stages simultaneously.



Penalty: increase in area as logic needs to be duplicated for different stages


Reducing Latency

 - Closely related to reducing critical path delay.
- Reducing pipeline registers reduces latency.




Reducing Latency

 - Closely related to reducing critical path delay.
- Reducing pipeline registers reduces latency.



Timing Optimization

 - Maximal clock frequency determined by the longest path delay in any combinational logic blocks.
- Pipelining is one approach.



Timing Optimization: Spatial Computing

- Extract independent operations
- Execute independent operations in parallel.

$$X = A + B + C + D$$

```
process (clk, rst) begin  
  if rising_edge(clk) then  
    X1 := A + B;  
    X2 := X1 + C;  
    X  <= X2 + D;  
  end if;  
end process;
```

Critical path delay: 3 adders

```
process (clk, rst) begin  
  if rising_edge(clk) then  
    X1 := A + B;  
    X2 := C + D;  
    X  <= X1 + X2;  
  end if;  
end process;
```


Critical path delay: 2 adders

Timing Optimization: Avoid Unwanted Priority

```
process (clk, rst) begin
    if rising_edge(clk) then
        if      c[0]='1' then r[0] <= din;
        elsif  c[1]='1' then r[1] <= din;
        elsif  c[2]='1' then r[2] <= din;
        elsif  c[3]='1' then r[3] <= din;
        end if;
    end if;
end process;
```

Critical path delay: 3-input AND gate + 4x1 MUX.

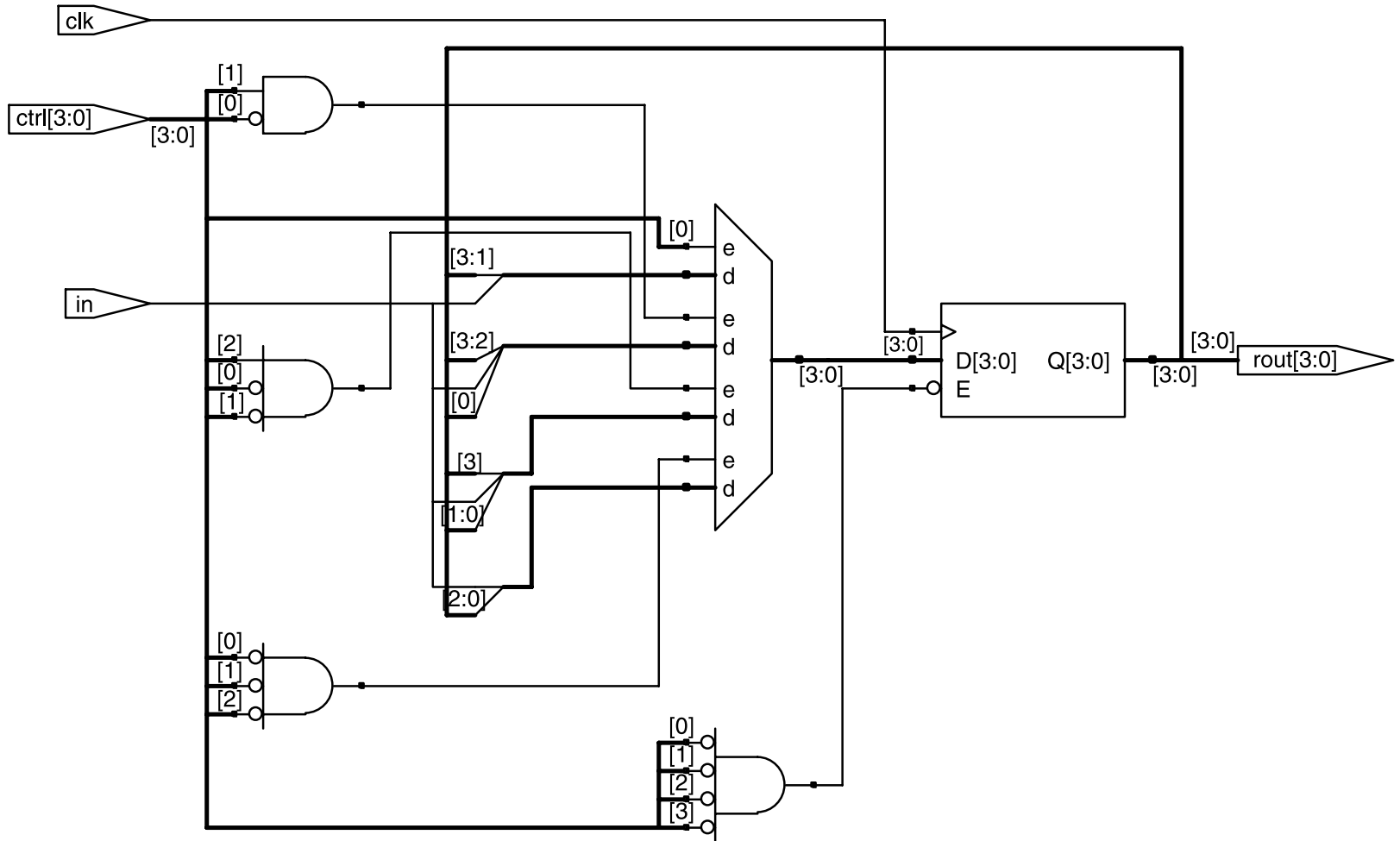Timing Optimization: Avoid Unwanted Priority




Critical path delay: 3-input AND gate + 4x1 MUX.

Timing Optimization: Avoid Unwanted Priority

```
process (clk, rst) begin
    if rising_edge(clk) then
        if c[0]='1' then r[0] <= din; end if;
        if c[1]='1' then r[1] <= din; end if;
        if c[2]='1' then r[2] <= din; end if;
        if c[3]='1' then r[3] <= din; end if;
    end if;
end process;
```

Critical path delay: 2x1 MUX



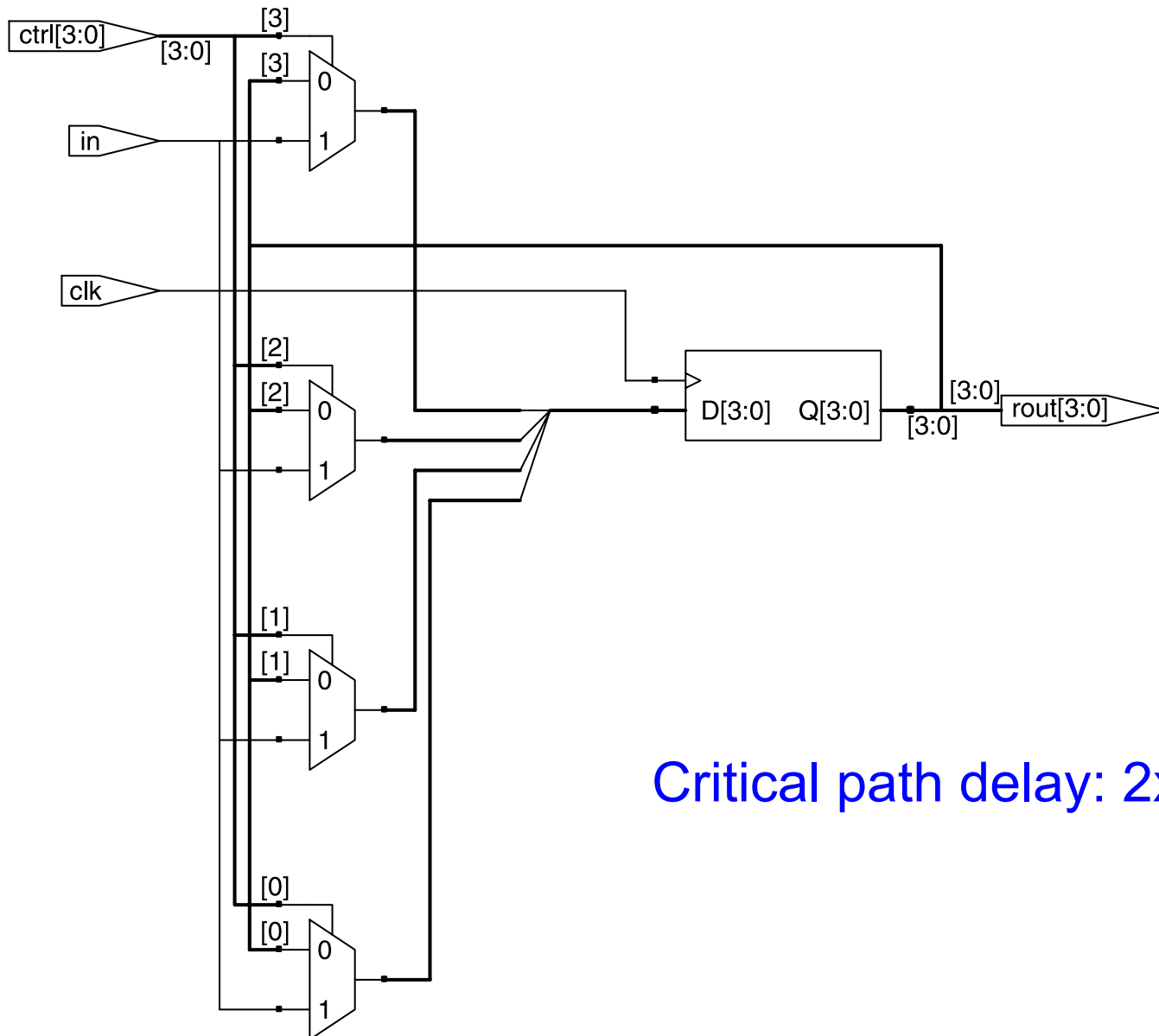
Timing Optimization: Avoid Unwanted Priority



Critical path delay: 2x1 MUX

Timing Optimization: Register Balancing

   - **Maximal** clock frequency determined by the **longest** path delay in any combinational logic blocks.




Timing Optimization: Register Balancing

```
process (clk, rst) begin
  if rising_edge(clk) then
    rA <= A;
    rB <= B;
    rC <= C;
    sum <= rA + rB + rC;
  end if;
end process;
```

```
process (clk, rst) begin
  if rising_edge(clk) then
    sumAB <= A + B;
    rC <= C;
    sum <= sumAB + rC;
  end if;
end process;
```


Timing Optimization: Register Balancing
 
```
process (clk, rst) begin
  if rising_edge(clk) then
    rA <= A;
    rB <= B;
    rC <= C;
    sum <= rA + rB + rC;
  end if;
end process;
```



Timing Optimization: Register Balancing


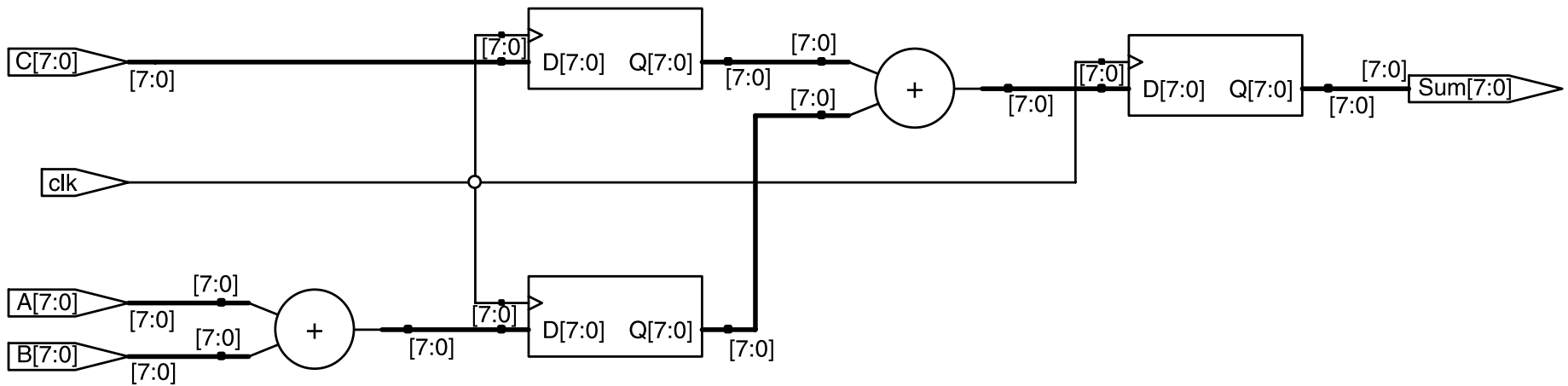
```
process (clk, rst) begin
  if rising_edge(clk) then
    sumAB <= A + B;
    rC <= C;
    sum <= sumAB + rC;
  end if;
end process;
```



Optimization for Area

Area Optimization: Resource Sharing

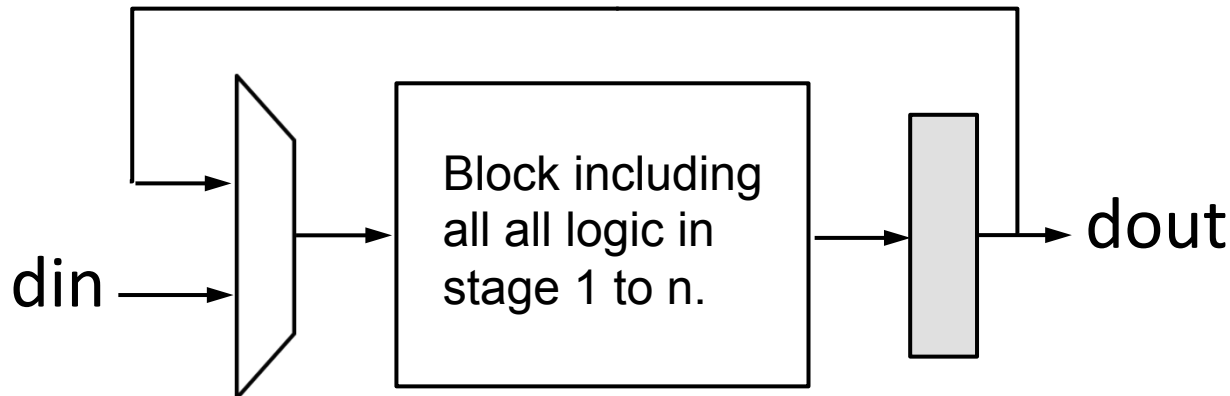 
- Rolling up pipeline: share common resources at different time – a form of **temporal** computing



Area Optimization: Resource Sharing

- Use registers to hold inputs
- Develop FSM to select which inputs to process in each cycle.



$$X = A + B + C + D$$

 

Area Optimization: Resource Sharing

- Use registers to hold inputs
- Develop FSM to select which inputs to process in each cycle.


$$X = A + B + C + D$$

  

A, B, C, D need to hold steady until X is processed


Area Optimization: Resource Sharing

Merge duplicate
components
together

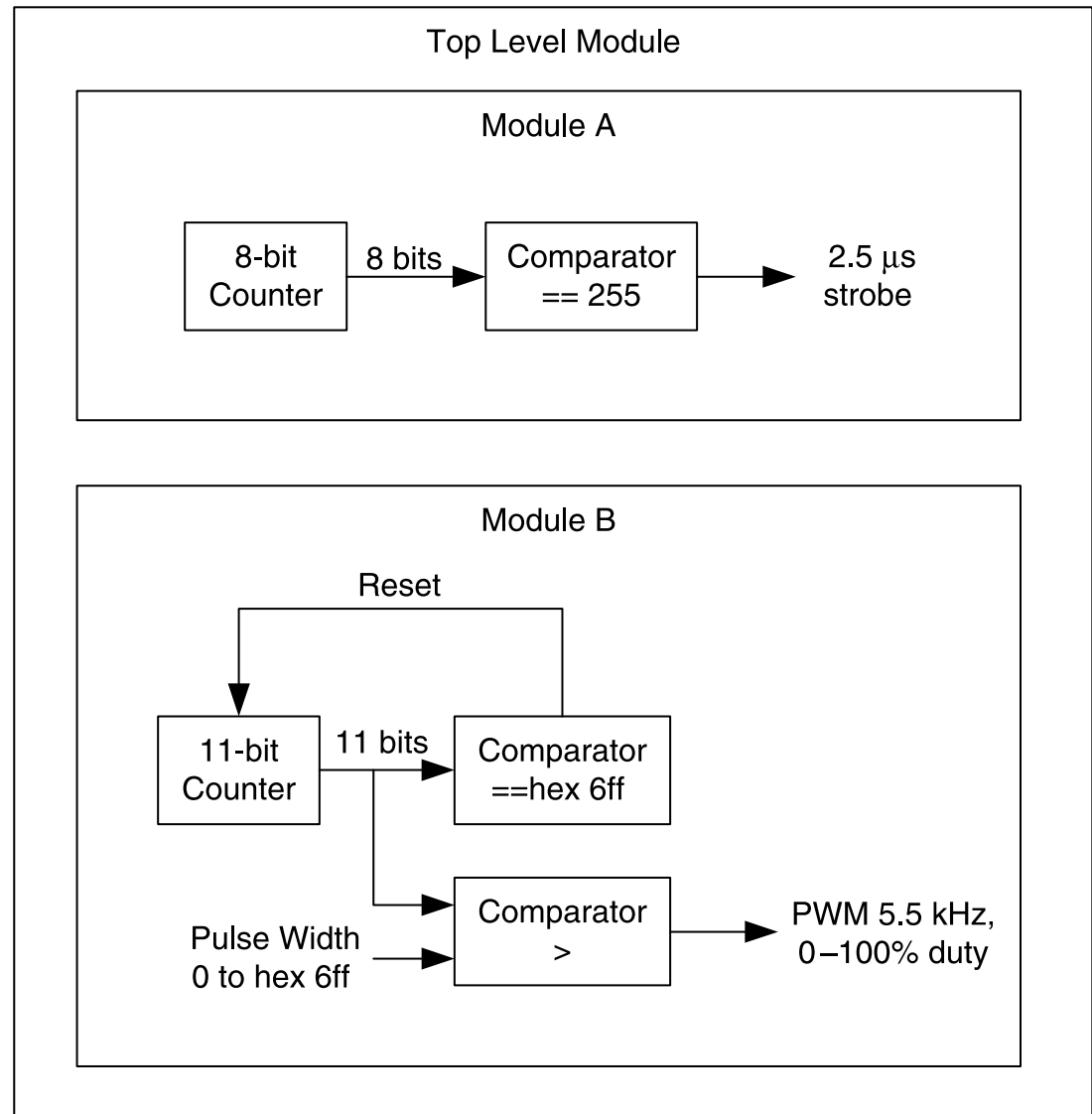

Area Optimization: Resource Sharing

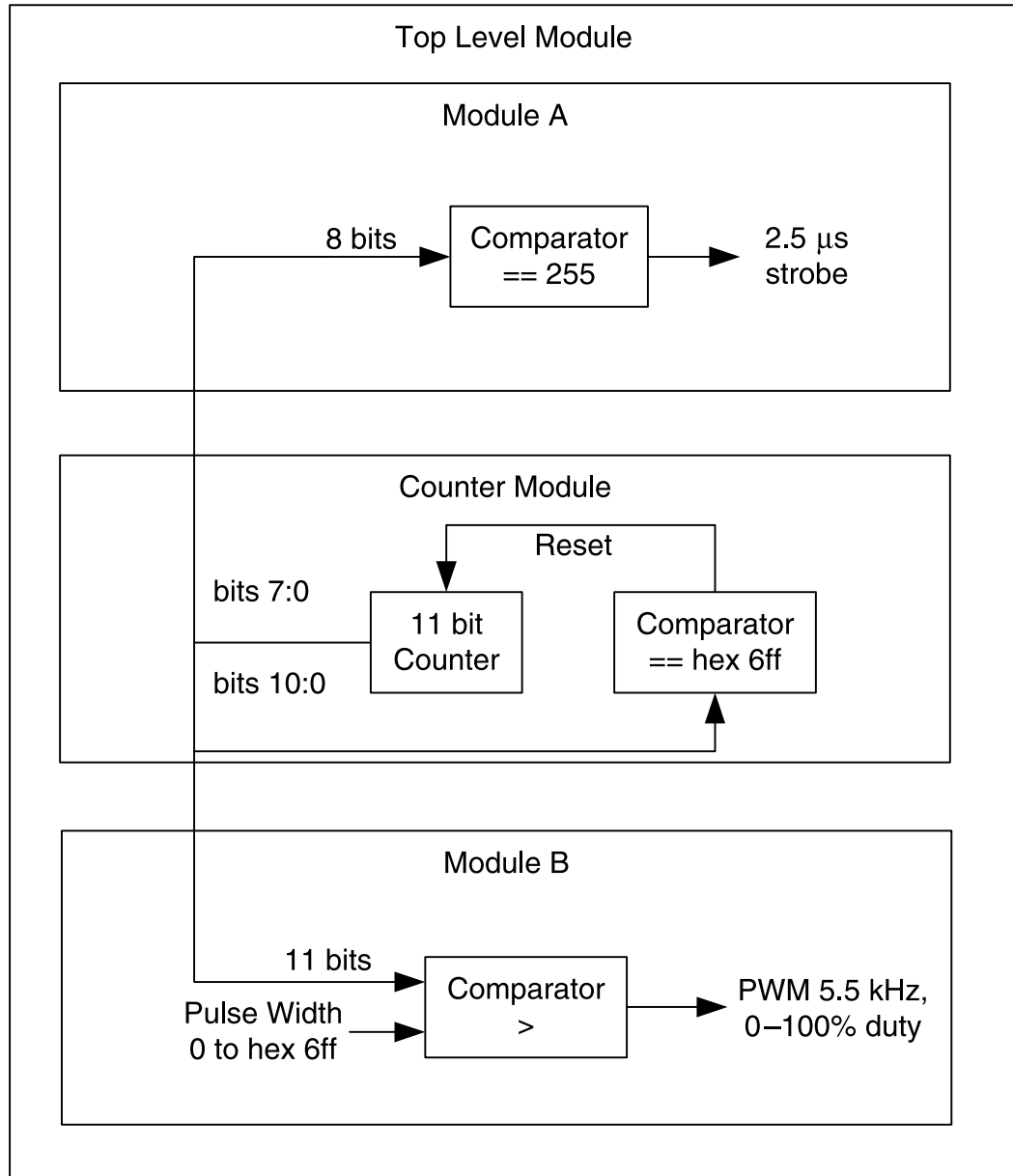Merge duplicate components together – reduces a 8-bit counter



Impact of Reset on Area (Xilinx Specific)

Do not set or reset Registers asynchronously.


- Control set remapping becomes impossible.
- Sequential functionality in device resources such as block RAM components and DSP blocks can be set or reset synchronously only.
- You will be unable to leverage device resources resources, or they will be configured sub-optimally.
- Use synchronous initialization instead.

Do not describe Flip-Flops with both a set and a reset.


- No Flip-Flop primitives feature both a set and a reset, whether synchronous or asynchronous.
- If not rejected by the software, Flip-Flop primitives featuring both a set and a reset may adversely affect area and performance.

Reset or No Reset?
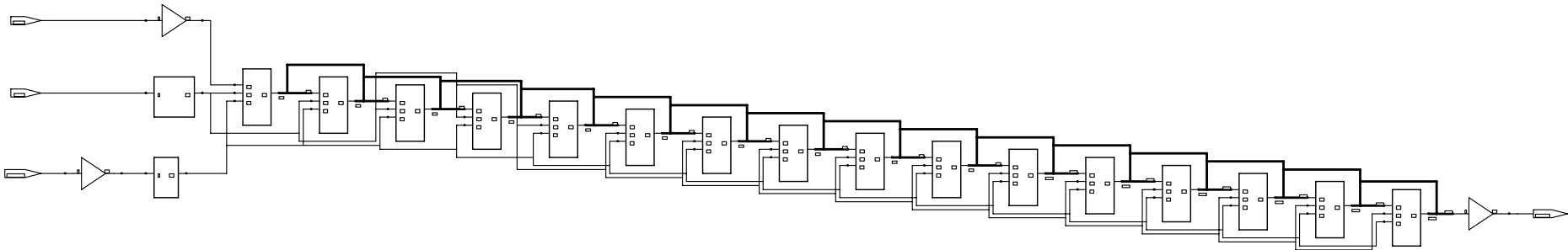
```
process (clk) begin
  if rising_edge(clk) then
    if rst = '0' then
      sr <= (others <= '0');
    else
      sr <= din & sr(14 downto 0);
    end if;
  end if;
end process;
```



Reset or No Reset?

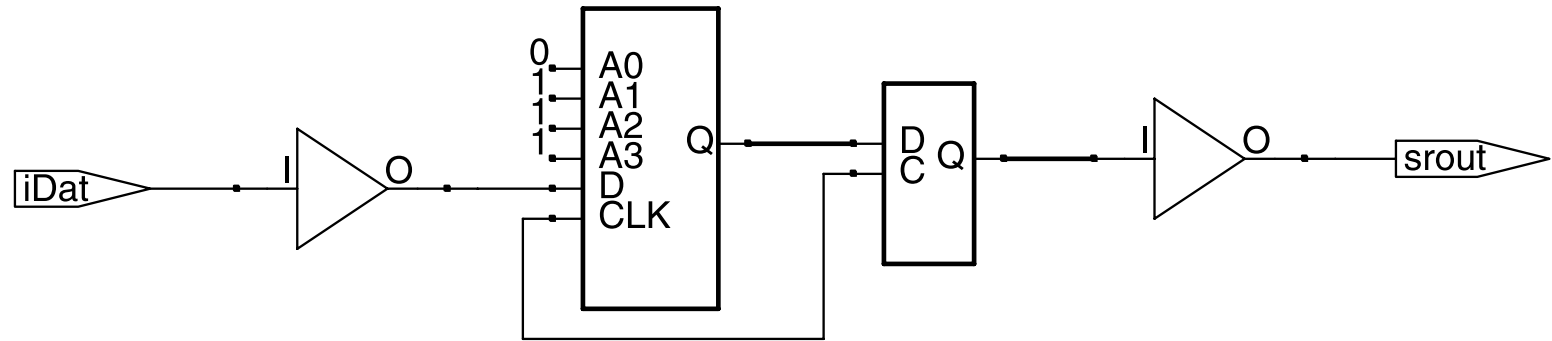

```
process (clk) begin
  if rising_edge(clk) then
    sr <= din & sr(14 downto 0);
  end if;
end process;
```


Reset or No Reset?

Table 2.1 Resource Utilization for Shift Register Implementations

Implementation	Slices slice	Flip-flops
Resets defined	9	16
No resets defined	1	1

Resetting Block RAM

- Block RAM only supports synchronous reset.
- Suppose that Mem is 256x16b RAM.
- Implementations of Mem with synchronous and asynchronous reset on Xilinx Virtex-4.

Implementation	Slices slice	Flip-flops	4 Input LUTs	BRAMs
Asynchronous reset	3415	4112	2388	0
Synchronous reset	0	0	0	1

VHDL model should match features offered by FPGA building blocks in order for those devices instantiated in the implementation.

Utilizing Set/Reset FF Pins

 


Figure 2.11 Simple synchronous logic with OR gate.

 


Figure 2.12 OR gate implemented with set pin.

 


Figure 2.13 Simple synchronous logic with AND gate.

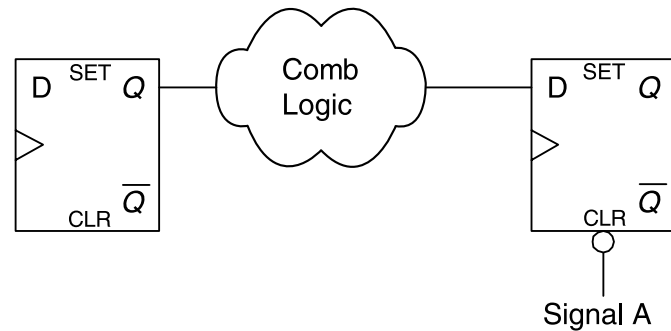


Figure 2.14 AND gate implemented with CLR pin.

Utilizing Set/Reset FF Pins – Example

```
process (clk, reset)
begin
  if reset='0' then
    oDat <= '0';
  else
    oDat <= iDat1 | iDat2;
  end if;
end process;
```

 


Figure 2.15 Simple asynchronous reset.

Utilizing Set/Reset FF Pins – Example

```
process (clk, reset)
begin
  oDat <= iDat1 | iDat2;
end process;
```

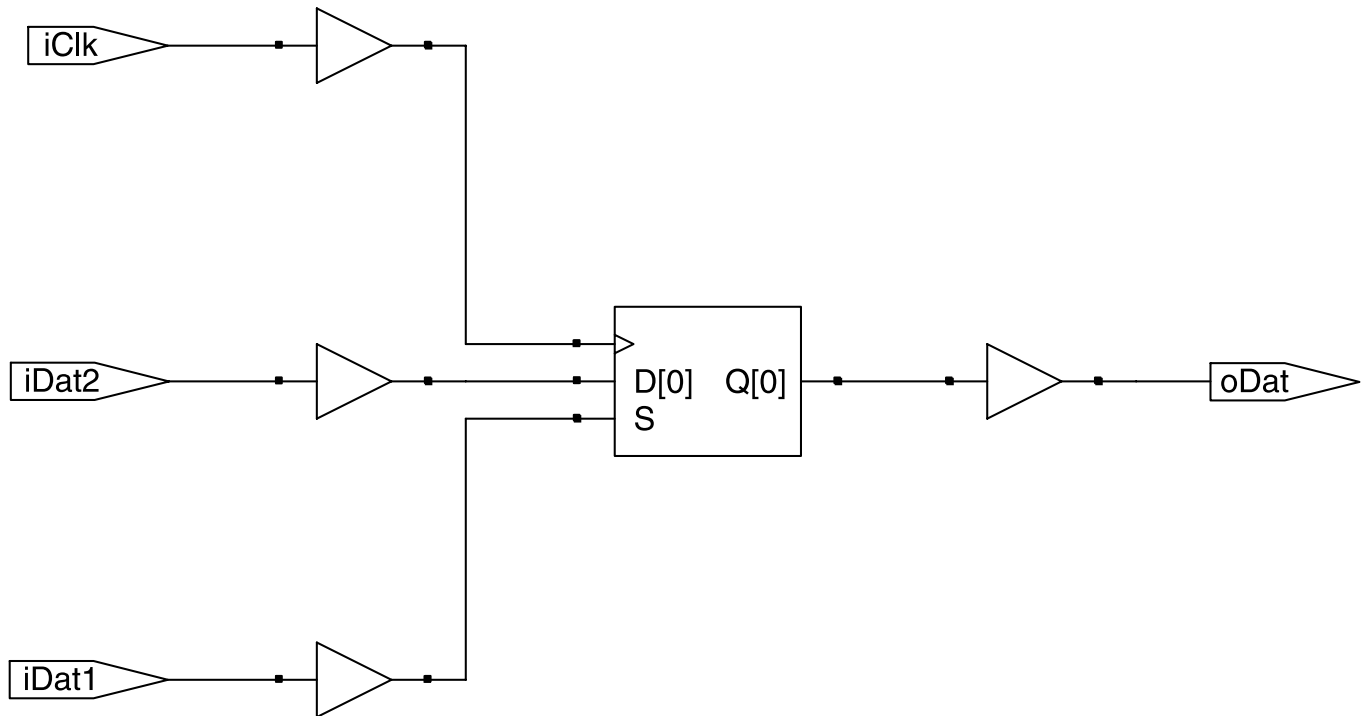


Figure 2.16 Optimization without reset.

Optimization for Power

Power Reduction Techniques

- In general, FPGAs are power hungry.
- Power consumption is determined by

$$P = V^2 \cdot C \cdot f$$


where V is voltage, C is load capacitance, and f is switching frequency

- In FPGAs, V is usually fixed, C depends on the number of switching gates and length of wires connecting all gates.
- To reduce power,
 - turn off gates not actively used,
 - have multiple clock domains,
 - reduce f .


Dual-Edge Triggered FFs

- A design that is active on both clock edges can reduce clock frequency by 50%.

Example 1

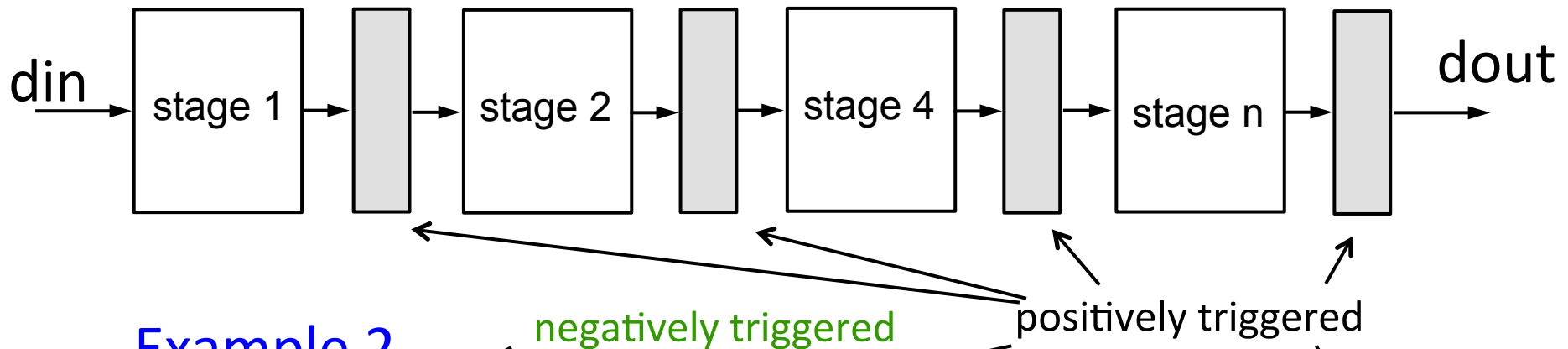

Example 2

 

Dual-EdgeTriggered FFs – Example

```
process(clk)
begin
    if (rising_edge(clk)) then
        reg(0) <= din;
        reg(2) <= reg(1);
    end if;
end process;
```

```
process(clk)
begin
    if(rising_edge(clk)) then
        reg(1) <= reg(0);
        reg(3) <= reg(2);
    end if;
end process;
```