

CDA 4253/CIS 6930 FPGA System Design

Modeling of Combinational Circuits

Hao Zheng
Dept of Comp Sci & Eng
USF

Reading

- P. Chu, *FPGA Prototyping by VHDL Examples*
 - **Chapter 3, RT-level combinational circuit**
 - **Sections 3.1 - 3.2, 3.5 - 3.7.**
- *XST User Guide for Virtex-6, Spartan-6, and 7 Series Devices*
 - **Chapter 3 and 7**

VHDL Model Template: Recap

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity entity_name is  
    port declarations  
end [entity] entity_name;  
  
ARCHITECTURE architecture_name OF entity_name IS  
    signal & component declarations  
BEGIN  
    Concurrent statements  
END [ARCHITECTURE] architecture_name;
```

Concurrent Statements

→ Simple concurrent signal assignment

→ $z \leq a \text{ xor } b$


→ Conditional signal assignment (when-else)

→ selected concurrent signal assignment (with-select-when)

→ Process statements

→ To be covered later

VHDL Modeling Styles


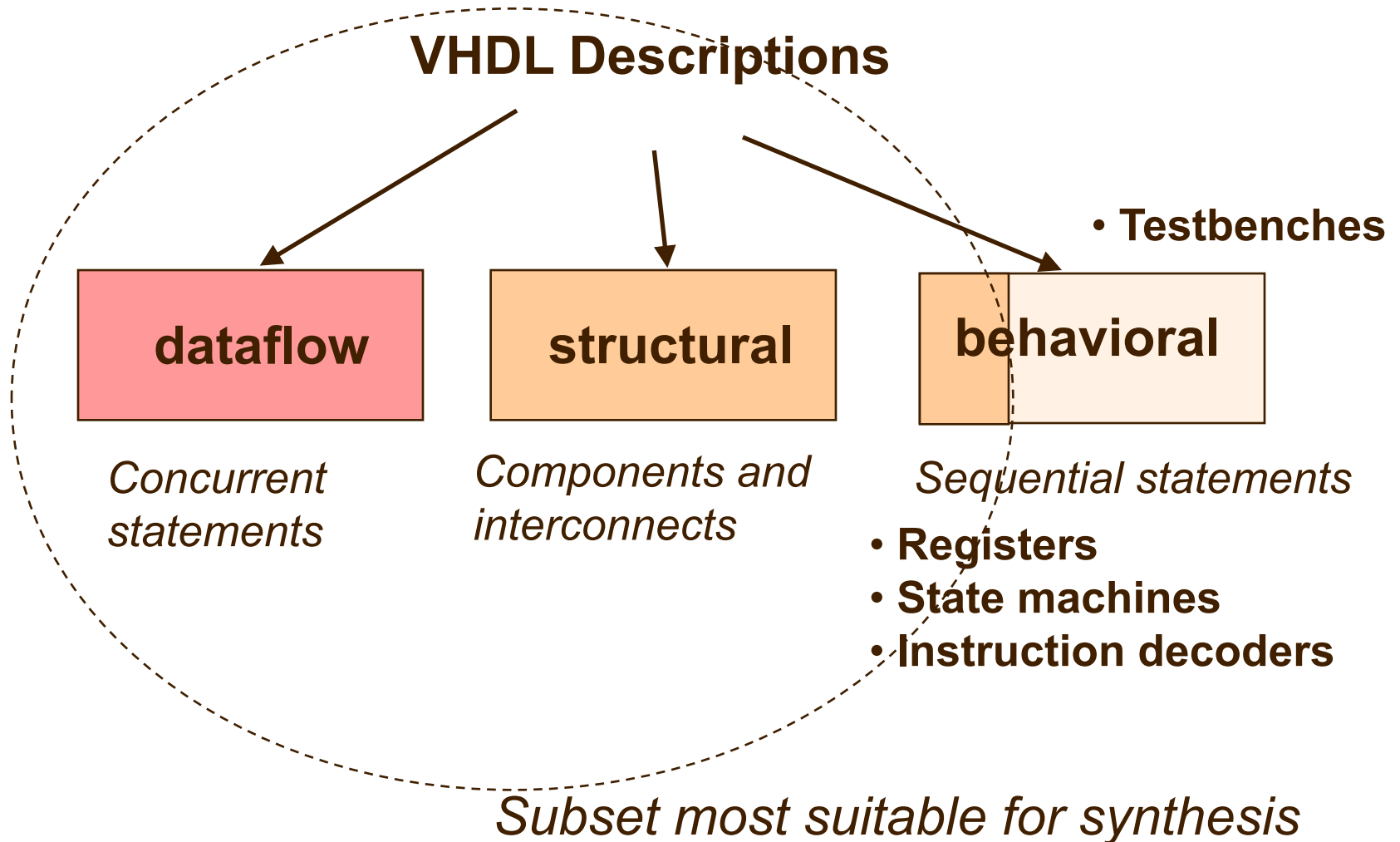


Combinational Circuit Building Blocks

Fixed Shifters & Rotators

Fixed Logical Shift Right in VHDL
  
```
SIGNAL A : STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL C : STD_LOGIC_VECTOR(3 DOWNTO 0);
```



srl: logic shift right



```
C <= A srl 1;
```

```
C <= '0' & A(3 downto 1);
```


Fixed Arithmetic Shift Right in VHDL

```
SIGNAL A : STD_LOGIC_VECTOR(3 DOWNTO 0);
```
 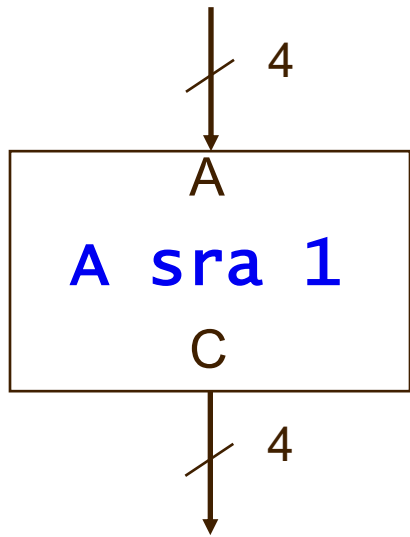
```
SIGNAL C : STD_LOGIC_VECTOR(3 DOWNTO 0);
```



sra: arithmetic shift left



```
C <= A sra 1;
```

```
c <= A(3) & A(3 downto 1);
```

Fixed Rotation in VHDL

```
SIGNAL A : STD_LOGIC_VECTOR(3 DOWNTO 0);
```
 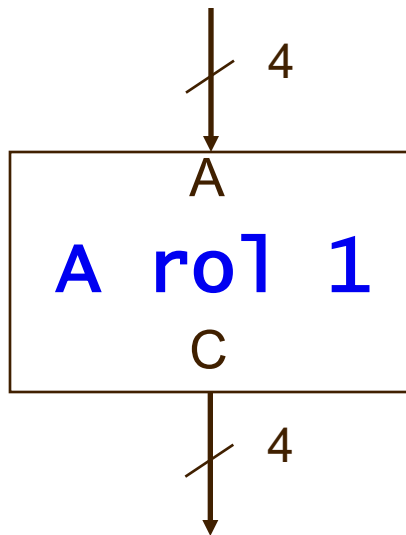
```
SIGNAL C : STD_LOGIC_VECTOR(3 DOWNTO 0);
```




rol: rotation to left


```
C <= A rol 1
```

Logic Gates


Basic Gates – AND, OR, NOT

 

(a) AND gates

 


(b) OR gates

 


(c) NOT gate

Basic Gates – NAND, NOR

 

(a) NAND gates

 


(b) NOR gates


Basic Gates – XOR

x_1	x_2	$f = x_1 \oplus x_2$
0	0	0
0	1	1
1	0	1
1	1	0

(a) Truth table

 

(b) Graphical symbol

 


(c) Sum-of-products implementation


Basic Gates – XNOR

x_1	x_2	$f = \overline{x_1 \oplus x_2}$
0	0	1
0	1	0
1	0	0
1	1	1

(a) Truth table

 


(b) Graphical symbol

 

(c) Sum-of-products implementation

1-Bit Full Adder

 

1-Bit Full Adder


```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY fa1b IS  
    PORT(  
        x : IN STD_LOGIC ;  
        y : IN STD_LOGIC ;  
        cin : IN STD_LOGIC ;  
        s : OUT STD_LOGIC ;  
        cout : OUT STD_LOGIC ) ;  
END fa1b;
```

1-Bit Full Adder

ARCHITECTURE dataflow OF fa1b IS
BEGIN

```
s      <=  x XOR y XOR cin ;  
cout   <=  (x AND y) OR (cin AND x)  
        OR (cin AND y) ;
```

END dataflow ;

 

Logic Operators

- Logic operators

and	or	nand	nor	xor	not	xnor
-----	----	------	-----	-----	-----	------

- Logic operators precedence

Highest



Lowest

			not			
and	or	nand	nor	xor	xnor	

No Implied Precedence

Wanted: $y = ab + cd$

Incorrect

$y \leq a \text{ and } b \text{ or } c \text{ and } d;$

equivalent to

$y \leq ((a \text{ and } b) \text{ or } c) \text{ and } d;$

equivalent to


$y = (ab + c)d$

Correct

$y \leq (a \text{ and } b) \text{ or } (c \text{ and } d);$

**Modeling Routing Structures
with
Conditional Concurrent Signal Assignment
(when-else)**

2-to-1 Multiplexer

 

(a) Graphical symbol

sel	f
0	W_0
1	W_1

(b) Truth table

2-to-1 Multiplexer

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT( w0, w1, sel : IN      STD_LOGIC ;
          f           : OUT     STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE dataflow OF mux2to1 IS
BEGIN
    f <= w0 WHEN sel = '0' ELSE
        w1;
END dataflow ;
```

Conditional Concurrent Signal Assignment

```
target_signal <= value1 when condition1 else  
                  value2 when condition2 else  
                  . . .  
                  valueN+1 when conditionN+1 else  
                  valueN;
```

- Branches are evaluated one by one from top to bottom.
- Induces priority among branches


Cascade of Multiplexers

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux_cascade IS
    PORT (w1, w2, w3      : IN  STD_LOGIC ;
          s1, s2         : IN  STD_LOGIC ;
          f              : OUT STD_LOGIC ) ;
END mux_cascade ;

ARCHITECTURE dataflow OF mux_cascade IS
BEGIN
    f  <= w1 WHEN s1 = '1'    ELSE
        w2 WHEN s2 = '1'    ELSE
        w3;
END dataflow ;
```


Cascade of Multiplexers

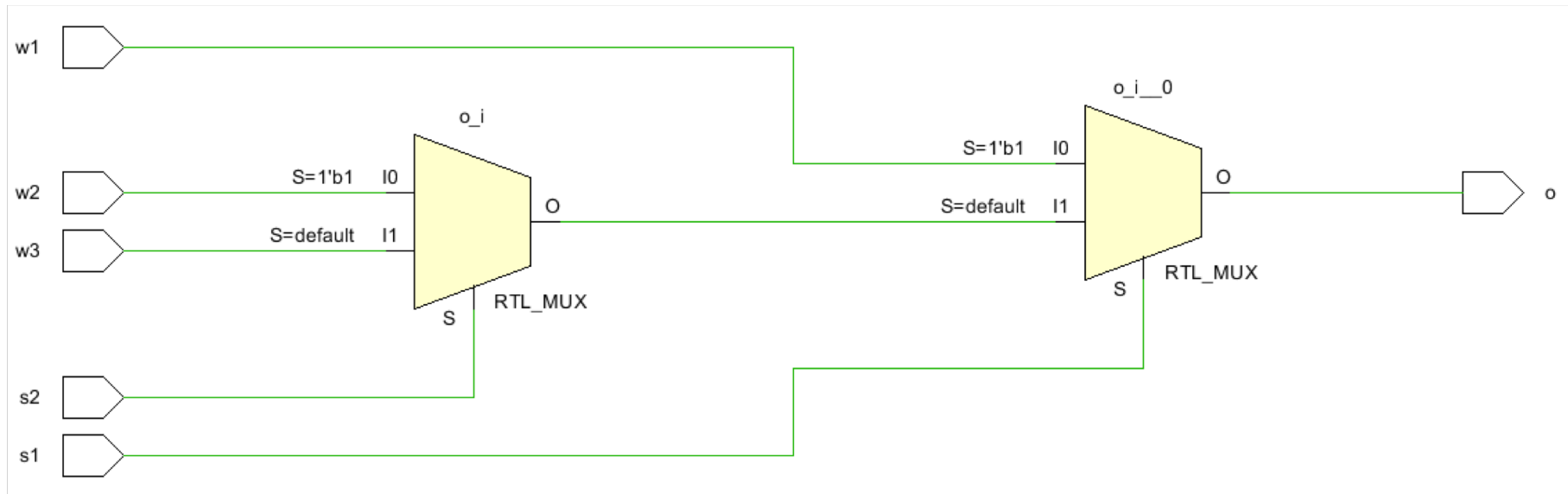

Notice the priority of selection.

Conditional Concurrent Signal Assignment
 
```
target_signal <= value1 when condition1 else  
                value2 when condition2 else  
                . . .  
                valueN+1 when conditionN+1 else  
                valueN;
```



More Operators

- Relational operators

=	/=	<	<=	>	>=
---	----	---	----	---	----

- Logic and relational operators precedence

Highest
↓
Lowest

=	/=	<	<=	>	>=
and	or	nand	nor	xor	xnor

not

Precedence of Logic and Relational Operators

Comparison

$$a = bc$$

Incorrect

... when $a = b$ and c else ...

equivalent to


... when $(a = b)$ and c else ...

Correct

... when $a = (b \text{ and } c)$ else ...

**Modeling Routing Structures
with
Selected Concurrent Signal Assignment
(with-select-when)**

4-to-1 Multiplexer

 

(a) Graphic symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table

No priority, and choices are disjoint.


A 4-to-1 Multiplexer

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux4to1 IS
    PORT( w0, w1, w2, w3      : IN      STD_LOGIC ;
          s                    : IN    STD_LOGIC_VECTOR(1 DOWNTO 0);
          f                    : OUT   STD_LOGIC ) ;
END mux4to1 ;

ARCHITECTURE dataflow OF mux4to1 IS
BEGIN
    WITH s SELECT
        f <=      w0 WHEN "00",
                 w1 WHEN "01",
                 w2 WHEN "10",
                 w3 WHEN OTHERS;
END dataflow;
```

default condition

 


Selected Concurrent Signal Assignment

```
with choice_expression select  
    target <= expression1 when choices_1,  
        expression2 when choices_2,  
        . . .  
        expressionN when choices_N;
```

*All choices are mutually exclusive
and
cover all values of choice_expression.*

Selected Concurrent Signal Assignment
 
```
with choice_expression select  
  target <= expression1 when choices_1,  
            expression2 when choices_2,  
            . . .  
            expressionN when choices_N;
```



Formats of Choices

- **when** *Expr*
- **when** *Expr_1* | ... | *Expr_N*
 - this branch is taken if any of *Expr_x* matches *choice_expression*
- **when others**

Formats of Choices - Example

```
with sel select
```


```
    y <= a when "000",  
        c when "001" | "111",  
        d when others;
```

Decoders

2-to-4 Decoder

En	w_1	w_0	y_3	y_2	y_1	y_0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0
0	x	x	0	0	0	0

(a) Truth table

 

(b) Graphical symbol


VHDL Code for a 2-to-4 Decoder

```
-- LIBRARY not shown
ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          En     : IN      STD_LOGIC ;
          y      : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END dec2to4 ;

ARCHITECTURE dataflow OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y      <= "0001" WHEN "100",
              "0010" WHEN "101",
              "0100" WHEN "110",
              "1000" WHEN "111",
              "0000" WHEN OTHERS ;
END dataflow ;
```

Encoders

Priority Encoder

 

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	x	x	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

VHDL code for a Priority Encoder

```
-- library not shown
```

```
ENTITY priority IS
```

```
    PORT (    w      : IN   STD_LOGIC_VECTOR(3 DOWNTO 0) ;
            y      : OUT   STD_LOGIC_VECTOR(1 DOWNTO 0) ;
            z      : OUT   STD_LOGIC ) ;
```

```
END priority ;
```

```
ARCHITECTURE dataflow OF priority IS
```

```
BEGIN
```


```
    y <= "11" when w(3) = '1' else
        "10" when w(2) = '1' else
        "01" when w(1) = '1' else
        "00" when others;
```

```
    z <= '0' when w = "0000" else
        '1' when others;
```

```
END dataflow ;
```

Adders

16-bit Unsigned Adder

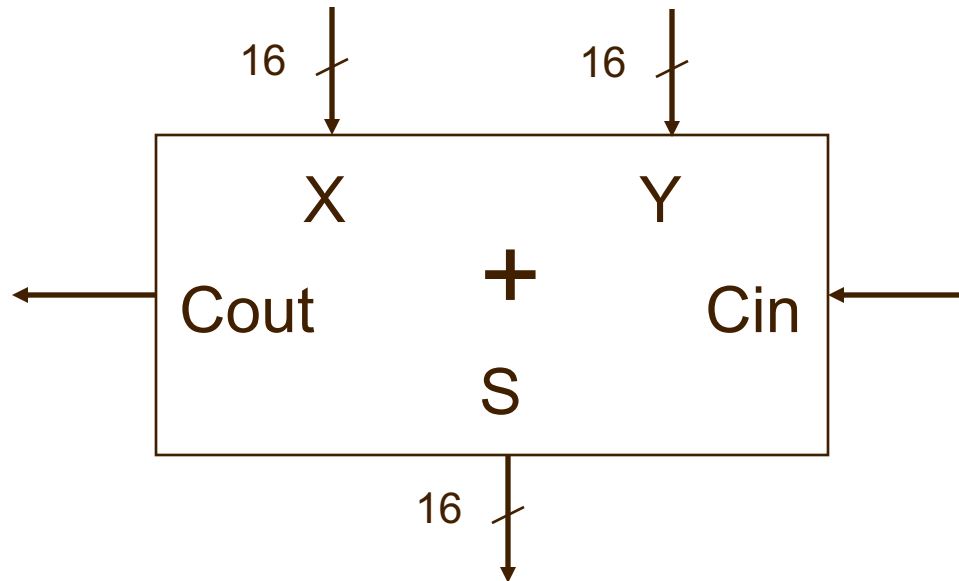

$$S = X + Y$$

Operations on Unsigned Numbers

For operations on **unsigned** numbers

USE

`ieee.numeric_std.all`

and

signals of the type **UNSIGNED**

and

conversion functions `std_logic_vector()`, `unsigned()`

OR USE

`ieee.std_logic_unsigned.all`

and

signals of the type **STD_LOGIC_VECTOR**

16-bit Unsigned Adder

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE ieee.std_logic_unsigned.all ; --non-IEEE standard
```

```
ENTITY adder16 IS  
    PORT( Cin          : IN    STD_LOGIC ;  
          X            : IN    STD_LOGIC_VECTOR(15 DOWNTO 0) ;  
          Y            : IN    STD_LOGIC_VECTOR(15 DOWNTO 0) ;  
          S            : OUT   STD_LOGIC_VECTOR(15 DOWNTO 0) ;  
          Cout         : OUT   STD_LOGIC ) ;  
END adder16 ;
```

```
ARCHITECTURE dataflow OF adder16 IS  
    SIGNAL Sum : STD_LOGIC_VECTOR(16 DOWNTO 0) ;  
BEGIN  
    Sum    <= ('0' & X) + Y + Cin ;  
    S     <= Sum(15 DOWNTO 0) ;  
    Cout  <= Sum(16) ;  
END dataflow ;
```

Addition of Unsigned Numbers (1)

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE ieee.numeric_std.all; -- IEEE standard
```

```
ENTITY adder16 IS  
    PORT( Cin          : IN    STD_LOGIC ;  
          X            : IN    STD_LOGIC_VECTOR(15 DOWNTO 0) ;  
          Y            : IN    STD_LOGIC_VECTOR(15 DOWNTO 0) ;  
          S            : OUT   STD_LOGIC_VECTOR(15 DOWNTO 0) ;  
          Cout         : OUT   STD_LOGIC ) ;  
END adder16 ;
```

Addition of Unsigned Numbers (2)

ARCHITECTURE dataflow OF adder16 IS

```
SIGNAL Xu, Yu : UNSIGNED(15 DOWNT0 0);
```

```
SIGNAL Su      : UNSIGNED(16 DOWNT0 0) ;
```

BEGIN

```
Xu <= unsigned(X);
```

```
Yu <= unsigned(Y);
```

```
Su <= ('0' & Xu) + Yu + unsigned('0' & cin)
```

```
;
```

```
S  <= std_logic_vector(Su(15 DOWNT0 0)) ;
```

```
Cout <= Su(16) ;
```

END dataflow ;

Signed and *unsigned* are arrays of *std_logic*.

Operations on Signed Numbers

For operations on `signed` numbers

- Either use
`ieee.numeric_std.all`,
signals of the type `SIGNED`, and
conversion `std_logic_vector()`, `signed()`
- Or use
`ieee.std_logic_signed.all`, and
signal type `STD_LOGIC_VECTOR`

Signed/Unsigned Types in `numeric_std`

→ Behave exactly like

`std_logic_vector`

→ They determine whether a given vector should be treated as a signed or unsigned number.

→ Prefer to use

`ieee.numeric_std.all;`

→ Use either `numeric_std` or `std_logic_unsigned` (or `signed`).

→ Do NOT mix them together.

Multipliers

Unsigned vs. Signed Multiplication

Unsigned


$$\begin{array}{r} 1111 \\ \times 1111 \\ \hline 11100001 \end{array}$$
$$\begin{array}{r} 15 \\ \times 15 \\ \hline 225 \end{array}$$

Signed

$$\begin{array}{r} 1111 \\ \times 1111 \\ \hline 00000001 \end{array}$$
$$\begin{array}{r} -1 \\ \times -1 \\ \hline 1 \end{array}$$

In Xilinx, a multiplier can be implemented either in a DSP or CLB

8x8-bit Unsigned Multiplier

 


```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
USE ieee.std_logic_unsigned.all;
```

```
entity mult8b is  
    port(...);  
end mult8b;
```

```
architecture arch of mult8b is  
begin  
    c <= a * b;  
end arch;
```

8x8-bit Signed Multiplier

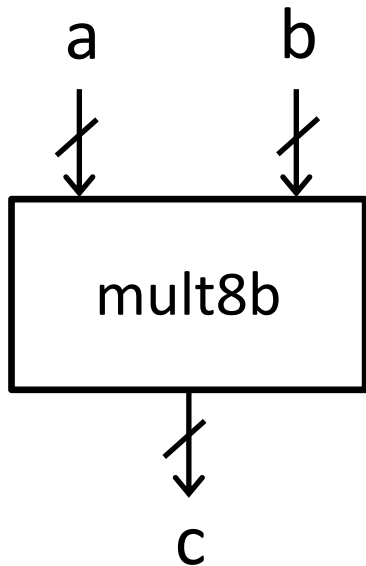

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
USE ieee.std_logic_signed.all;
```

```
entity mult8b is  
    port(...);  
end mult8b;
```

```
architecture arch of mult8b is  
begin  
    c <= a * b;  
end arch;
```

Signed/Unsigned Multiplication

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all ;

entity multiply is
    port(
        a : in STD_LOGIC_VECTOR(7 downto 0);
        b : in STD_LOGIC_VECTOR(7 downto 0);
        cu : out STD_LOGIC_VECTOR(15 downto 0);
        cs : out STD_LOGIC_VECTOR(15 downto 0));
end multiply;

architecture dataflow of multiply is
begin
    -- signed multiplication
    cs <= std_logic_vector(signed(a)*signed(b));
    -- unsigned multiplication
    cu <=
        std_logic_vector(unsigned(a)*unsigned(b));
end dataflow;
```

Multiplication with Constants

→ If either A or B in $A * B$ is a constant, more efficient implementation with shifts and additions.

$$A * 9$$

can be implemented as

$$A \ll 3 + A$$

Operators in numeric_std Package

overloaded operator	description	data type of operand a	data type of operand b	data type of result
abs a - a	absolute value negation	signed		signed
a * b a / b a mod b a rem b a + b a - b	arithmetic operation	unsigned unsigned, natural signed signed, integer	unsigned, natural unsigned signed, integer signed	unsigned unsigned signed signed
a = b a /= b a < b a <= b a > b a >= b	relational operation	unsigned unsigned, natural signed signed, integer	unsigned, natural unsigned signed, integer signed	boolean boolean boolean boolean

Parameterized Models

Design Reuse

→ How to design for the 32-bit problem below?

$$O = A + B + C$$

→ Create a new 32-bit adder

→ waste of effort

→ Reuse previously designed adder

→ but it is 16-bit

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity gen_add_w_carry is
    generic(N : integer := 4);
    port(
        a, b : in  std_logic_vector(N - 1 downto 0);
        cout : out std_logic;
        sum  : out std_logic_vector(N - 1 downto 0)
    );
end gen_add_w_carry;

architecture arch of gen_add_w_carry is
    signal a_ext, b_ext, sum_ext : unsigned(N downto 0);
begin
    a_ext    <= unsigned('0' & a);
    b_ext    <= unsigned('0' & b);
    sum_ext  <= a_ext + b_ext;
    sum     <= std_logic_vector(sum_ext(N - 1 downto 0));
    cout    <= sum_ext(N);
end arch

```

Instances of Generic Models

— instantiate 8-bit adder

```
adder_8_unit: work.gen_add_w_carry(arch)
```

```
  generic map(N=>8)
```

```
    port map(a=>a8, b=>b8, cout=>c8, sum=>sum8));
```

— instantiate 16-bit adder

```
adder_16_unit: work.gen_add_w_carry(arch)
```

```
  generic map(N=>16)
```

```
    port map(a=>a16, b=>b16, cout=>c16, sum=>sum16));
```

— instantiate 4-bit adder

— (generic mapping omitted, default value 4 used)

```
adder_4_unit: work.gen_add_w_carry(arch)
```

```
  port map(a=>a4, b=>b4, cout=>c4, sum=>sum4));
```

A Word on Generics

- Generics are typically **integer** values
 - In this class, the entity inputs and outputs should be `std_logic` or `std_logic_vector`.
 - But the generics should be **integer**.
- Generics are given a default value
 - **GENERIC (N : INTEGER := 16) ;**
 - This value can be overwritten when entity is instantiated as a component
- Generics are very useful when instantiating an often-used component
 - Need a 32-bit register in one place, and 16-bit register in another
 - Can use the same generic code, just configure them differently

Constants – Make Code More Readable

Syntax:

```
constant name : type := value;
```

Examples:

```
constant init_val : STD_LOGIC_VECTOR(3 downto 0) := "0100";  
constant ANDA_EXT : STD_LOGIC_VECTOR(7 downto 0) := x"B4";  
constant counter_width : INTEGER := 16;  
constant buffer_address : INTEGER := x"FFFE";  
constant clk_period : TIME := 20 ns;  
constant strobe_period : TIME := 333.333 ms;
```

Constants vs Generics

→ Constants:

- Create symbolic names
- Make code more readable
- Declared in packages, entity, or architecture.
- Cannot create generic designs: still need two design entities for Adder_8b and Adder_32b.

→ Generics:

- Can be passed through design hierarchy through component instantiation
- Used for creating generic designs: a single design entity Adder for Adder_8b and Adder_32b.

Binary to BCD Conversion

Shift and Add-3 (Double-Dabble)

```
for(i=0; i<8; i++) {  
    // add 3 to a column if it is >= 5  
    for each column  
        if (column >= 5)  
            column += 3;  
    // shift binary digits left 1  
    Hundred << 1;  
    Hundreds[0] = Tens[3];  
    Tens << 1;  
    Tens[0] = Ones[3];  
    Ones << 1;  
    Ones[0] = Binary[7];  
    Binary << 1;  
}
```

Shift and Add-3 (Double-Dabble)

1. If the binary value in any of the BCD columns is 5 or greater, add 3 to that value in that BCD column.
2. Shift the binary number left one bit.
3. If 8 shifts have taken place, the BCD number is in the *Hundreds*, *Tens*, and *Ones* column. Terminate
4. Otherwise, go to 1.

Example:

Hundreds	Tens	Ones	Binary
0000	0000	0000	11110011

Shift and Add-3 (Double-Dabble)

100's	10's	1's	Binary	Operation
0000	0000	0000	10100010	

Shift and Add-3 (Double-Dabble)

100's	10's	1's	Binary	Operation
0000	0000	0000	10100010	
0000	0000	0001	0100010	<< 1

Shift and Add-3 (Double-Dabble)

100's	10's	1's	Binary	Operation
0000	0000	0000	10100010	
0000	0000	0001	0100010	<< 1
0000	0000	0010	100010	<< 1

Shift and Add-3 (Double-Dabble)

100's	10's	1's	Binary	Operation
0000	0000	0000	10100010	
0000	0000	0001	0100010	<< 1
0000	0000	0010	100010	<< 1
0000	0000	0101	00010	<< 1
0000	0000	1000	00010	+3

Shift and Add-3 (Double-Dabble)

100's	10's	1's	Binary	Operation
0000	0000	0000	10100010	
0000	0000	0001	0100010	<< 1
0000	0000	0010	100010	<< 1
0000	0000	0101	00010	<< 1
0000	0000	1000	00010	+3
0000	0001	0000	0010	<< 1
0000	0010	0000	010	<< 1
0000	0100	0000	10	<< 1

Shift and Add-3 (Double-Dabble)

100's	10's	1's	Binary	Operation
0000	0000	0000	10100010	
0000	0000	0001	0100010	<< 1
0000	0000	0010	100010	<< 1
0000	0000	0101	00010	<< 1
0000	0000	1000	00010	+3
0000	0001	0000	0010	<< 1
0000	0010	0000	010	<< 1
0000	0100	0000	10	<< 1
0000	1000	0001	0	<< 1
0000	1011	0001	0	+3

Shift and Add-3 (Double-Dabble)

100's	10's	1's	Binary	Operation
			1010 0010	← 162
		1	010 0010	<< #1
		10	10 0010	<< #2
		101	0 0010	<< #3
		1000		add 3
	1	0000	0010	<< #4
	10	0000	010	<< #5
	100	0000	10	<< #6
	1000	0001	0	<< #7
	1011			add 3
1	0110	0010		<< #8

↑ 1
 ↑ 6
 ↑ 2

Goto wiki for more information and VHDL implementation


Summary

- More concurrent statements for DF modeling
 - describing routing structures
- Modeling of basic combinational circuit blocks
 - Adders, multipliers, muxes, encoder/decoder
- Generic design modeling
 - Using VHDL generics

Backup

Comparators

2-bit Number Comparator

 

4-bit Unsigned Number Comparator

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all ;

entity compare is
    port( A, B      : in      STD_LOGIC_VECTOR(1 downto 0);
          AeqB     : out     STD_LOGIC );
end compare ;

architecture dataflow of compare is
begin
    AeqB <= '1' when A = B else
           '0';
end dataflow ;
```

4-bit Unsigned Number Comparator

```
library ieee;
use ieee.std_logic_1164.all;

entity compare is
    port( A, B      : in      STD_LOGIC_VECTOR(1 downto 0);
          AeqB     : out     STD_LOGIC );
end compare ;
-- Create a different model?
architecture dataflow of compare is
begin

end dataflow ;
```


4-bit Signed Number Comparator


```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_signed.all;

entity compare is
    port( A, B          : in  STD_LOGIC_VECTOR(1 downto 0);
          AeqB         : out STD_LOGIC);
end compare ;

architecture dataflow of compare is
begin
    AeqB  <= '1' when A = B else
            '0';
end dataflow ;
```


Hexadecimal to 7-Segment Display

7-Segment Display

 


To illuminate a segment, the corresponding control signal should be driven **low**.

7-Segment Display

 

To illuminate a segment, the corresponding control signal should be driven **low** – A = '0,' ..., F = '0', G = '1'

7-Segment Display

 


To illuminate a segment, the corresponding control signal should be driven **low** – A = '0,' ..., E = '1', F = '0', G = '0'

Hex to 7-Segment


Hex Input	7-Segment Control GFE...BCA
0000 (0)	1000000
0001 (1)	1111001
0010 (2)	0100100
0011 (3)	0110000
0100 (4)	0011001
0101 (5)	0010010
0110 (6)	0000010
0111 (7)	1111000
1000 (8)	0000000
1001 (9)	0010000
1010 (A)	0001000

7-Segment Display

 

- All four displays share common segment control signals.
- Only one display can be illuminated at a time when signal AN_x is driven high.


7-Segment Display Controller

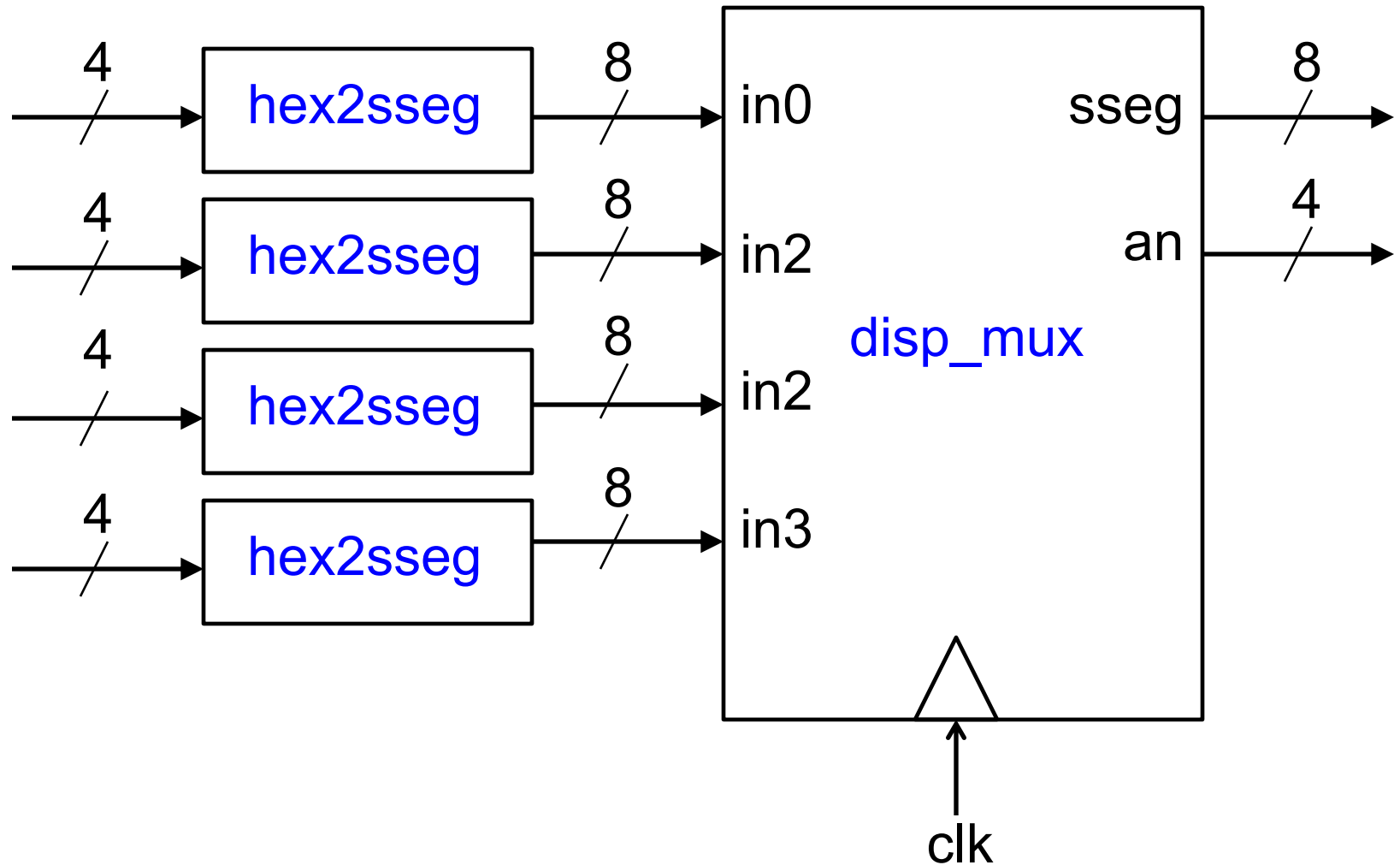

BCD to Binary Conversion


1. Right shift bcd1, with the LSB shifting to the MSB of bcd0.
2. Right shift bcd0, with the LSB shifting to the MSB of bin.
3. If bcd0 is now > 4 , subtract 3
4. repeat steps 1-3, 7 times.

8-bit Variable Rotator Left


 


Tri-State Buffers

Tri-State Buffers

 

(a) A tri-state buffer

  


(b) Equivalent circuit


e	x	f
0	0	Z
0	1	Z
1	0	0
1	1	1

(c) Truth table


Four types of Tri-state Buffers

 


(a)

 

(b)

 

(c)

 

(d)

Tri-state Buffer – Example (1)


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

entity tri_state is
    port(      ena, input :      IN STD_LOGIC;
           output       :      OUT STD_LOGIC);
end tri_state;

architecture dataflow of tri_state is
begin
    output <=  input when (ena = '1') else
               'Z';
end dataflow;
```

ROM

ROM 8x16 example (1)

 

ROM 8x16 example (2)

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;

entity rom is
    port (
        Addr : in    STD_LOGIC_VECTOR(2 downto 0);
        Dout : out   STD_LOGIC_VECTOR(15 downto 0));
end rom;
```

-- architecture body is defined on the next slide

ROM 8x16 example (3)

architecture dataflow of rom is

```
    signal temp: integer range 0 to 7;
    type vector_array is array(0 to 7) of
        std_logic_vector(15 downto 0);
    constant memory : vector_array := (
        X"800A",
        X"D459",
        X"A870",
        X"7853",
        X"650D",
        X"642F",
        X"F742",
        X"F548");
```

begin

```
    temp    <= to_integer(unsigned(Addr));
    Dout    <= memory(temp);
```

end dataflow;