

# **CIS 4930 Digital System Testing Modeling**

Dr. Hao Zheng  
Comp Sci & Eng  
U of South Florida


# Reading

- Chapter 2

## 2.1 Basic Concepts

- Functional modeling at logic level
- Functional modeling at register level
- Structural models

# Black Box View

 

- A system can be viewed as a black box i.e., generates **outputs** in response **to inputs**.
- Behavior is defined by the I/O mapping.
  - i.e. value transformation
  - Different value representations at different levels.

# Behavioral/Functional Model

- System **Behavior** is defined by
  - I/O Mapping occurs over time
- A **logic function** is a I/O Mapping without timing.
- A **functional model** is a representation of logic function
- A **behavioral model** is
  - A functional Model + A representation of timing relations

# Structural Model

- Collection of interconnected smaller boxes called components/elements
- Often hierarchical
  - A component itself represented by a structural model.
- Bottom-level boxes known as **primitive** elements
- Can shown as block Diagrams, or schematics
- In practice structural and functional are inter-mixed.
- Often necessary to describe large systems.

## 2.2 Functional Modeling at Logic Level

- Truth Tables
- Primitive Cubes
- State Tables
- Flow Tables
- BDDs – Binary Decision Diagrams
- Programs

# Truth Tables & Primitive Cubes

$x_1$	$x_2$	$x_3$	$Z$
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

(a)

$x_1$	$x_2$	$x_3$	$Z$
$x$	1	0	0
1	1	$x$	0
$x$	0	$x$	1
0	$x$	1	1

(b)

**Figure 2.2** Models for a combinational function  $Z(x_1, x_2, x_3)$  (a) truth table (b) primitive cubes



# Cubical Notation

$x_1$	$x_2$	$x_3$	$Z$
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

- First two rows can be combined  
 $00x \mid 1$   
where  $x$  is a don't care
- A cube of a function  $Z(x_1, x_2, x_3)$  has the form  
 $(v_1, v_2, v_3 \mid v_Z)$   
where  $v_Z = Z(v_1, v_2, v_3)$
- A cube of  $Z$  can represent multiple rows in a truth table

# Cubical Notation

- If cube  $q$  can be obtained from cube  $p$  by replacing one or more  $x$  in  $p$  by 0 or 1 then  $p$  **covers**  $q$

Eg:  $00x \mid 1$  covers cubes  $000 \mid 1$  and  $001 \mid 1$

# Implicants

- An **implicant**  $g$  of  $Z$  is a sub-function such that
$$(g = 1) \Rightarrow (Z = 1)$$
- An implicant “covers” one or more minterms in a truth table.
  - A disjunction of some minterms.
- If an implicant covers at least one row that is not covered by any other implicants, it is known as a **prime implicant**.

# Prime Implicant and Primitive Cube

- Cube  $00x \mid 1$  represents implicant

$$\overline{x_1} \overline{x_2}$$

- A cube that represents a prime implicant is known as **primitive cube**.

# Primitive Cube Representation

$x_1$	$x_2$	$x_3$	$Z$
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

(a)

$x_1$	$x_2$	$x_3$	$Z$
$x$	1	0	0
1	1	$x$	0
$x$	0	$x$	1
0	$x$	1	1

(b)

Compact  
Representation  
of function  $Z$

**Figure 2.2** Models for a combinational function  $Z(x_1, x_2, x_3)$  (a) truth table  
(b) primitive cubes

# Intersection Operator

$\cap$	0	1	$x$
0	0	$\emptyset$	0
1	$\emptyset$	1	1
$x$	0	1	$x$

$x_1$	$x_2$	$x_3$	$Z$
$x$	1	0	0
1	1	$x$	0
$x$	0	$x$	1
0	$x$	1	1

Figure 2.3 Intersection operator


Find  $Z$  for 001

- $x10 \cap 001$  -- Inconsistent
- $11x \cap 001$  -- Inconsistent
- $x0x \cap 001$  -- Consistent
- $0x1 \cap 001$  -- Consistent

Output is  $Z = 1$
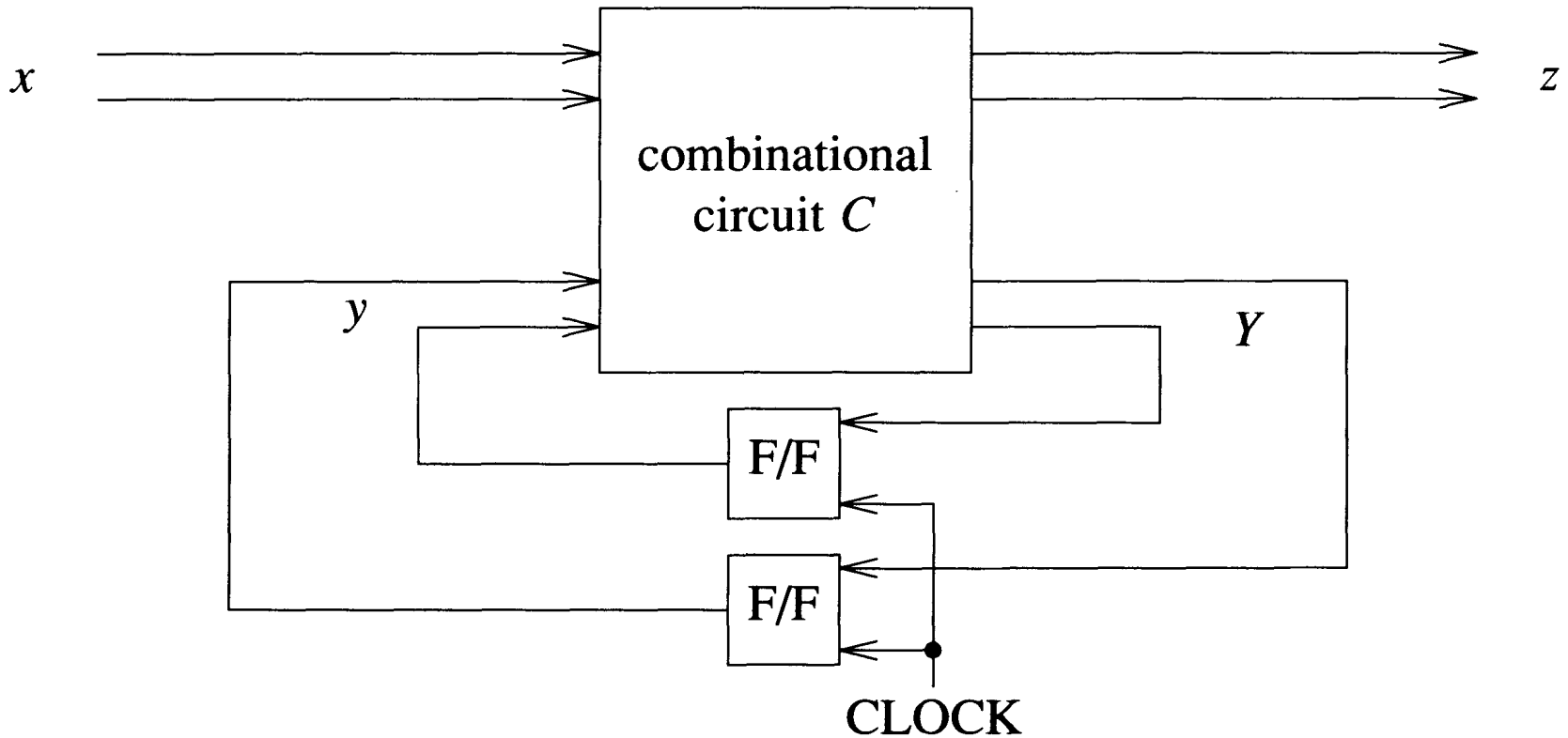
# Modeling Synchronous Sequential Circuit

- Canonical structure of synchronous circuits



# State Table Representation

- FSM – Finite State Machine can be represented by a state table
- Inputs are sampled at regular intervals and next state and output computed


		$x$	
		0	1
$q$	1	2,1	3,0
	2	2,1	4,0
	3	1,0	4,0
	4	3,1	3,0

$N(q,x), Z(q,x)$


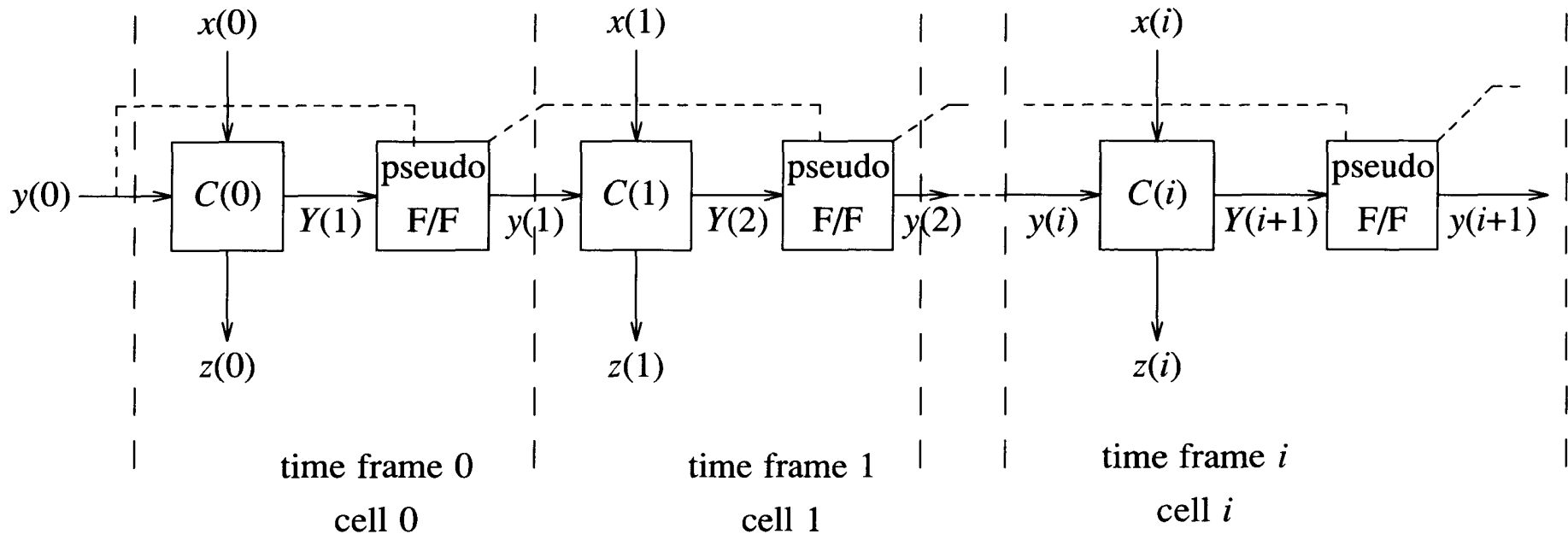
# Pseudo-combinational -- Iterative Array

- Unroll seq circuit  $\rightarrow$  pseudocombinational cir.



# Asynchronous Circuit

- Represented by a flow table
- Single input change can lead to multiple state changes until a stable configuration is reached
- Stable configurations are shown in **bold** font

	$x_1x_2$			
	00	01	11	10
1	<b>1,0</b>	5,1	2,0	<b>1,0</b>
2	1,0	<b>2,0</b>	<b>2,0</b>	5,1
3	<b>3,1</b>	2,0	4,0	<b>3,0</b>
4	3,1	5,1	4,0	<b>4,0</b>
5	3,1	<b>5,1</b>	4,0	<b>5,1</b>

Figure 2.7 A flow table

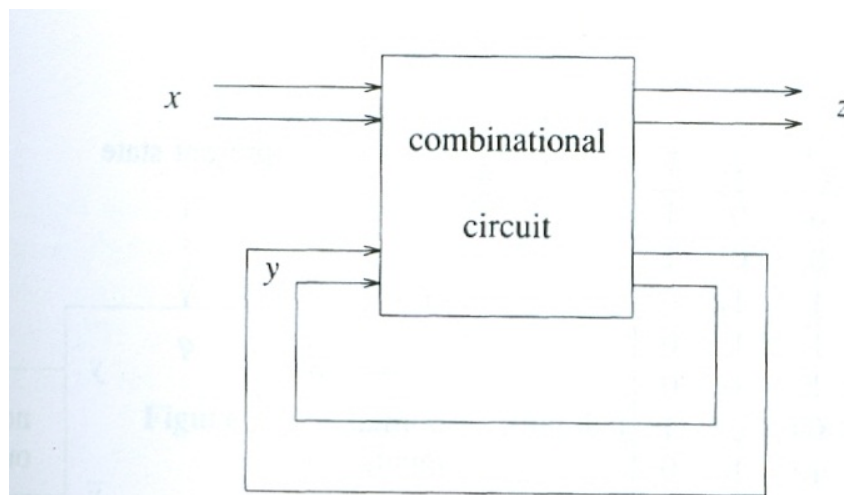
 


Figure 2.8 Canonical structure of an asynchronous sequential circuit

# Binary Decision Diagrams (BDDs)

- A graph representation of circuit functions

 


**Figure 2.11** Binary decision diagram of  $f = \bar{a}b\bar{c} + ac$


# Constructing BDD

<i>a</i>	<i>b</i>	<i>c</i>	<i>f</i>
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


(a)




(b)

 


(b)

 

(c)

 

(d)

 

(e)

# BDD for a JK FF

 


Figure 2.12 Binary decision diagram for a JK F/F

# Program as Functional Model

## Assembly Program

 


Figure 2.14

```
LDA A /* load acc with A */
AND B /* compute A.B */
AND C /* compute A.B.C */
STA E /* store partial result */
LDA D /* load acc with D */
INV /* compute not D */
OR E /* compute A.B.C + ~(D) */
STA Z /* store results */
```

## C Program

```
E = A & B & C ;
F = ~ D ;
Z = E | F ;
```

“Compiled Code Model”

## 2.3 Functional Modeling at Register Level

- System model at register and instruction set levels
- Storage declarations:  

```
register IR [0 → 7]           //8-bit register  
memory ABC [0 →255; 0 → 15] // 256 word memory
```
- Data paths implicitly defined with operations on registers.
- Data processing by primitive operators:  

```
C = A + B           // add two registers A and B
```



# RTL constructs

- Control flow:
  - **if**  $X$  **then**  $C = A + B$
  - **if** (  $CLOCK$  *and* (  $AREG < BREG$  )) **then**  $AREG = BREG$
  - **test** (  $IR [ 0 \rightarrow 3 ]$  )
    - case 0: operation0*
    - case 1: operation1*
    - :
  - testend**

# FSM modeling

- One block per state
- Only one state is active/current at any time

```
state S1, S2, S3 /* state register */
```

```
S1: if X then
```

```
    begin
```

```
         $P = Q + R$ 
```

```
        go to S2
```

```
    end
```

```
    else
```

```
         $P = Q - R$ 
```

```
        go to S3
```

```
S2: ...
```

# Procedural and Non-procedural RTLs

- Procedural RTLs (sequential semantics, ex. C)
  - Use a sequential programming language
  - implicit cycle-based timing model (i.e., assures that the state of the model accurately reflects state of processor at the end of a cycle)
- Non-procedural RTLs (concurrent semantics, ex. VHDL)
  - Statements conceptually executed in parallel
- Example:  $A = B$   
 $C = A$ 
  - if the above is procedural code, register C gets value B after execution
  - If the above is non-procedural code, then C gets old value of A

# Timing Modeling

- Explicitly specify delay to add more details.
  - Make a model more accurate.
- Examples:

```
// delay updating C by 100.
```

```
C = A + B, delay = 100
```

```
// delay every update to C by 100.
```

```
delay C 100
```

# 2.4 Structural Models

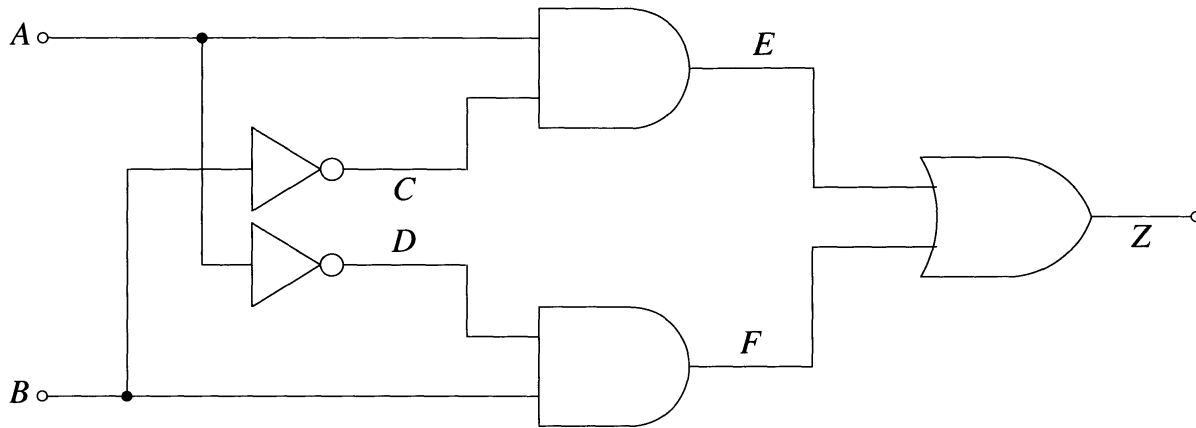


Figure 2.15 Schematic diagram of an XOR circuit


CIRCUIT XOR  
INPUTS = A,B  
OUTPUTS = Z

NOT D, A  
NOT C, B  
AND E, (A, C)  
AND F, (B, D)  
OR Z, (E, F)

Connections are implicitly done via name matching.

# Fanout-Free Circuit


- If a gate drives more than one gate then it has a **fanout**.
- A fanout-free circuit can be represented as a tree

 

**Figure 2.17** Fanout-free circuit and its graph (tree) representation

# Reconvergent Fanout


- A signal fans out into two or more paths which later converge at a gate.
- Common in real circuits
- Makes fault detection problem more difficult

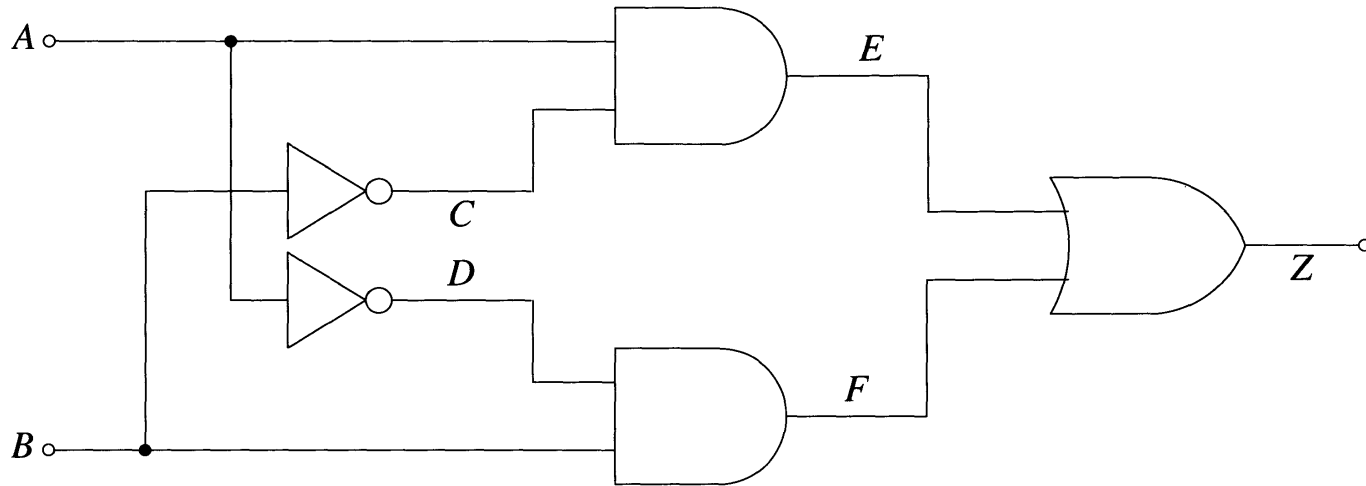

**Figure 2.15** Schematic diagram of an XOR circuit
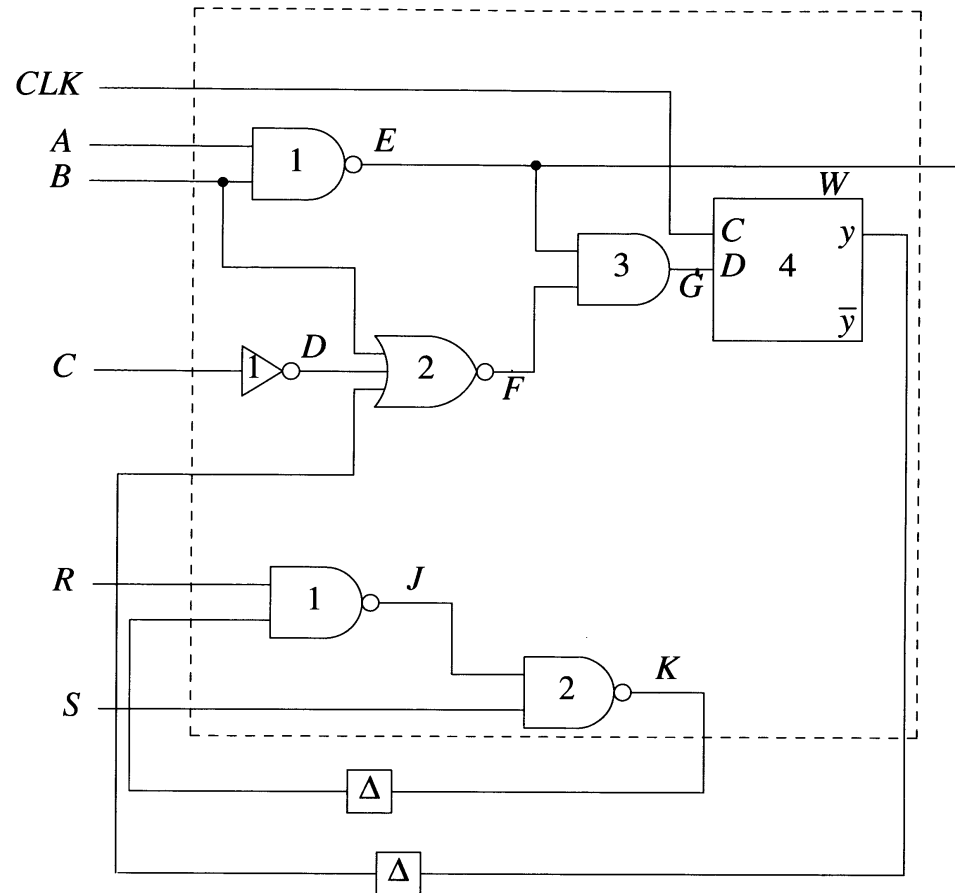
# Logic Levels

- Logic level of a gate is its distance from primary inputs
- Can be computed in a breadth-first manner






# Summary

- Digital system model
  - representation of the actual system
  - can be done at logic and RT-levels
- Behavioral model = Functional Model + Timing
- Models for combinational circuits: truth table, primitive cubes, BDDs, programs (compiled-code models)
- Sequential circuits: state tables, RT level case statement
- Reconvergent Fanout – signal branches and later converges on a gate
- Non-procedural language used for RTL modeling to mimic concurrent execution of the hardware

# Backup

# Fanout Terminology

- Stem and fanout branches

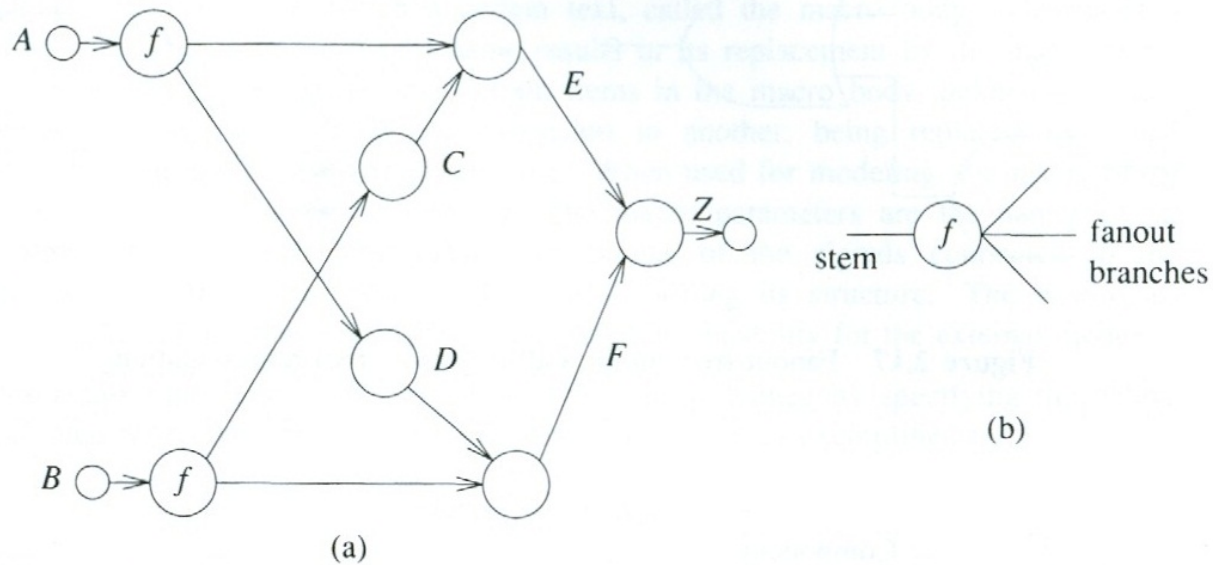

**Figure 2.19** (a) Graph model for the circuit of Figure 2.15 (b) A fanout node