

CIS 4930. Digital System Testing Fault Modeling

Dr. Hao Zheng
Comp. Sci & Eng
U of South Florida

Overview

- Logic Fault Models
- Fault Detection & Redundancy
- Fault Equivalence & Fault Location
- Fault Dominance
- Single Stuck-Fault (SSF) Model
- Multiple Stuck-Fault (MSF) Model
- Summary

Recap: Testing Big Picture

- A circuit defect leads to a fault.
- A fault can cause a circuit error.
- A circuit error can result in a circuit failure.
- Testing a circuit:
 - Apply test vectors to the circuit inputs.
 - Compare circuit output responses to correct ones.
- Exhaustive testing
 - 2^n test vectors required for a n -input comb. circuit.
 - Difficult for comb. circuit, impossible for seq. circuit.

Recap: Testing Big Picture

- Goal: find a small set of test vectors that target specific faults.
 - Ideally, no redundant test vectors for the same fault.
 - The set contains enough test vectors to uncover all target faults.
- Impossible to achieve 100% fault coverage.
 - Due to undetectable faults.

Recap: Physical Faults

Recall that we have 4 types of errors

- Design Errors
- Fabrication Errors
- Fabrication Defects
- Physical Failures




Physical Faults

Physical Faults can be:


- Permanent
- Intermittent
- Transient

Recap: Logical Faults

 - Physical faults are difficult to handle mathematically
- Therefore, for a physical fault we identify equivalent logical fault
 - Example:



Physical fault
- Inputs are shorted

 

Logical fault
- Gate now behaves as an inverter

4.1 Logic Fault Models

- Fault model: representation of physical faults and their natures at logic level.
- Recall that
 - Behavior = Function + Timing
- Therefore, we can talk about two types of faults:
 - Logical Faults – modify circuit logic function.
 - Delay Faults - modify circuit operating speed.
- Our focus will be on Logical Faults

Logical Fault Modeling - Advantages

- Fault analysis becomes a logical problem.
 - Test can start before silicon is available.
- Fault analysis become less complex.
 - *Many physical faults can be modeled by the same logical fault*
- Technology independent
- Tests derived for logical faults may be used for physical faults whose effect
 - not completely understood
 - or too complex to analyze

Structural and Functional Faults

→ Structural faults

- Faults defined on a structural circuit model.
- Effect: modify interconnections

→ Functional faults

- Faults defines on a functional circuit model
- Effect: modify truth table etc.

→ Intermittent & Permanent Faults

- Statistical data on probability of occurrence of transient/intermittent faults are difficult to have.
- Our focus in this discussion is on structural and permanent faults

Single Fault Assumption - Justification

- Assumption – one logical fault in the system.
- Justification
 - Frequent testing strategy (test often so that prob. of multiple faults developing in between too low)
 - Usually tests derived for individual single faults are applicable for detecting multiple faults composed of the single ones.

Structural Fault Models

→ Assumptions:

- Components are fault free and,
- Only interconnections are affected – shorts & opens.


→ **Stuck-at-v Fault:**

- **Short** (with supply/gnd) or **Open** lines behave as “stuck at” fixed logic value v ($v \in \{0,1\}$)

→ **Bridging fault:**


- Short between two lines → usually new logic function (AND or OR bridging)
- We will discuss bridging faults later

Single Stuck Fault – Open Line

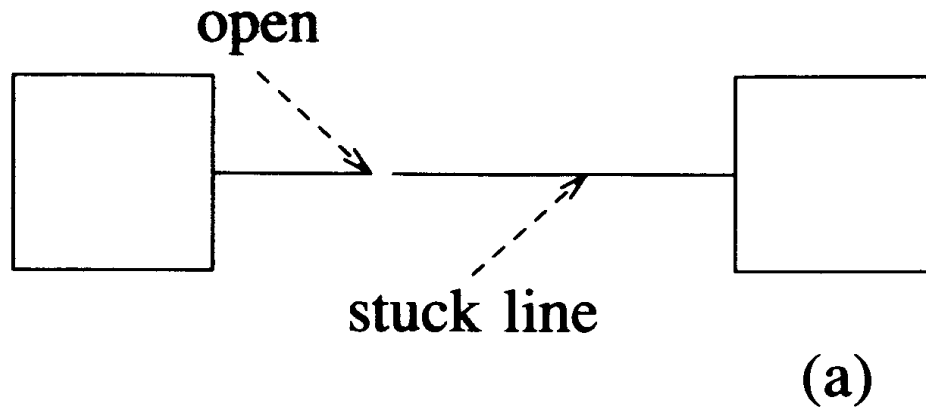

- Open on an unidirectional line
- Unconnected input assumes a constant logic value
- Single logical fault, *i-stuck-at-a* can represent
 - Line *i* open
 - Line *i* shorted to Vdd or GND ($a=1$ or $a=0$)
 - Internal fault in component driving line *i*

Multiple Stuck Fault

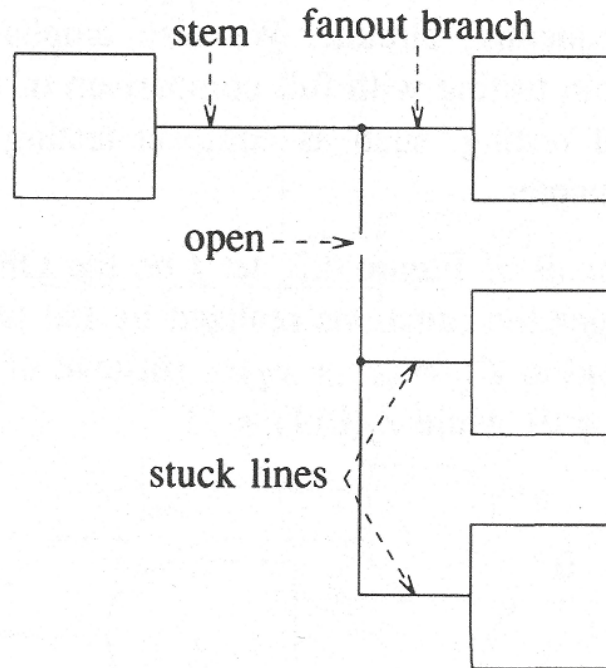


(b)

- Single open can result in multiple faults
- Under single fault model, we need to consider faults on all fanout branches separately.

4.2 Fault Detection and Redundancy

Fault Detection – Combinational Circuits

 

- Input vector t to N results in output response $Z(t)$.
- Test $T = \langle t_1, t_2 \dots t_m \rangle$ will yield $\langle Z(t_1), Z(t_2), \dots Z(t_m) \rangle$

Fault Detection – Comb Circuits

Definition 4.1 A test (vector) t **detects** a fault f
iff

$$z_f(t) \neq z(t)$$

- Note the above is applicable to comb. circuits only.
- Test vectors in T can be applied in any order, so T is *set of tests*
- Applicable to *edge-pin testing*
 - Components are assumed to be fault free.

Example 1

 


Figure 4.2

Let f = OR-bridging fault between x_1 and x_2

$Z_1 =$ _____ $Z_{1f} =$ _____

$Z_2 =$ _____ $Z_{2f} =$ _____

Give a test vector that detects the fault:

$\langle x_1, x_2, x_3 \rangle =$ _____

Fault Detection and Test Vectors

→ For a single-output circuit, a test t that detects a fault f makes


→ $Z(t) = 0$ and $Z_f(t) = 1$ or

→ $Z(t) = 1$ and $Z_f(t) = 0$

→ Thus, the set of all tests that detect f is given by

$$Z_f(t) \oplus Z(t) = 1$$

Example 2

 


Let the fault f be x_4 s-a-0. Find all test vectors that detect f

Example 3

Let $f = x_4$ s-a-0.


For test vector 1001 that detects f , simulate without and with fault f

 

Example 3


v/v_f : fault-free/faulty

Fault: G2 s-a-1

 

Fault – Sensitization

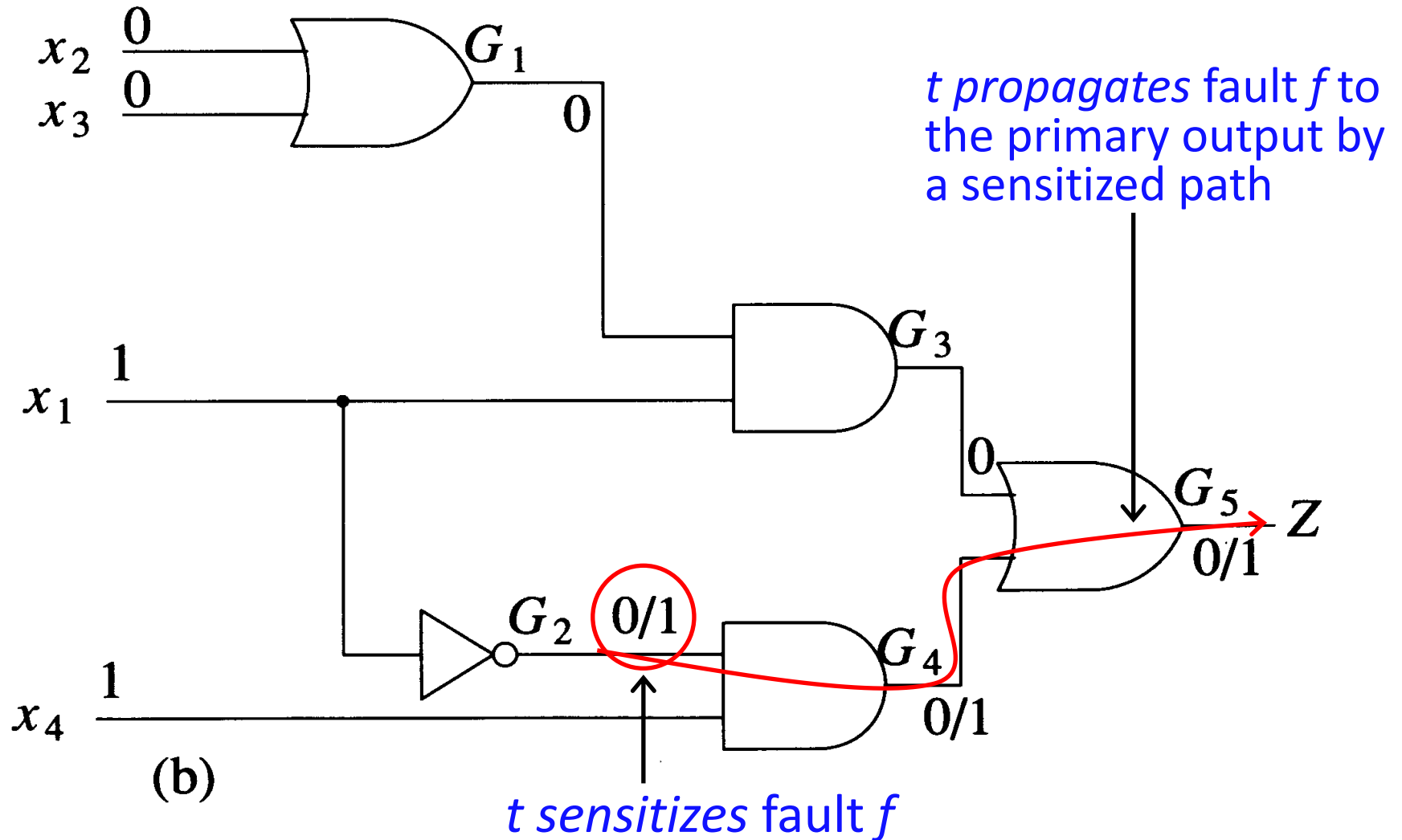$f = G2 \text{ s-a-1}$, Test vector $t = 1 \ 0 \ 0 \ 1$



Fault Sensitization – Terminology

- **Fault Activation:** A test t activates a fault on a line if it generates an error at the site of the fault.
- **Fault Propagation:** A test t propagates the error to a primary output by creating at least one path from fault site to the primary output.
- **Line Sensitization:** A line whose value under the test t changes in the presence of the fault f is said to *be sensitized to the fault f by the test t*
- **Sensitized Path:** A path composed of sensitive lines


Gate Controlling and Enabling Values

→ **Controlling value c** : If at least one input assumes value c , then the gate's output assumes value

$$c \oplus i$$

→ **Enabling value \bar{c}** : If all inputs of a gate have the enabling value, then the gate's output assumes the value $\bar{c} \oplus i$.

Example

 

Control value = _____

Enabling value = _____

NAND: $c=0, i=1$.

Lemma 4.1

Let G be a gate with inversion i and controlling value c , whose output is sensitized to a fault f (by a test t).

1. All inputs of G sensitized to f have the same value (say, a).
2. All inputs of G not sensitized to f (if any) have value \bar{c} .
3. The output of G has value $a \oplus i$.

 


Figure 4.4 NAND gate satisfying Lemma 4.1 ($c=0$, $i=1$)


Faults – Detectability

A fault f is said to be **detectable** if there exists a test t that detects f

Otherwise, f is **undetectable**.


For undetectable fault, no test exists that can simultaneously activate and propagate the fault to the primary output.

Example: Undetectable Fault *a s-a-1*

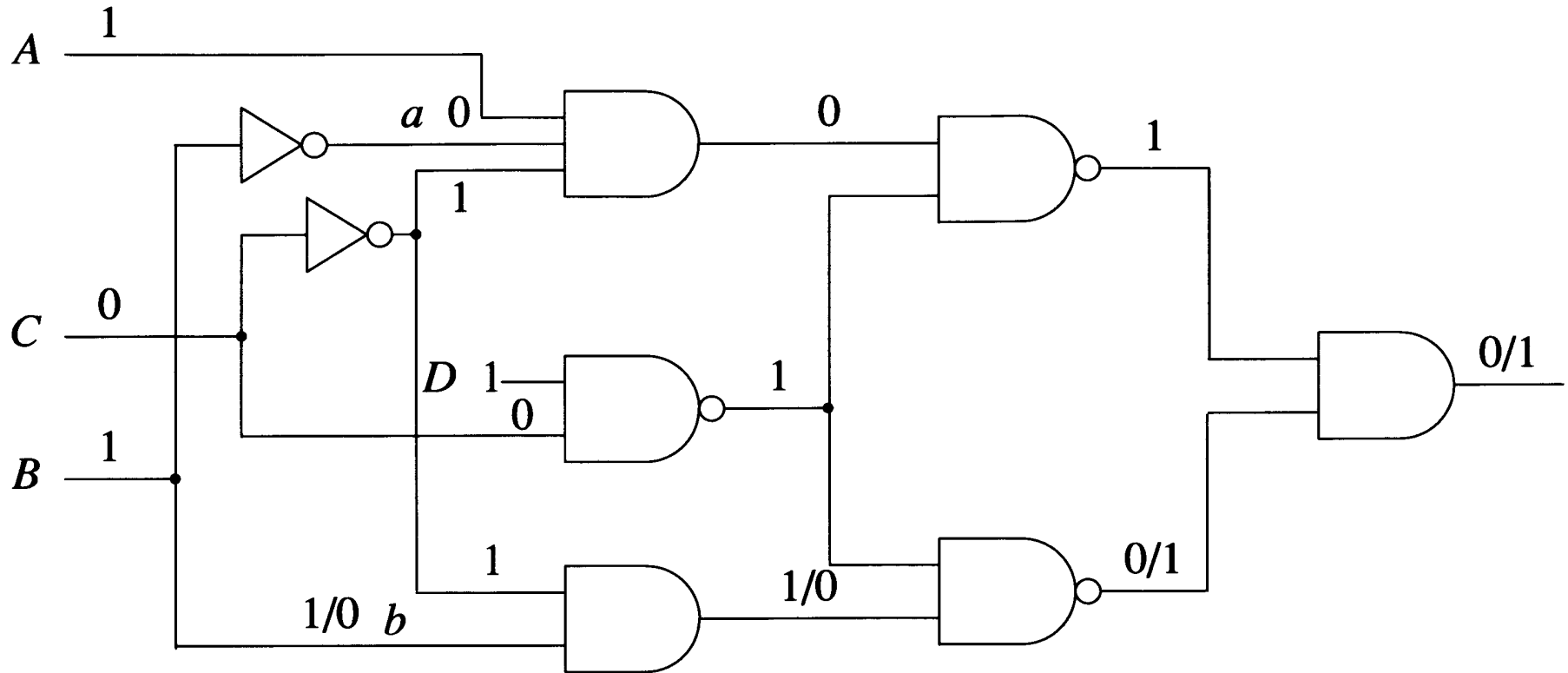


Example: Detectable Fault *bs-a-0*

bs-a-0 is detectable with $t = 1101$

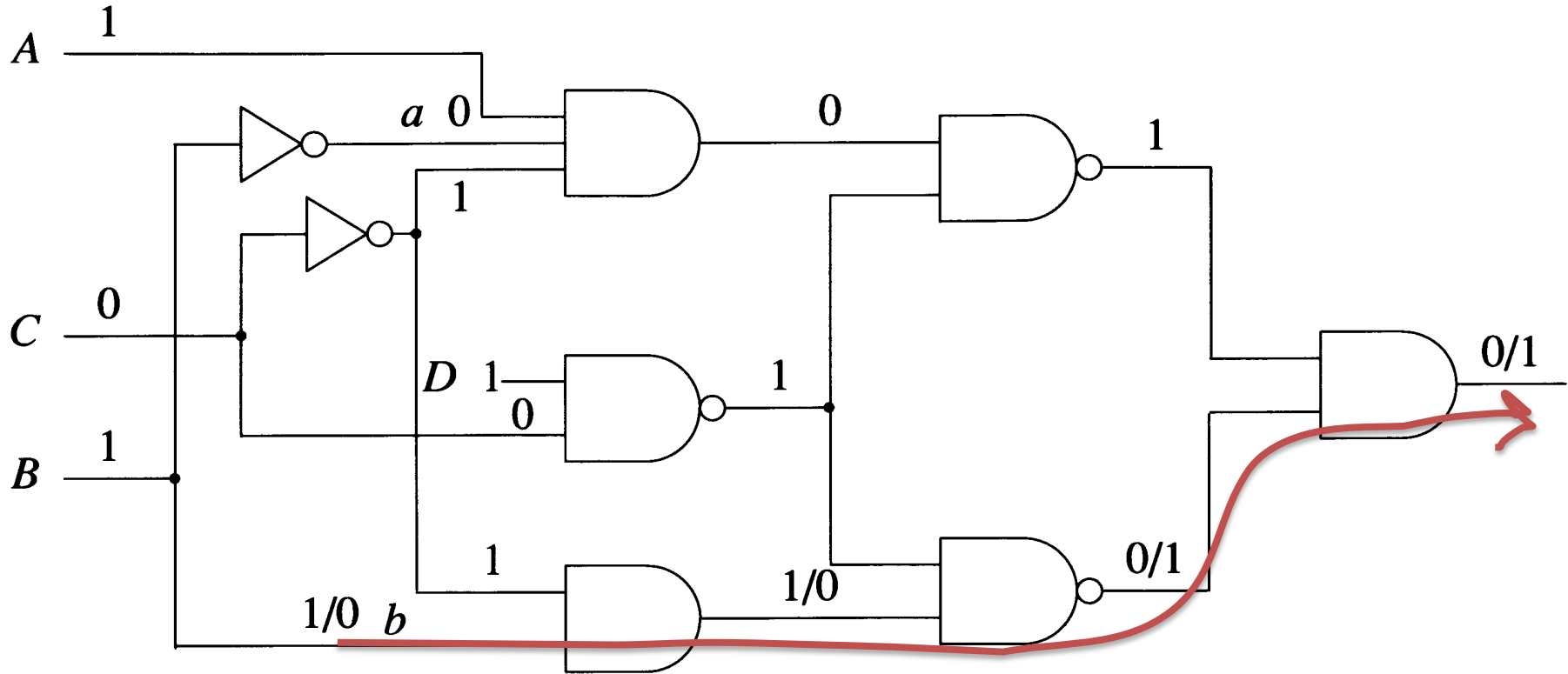


Example: Undetectable Fault

b s-a-0 becomes *undetectable* in the presence of
 a s-a-1 by test $t=1101$

 


Example 2: Undetectable Fault

q s-a-0 is detectable with $t = 111$

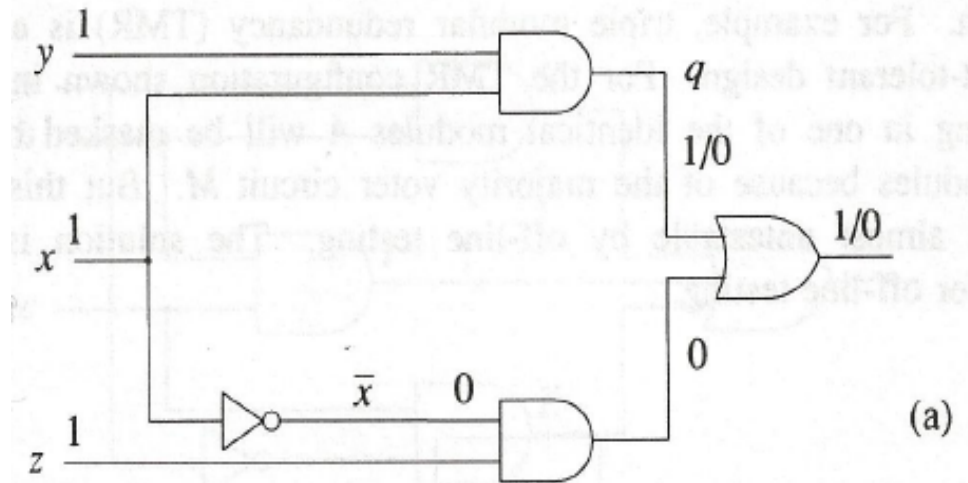

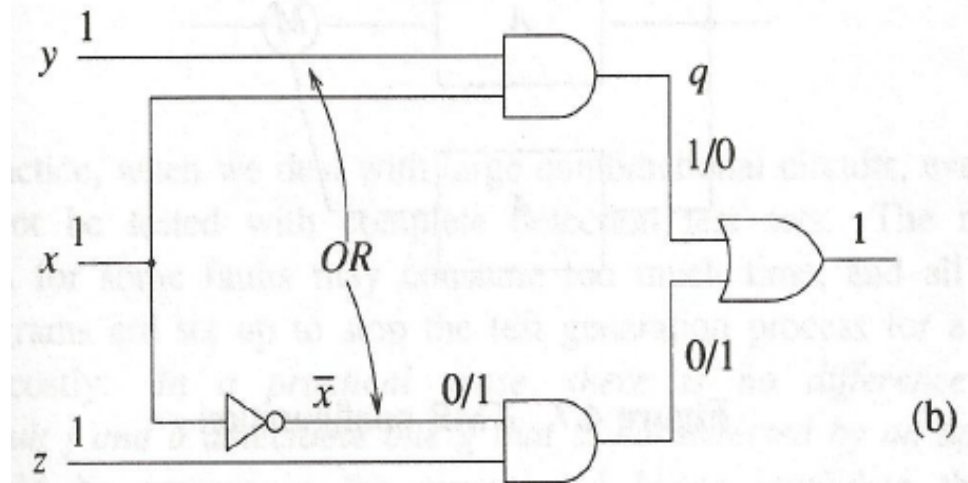
q s-a-0 is undetectable in the presence of OR Bridging fault between y and \bar{x} .



Fault – Redundancy

- A combinational circuit that contains an undetectable stuck fault is said to be **redundant**
- Such circuit can always be reduced by eliminating a gate or a gate input
- A combinational circuit in which all stuck faults are detectable is said to **irredundant**

 Example: Y s-a-0 is undetectable. Gate Y can be dropped.



Fault Interaction

- If f is a detectable fault and g is an undetectable fault, then f may become undetectable in the presence of g . Such a fault f is called a *second-generation redundant fault*.
- Two undetectable single faults f and g may become detectable if simultaneously present in the circuit. In other words, the multiple fault $\{f, g\}$ may be detectable even if its single-fault components are not.

Detecting Redundancy

- To show a line is redundant \Rightarrow to prove that no test exists for the corresponding fault
- Detecting Redundancy Problem \Rightarrow Test Generation Problem
- Test generation problem is an *NP*-complete problem
- Practical test generation algorithms run in polynomial time
- Redundant faults make test generation algorithms exhibit worst-case behavior

Large Combinational Circuits

- Even if the circuit is *irredundant*, we may not have complete test set due to time limitations
- In such a case, the fault (say f) for which no test exists, is no different from an *undetectable fault* (say g)
- Undetectable fault g may be present in the circuit and invalidate the single fault assumption.

Sequential Circuits

- Testing more difficult than combinational circuits
- Need a test sequence
- Response is a function of initial state
 - Let T be a test sequence – a sequence of test vectors.
 - $R(q, T)$ be the response to T with initial state q
 - $R_f(q_f, T)$ be the response for faulty circuit

T Strongly Detects f

→ Definition 4.2: A test sequence T **strongly detects** the fault f

if and only if


the output sequences $R(q, T) \neq R_f(q_f, T)$ for every possible pair of initial states q and q_f

Example

α line a $s-a-1$

β line b $s-a-0$

Test sequence $T=10111$

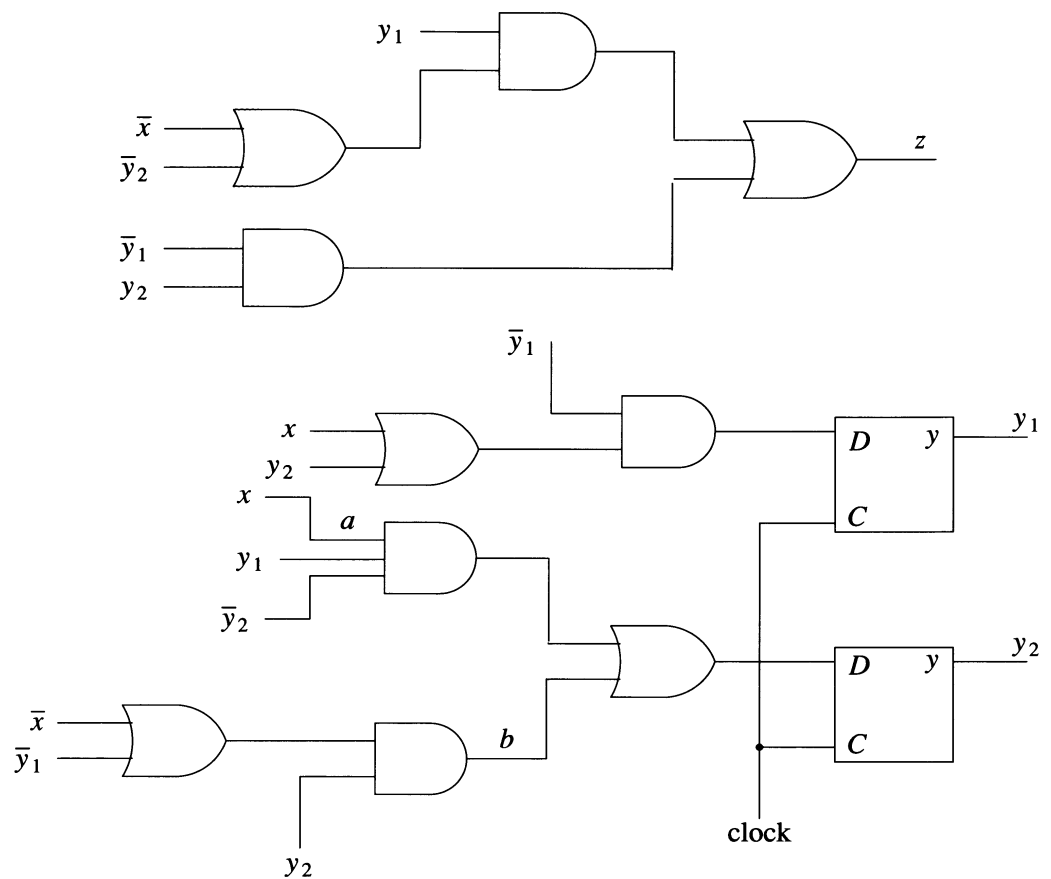

	x		y_1	y_2
	0	1		
A	A,0	D,0	0	0
B	C,1	C,1	0	1
C	B,1	A,0	1	1
D	A,1	B,1	1	0

Initial state	Output sequence		
	Fault-free	α (a $s-a-1$)	β (b $s-a-0$)
A	01011	01010	01101
B	11100	11100	11101
C	00011	00010	01010
D	11001	10010	11010

Figure 4.9 Output sequences as a function of initial state and fault

Example

- T does not strongly detect α
- T strongly detects β

	0	1	y_1	y_2	
<i>A</i>	<i>A</i> ,0	<i>D</i> ,0	0	0	
<i>B</i>	<i>C</i> ,1	<i>C</i> ,1	0	1	: <i>10111</i>
<i>C</i>	<i>B</i> ,1	<i>A</i> ,0	1	1	
<i>D</i>	<i>A</i> ,1	<i>B</i> ,1	1	0	

Initial state	Output sequence		
	Fault-free	α (<i>a s-a-1</i>)	β (<i>b s-a-0</i>)
<i>A</i>	01011	01010	01101
<i>B</i>	11100	11100	11101
<i>C</i>	00011	00010	01010
<i>D</i>	11001	10010	11010

T Detects f

→ Definition 4.3: A test sequence T ***detects*** the fault f

if and only if

for every possible pair of initial states q and q_f the output sequences $R(q, T) \neq R_f(q_f, T)$ for *some* specified vector $t_i \in T$

Testing with Initialization

- Phase I: Initialization sequence T_i such that N and N_f are brought to known states q_i and q_{if}
 - Output responses ignored during initialization
- Phase II: Apply T' (output responses are predictable)
 - t_i is first vector of T' for which an error is observed

Drawback

- Initialization may not be possible for faulty circuit
- Example:

 


Figure 4.10 Example of a fault preventing initialization

4.3 Fault Equivalence and Fault Location

Fault Equivalence – Combinational Circuits


→ **Definition 4.4:** Two faults f and g are said to be **functionally equivalent** iff

$$Z_f(x) = Z_g(x)$$


- A test t is said to **distinguish** between two faults f and g if $Z_f(t) \neq Z_g(t)$
- There exists no test that can distinguish functionally equivalent faults
- Faults are divided into equivalent classes.

Equivalence Fault Collapsing

 - Reduce faults into equivalent classes
- For a NAND gate,
 - All input $s-a-0$ faults and the output $s-a-1$ are functionally equivalent



(a)

 

(b)

$$\bullet : s - a - 1, \quad \circ : s - a - 0$$

Equivalence Fault Collapsing

- In general, for a gate with controlling value c and inversion i ,
 - All input s-a-c faults are *functionally equivalent* to output s-a- $(c \oplus i)$ faults
 - Reduce $2(n+1)$ faults to $n+2$ faults for a n -input NAND gate.

Fault Location

- Goal of testing is to locate the fault besides detecting the fault
- A *complete location test* distinguishes between every pair of distinguishable faults in a circuit
- A fault-free circuit contains *empty fault*, denoted by Φ .
 - Therefore $Z_{\Phi}(x) = Z(x)$
- A fault detection is a particular case of fault location, since a test that detects f distinguishes between f and Φ .

Functional Equivalence Under a Test

→ In practice, test sets are not complete

→ Affect diagnostic resolution

→ **Definition 4.5:** Two f and g are **functionally equivalent under a test set T ,**

iff

$$Z_f(t) = Z_g(t) \text{ for every test } t \in T$$

Note:

Functional equivalence implies functional equivalence under any test set, but not vice versa.

Fault Equivalence – Sequential Circuits

→ **Definition 4.6:** Two f and g are **strongly functionally equivalent** iff their corresponding state tables are equivalent.

→ Impractical

→ **Definition 4.6:** Two f and g are **functionally equivalent** iff for any T' ,

$$R_f(q_{I_f}, T') = Z_g(q_{I_g}, T')$$

4.4 Fault Dominance

Fault Dominance – Combinational Circuits

- Another fault relation to reduce faults to be considered
- **Definition 4.8:** Let T_g be the set of all tests that detect a fault g . We say that a fault f **dominates** the fault g
iff
 f and g are functionally equivalent under T_g .

Fault Dominance

- If f dominates g , then any test t that detects g , *i.e.*, $Z_g(t) \neq Z(t)$, will also detect f (on the same primary inputs) because $Z_f(t) = Z_g(t)$
- Therefore, we can drop f from the fault set



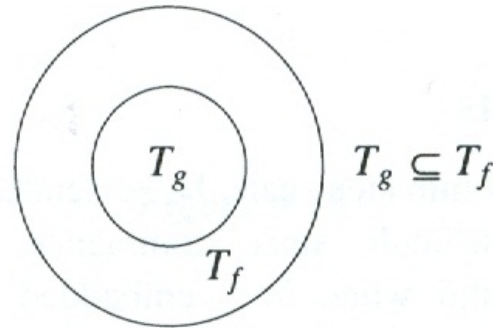


Figure 4.13 The sets T_f and T_g when f dominates g

Example

 

(b)

 

(c)

● : $s - a - 1$, ○ : $s - a - 0$

Fault g : y s-a-1

Fault f : z s-a-0

f dominates g

$$T_g = \{xy = 10\}$$

$$T_f = \{???\}$$

Dominant Fault Collapsing

- In general, for a gate with controlling value c and inversion i ,
 - Output $s-a-(c \oplus i)$ fault dominates input $s-a-\bar{c}$ faults.
- Better to choose a fault model dominated by other models
 - Tests detecting one model also detects other faults models

An Example

- Faults: $f : z_2 \text{ s-a-} 0$, $g : y_1 \text{ s-a-} 1$, test $t = 10$
- t detects both f and g , but they do not dominate each other

 


Figure 4.14

4.5 The Single Stuck-Fault Model

Fault Universe

- For n lines where SSFs can be defined, there are $2n$ stuck faults.
- For fanout-free circuits, the number of faults is $2(G+I)$.
 - G : gate count
 - I : number of primary inputs
- For circuits with fanout, the estimate is $2Gf$
 - f : average fanout count

Checking Functional Equivalence is Hard!

- In general, to determine whether two arbitrary faults are functionally equivalent is NP-complete
- Example: Are c s-a-1 and d s-a-1 functionally equivalent?

 


Figure 4.17

Structural Equivalence

- In a circuit N_f the fault f creates a set of lines with constant values.
- By removing all these lines (except POs), we obtain $S(N_f)$
- Two faults f and g are structurally equivalent if $S(N_f)$ and $S(N_g)$ are identical
- All structurally equivalent faults are functionally equivalent
- But not all functionally equivalent faults are structurally equivalent

Example: Structural Equivalence

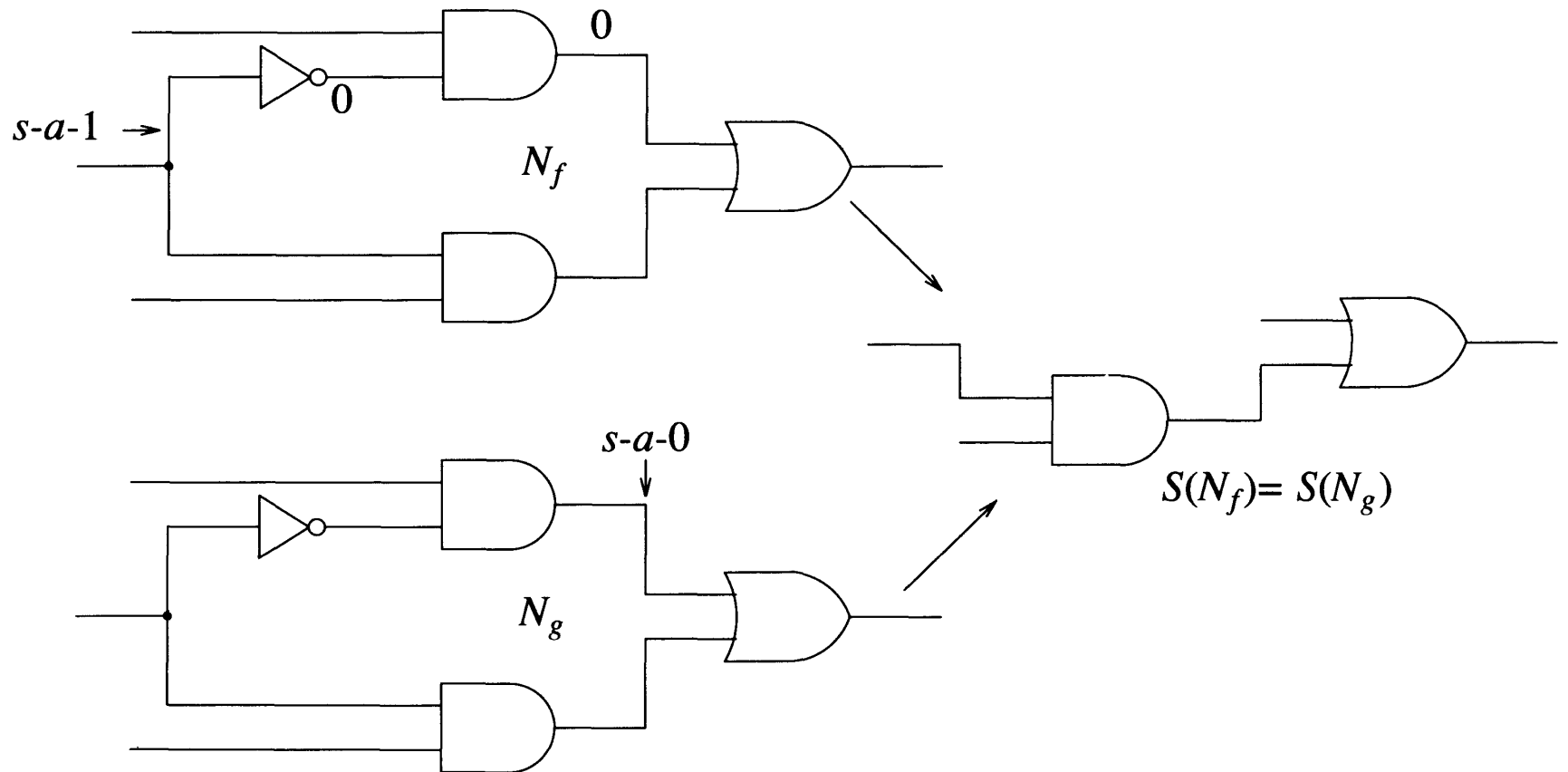


Figure 4.18 Illustration for structural fault equivalence

Structurally Equivalent Fault Collapsing

- For a line with fanout of 1, the faults at its sources are structurally eq. to those at its destination.
- For a gate, input $s-a-c$ is structurally eq. to output $s-a-(c \oplus i)$.
- For each eq. class, retain only one fault.


 


Figure 4.19 Example of structural equivalence fault collapsing

Structurally Equivalent Faults – Example

 

g s-a-1 and i s-a-0 ?

On average, about 50% SSFs can be reduced !

Fault Reduction by Dominance Relation

- **Theorem 4.1:** In a **fanout-free** combinational circuit C , any test set that detects all SSFs on the primary inputs of C detects all SSFs in C .
- **Theorem 4.2:** In a combinational circuit C any test set that detects all SSFs on the primary inputs and the fanout branches of C detects all SSFs in C .
 - These faults can be further reduced by structural equivalence and dominance relations.

Example

- How many faults after fault collapsing?
- Answer: 10 (verify this)

 


Figure 4.21

Stem and Fanout Faults – Example 1

- In general neither functional equivalence nor dominance relations exists between stem and fanout faults
- Stem fault j *s-a-0* is detected but k *s-a-0* and m *s-a-0* are not

 


Figure 4.22

Stem and Fanout Faults – Example 2

→ Fanout faults x_1 s-a-0 and x_2 s-a-0 are detectable but stem fault x s-a-0 is not

 


Figure 4.23

4.6 The Multiple Stuck-Fault Model

Multiple Stuck Fault (MSF) Model

- Several lines can be stuck simultaneously.
 - Straightforward extension of SSF
- For a n line circuit, there are
 - $2n$ SSFs, but
 - $3^n - 1$ possible MSFs
 - $\sum_{i=1}^k \binom{n}{i} 2^i$ possible MSFs for multiplicity k .
 - Too large a number to handle.
- A MSF F can be viewed as $\{f_1, f_2, \dots, f_k\}$.
- Why do we need to consider MSF?
 - Because of masking relation between faults

Functional Masking

→ **Definition 4.9:** Let T_g be the set of *all* tests that detect g . We say that f **functionally masks** g iff the multiple fault $\{f, g\}$ is not detected by any test in T_g

→ Example: a *s-a-1* masks c *s-a-0*

→ 011 only vector that detects c *s-a-0*

→ $\{c$ *s-a-0*, a *s-a-1* $\}$ is not detectable by 011

 


Figure 4.24

Masking under a Test Set

→ **Definition 4.10:** Let $T_g' \subseteq T$ be the set of all tests in T that detect a fault g . We say that a fault f **masks** the fault g *under a test set* T iff the multiple fault $\{f, g\}$ is not detected by any test in T_g'

→ Functional masking → masking under a test set

→
$$T'_g \subseteq T_g$$

Problem

→ If f masks g , then fault $\{f, g\}$ is not detected by tests that detect g alone. But can there be other tests to detect $\{f, g\}$?

$\{c\ s-a-0, a\ s-a-1\}$

 


Figure 4.24

Problem – Detection of Multiple Faults

→ Given a complete test set T that detects all single faults, can there exist a multiple fault $F = \{f_1, f_2, \dots, f_k\}$ such that F is not detected by T ?

Example

→ $T = \{1111, 0111, 1110, 1001, 1010, 0101\}$

→ $f = B s-a-1$ and $g = C s-a-1$

→ 1001 is the only vector that detects f and g SSFs, but...

 


Figure 4.25

Example

→ 1001 cannot detect $\{f, g\}$

→ f masks g , and g masks f – **circular masking**

 


Figure 4.25

What % of MSFs can escape detection by a complete SSF test set (T)?

- In an irredundant 2-level circuit, T also detects all MSFs
- In a fanout-free circuit, any T detects all double and triple faults, and there exists a T for SSFs that detects all MSFs
- In an internal fanout free circuit, any T detects at least 98% of MSFs with multiplicity $k < 6$
- A test set that detects all MSFs defined on all primary inputs without fanout and all fanout branches of a circuit C detects all multiple faults in C .

MSFs or Not?

- A test set T for SSFs also detects most MSFs.
 - Typically focus on MSFs not detectable by T .
- Probability of MSFs is low.
 - Modern semi-manufacturing is highly reliable
- A SSF is **guaranteed to be detected** (GTBD) if it can be detected unconditionally.
 - Any MSF that includes a GTBD SSF is also GTBD.

Summary

- Logic faults can represent various physical faults
- Fault detection
 - Find a test that causes deviation in output responses
 - Undetectable faults → redundancy
- Fault collapsing
 - Fault equivalence & dominance
- Single stuck-fault model
 - Possible to find a complete test set
- Multiple fault model
 - A SSF detection test set can find many MSFs

Backup

Corollary 4.1

Let j be a line sensitized to the fault l *s-a-v* (by a test t), and let p be the inversion parity of a sensitized path between l and j .

1. The value of j in t is $v \oplus p$.
2. If there are several sensitized paths between l and j , then all of them have the same inversion parity.

Redundancy in Circuits

→ Redundancy can be by design i.e., intentional

Fault tolerant design

 


Figure 4.8

Hazard-free design

 


Figure 4.8