

CIS 4930 Digital System Testing

Fault Simulation

Dr Hao Zheng
Comp. Sci & Eng.
U of South Florida

Overview

- Fault simulation applications
- Fault simulation techniques
 - Serial
 - Parallel
 - Deductive
 - Concurrent
- **tentative**
 - Fault simulation for combinational circuits
 - Fault sampling
 - Statistical fault analysis

5.1 Applications

Fault Simulation


- Simulation of a circuit in the presence of faults
- Used to
 - Evaluate a test T wrt fault coverage.
 - Generate tests T to achieve certain fault coverage.
 - Construct fault dictionary
 - Analyze circuit operation in the presence of faults

1 – Evaluate a Test T

- Usual metric: fault coverage
- Fault coverage relevant to the fault model
 - 100% FC does not mean 100% defects are covered if the fault model is limited.
 - Other defects may still exist if not considered in a fault model.
 - Lower bound on **defect coverage**
- Defect coverage d = probability that T detect any physical fault.
 - Has a big impact on product quality.

Yield and Defect Level

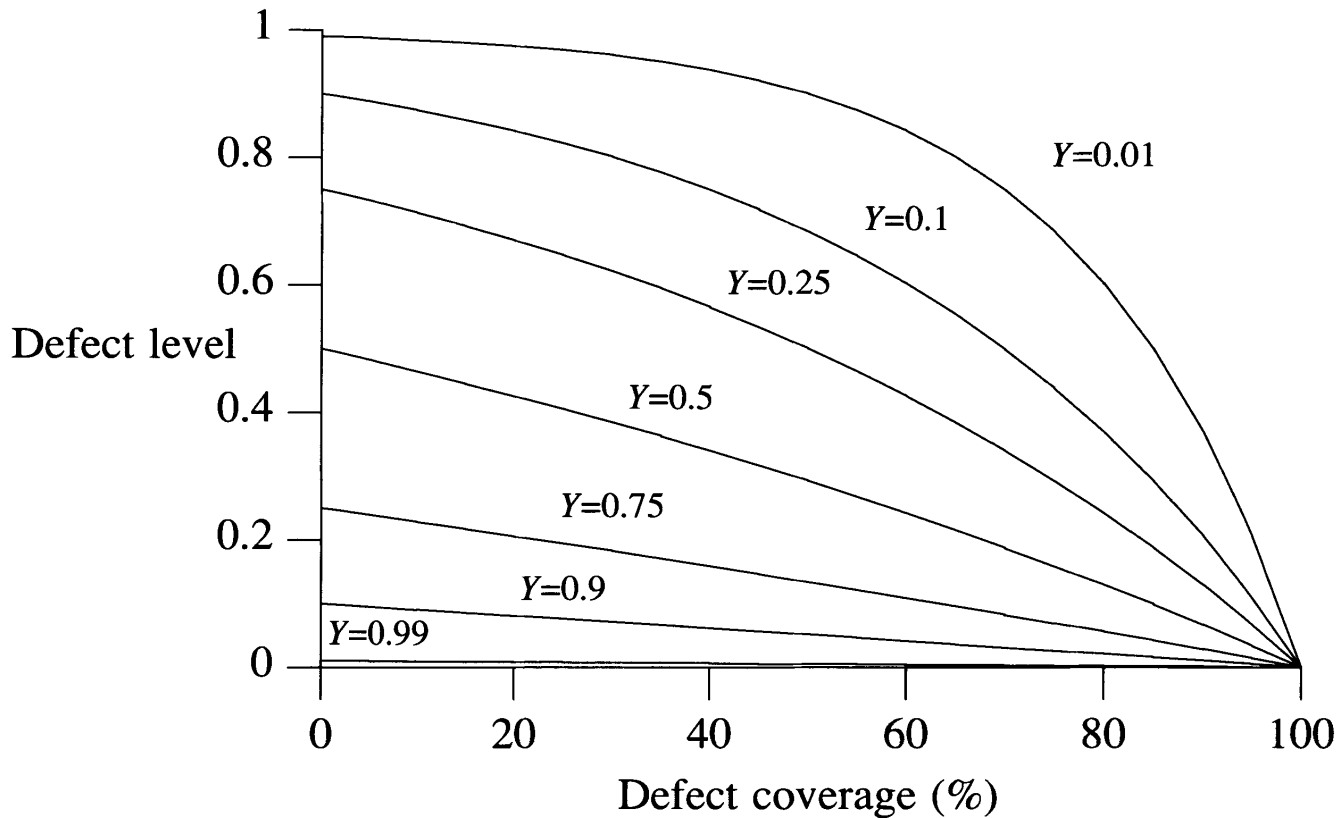- **Defect level (DL)** = prob. of shipping a defective product
- **Yield (Y)** = prob. that manufactured circuit is defect free



$$DL = 1 - Y^{1-d}$$

2 – Test Evaluation

→ Enhance T until adequate fault coverage is satisfactory


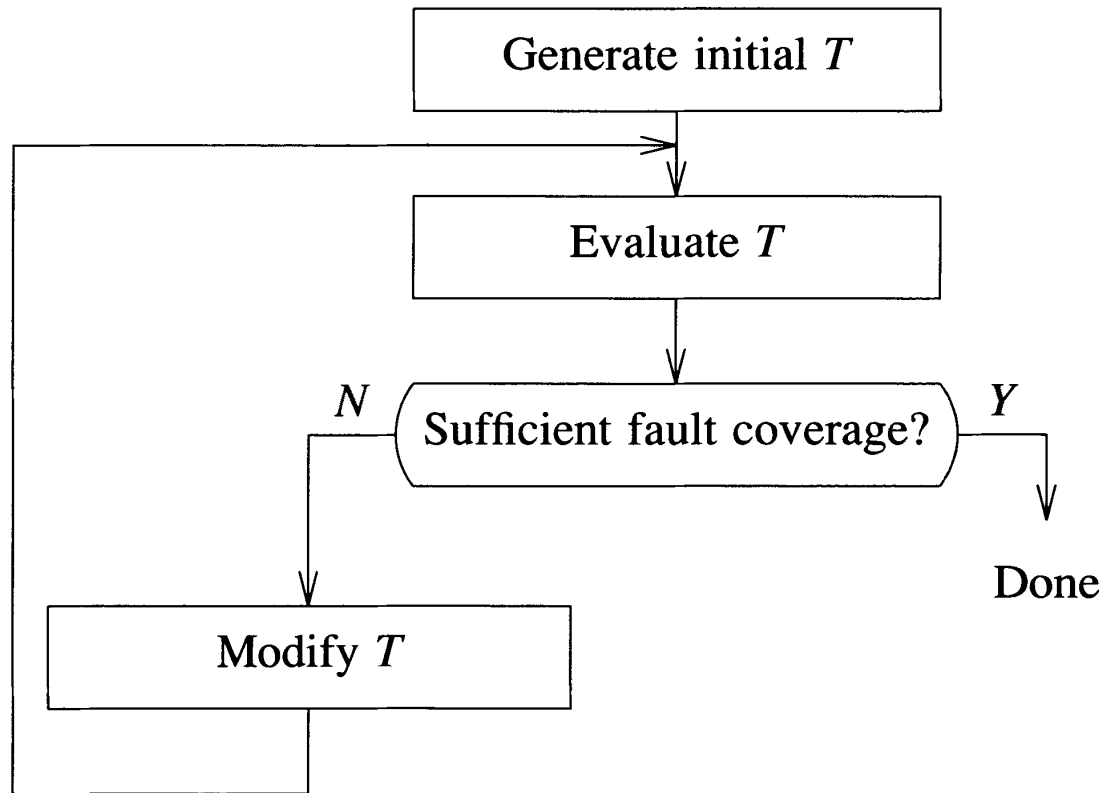


Figure 5.2 General use of fault simulation in test generation

Test Generation

Target fault oriented approach

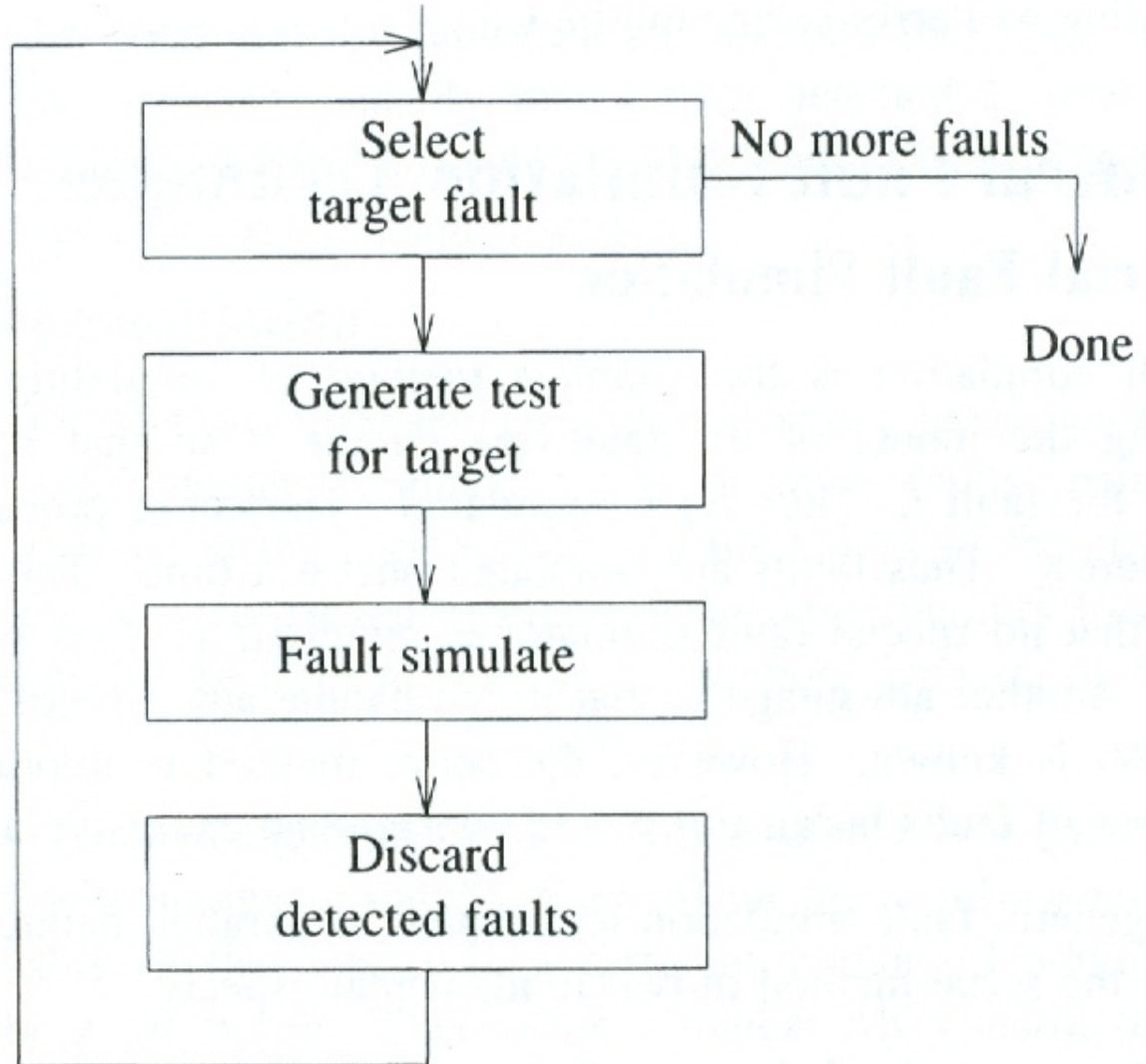

3 – Construct Fault Dictionaries

→ Fault Dictionary – stores output response (R_f) or *signature* $S(R_f)$ to T of every faulty circuit N_f

	f1	f2	..	fn
T1	0	1	..	1
T2	1	0	..	1
:	:	:		:
Tm	1	1	..	0

4 – Circuit Analysis

- Analyze circuit operations in presence of faults
- Some effects introduced by faults may not present in fault-free circuit:
 - Races and/or hazards
 - Oscillation and/or deadlock
 - Inhibit proper initialization of seq. circuit
 - Transform combinational to sequential
 - Transform synchronous to asynchronous

5.2 Fault Simulation Techniques

General Fault Simulation Techniques

- Serial Fault Simulation
- Parallel Fault Simulation
- Deductive Fault Simulation
- Concurrent Fault Simulation

Serial Fault Simulation

- Simulate faults one at a time
- Given a fault f , do the following:
 - Transform N to N_f
 - Simulate N_f
- Repeat for other faults under consideration.
- **Advantage**
 - No need for a special fault simulator
- **Disadvantage**
 - Impractical for large number of faults

Other Three Techniques

- Common characteristics:
 - Do not change the circuit model
 - Can simultaneously simulate a *set of faults(!)*
 - Simultaneously simulate *good* and *bad* circuits
- **One-Pass** – If all faults are simulated simultaneously
- **Multi-Pass** – For large set of faults, need multiple simulation runs

Tasks in Fault Simulation

- **Fault specification:** define set of modeled faults and perform fault collapsing
- **Fault insertion:** select a fault subset and create data structures to indicate fault presence.
- **Fault effect generation:** Say line i has $f s-a-1$ then whenever value 0 propagates on line i , then simulator changes it to 1
- **Fault effect propagation:** Propagate v/v_f to primary output for fault detection
- **Fault discarding:** Inverse of fault insertion
 - Discard a fault if it is detected for k times.

Parallel Fault Simulation

- Simultaneously simulate the good circuit and W copies of faulty circuits
- Set F of faults needs $\lceil F/W \rceil$ number of passes
- Values of the same signal in different circuits are packed into one memory location (a word or multi-words).

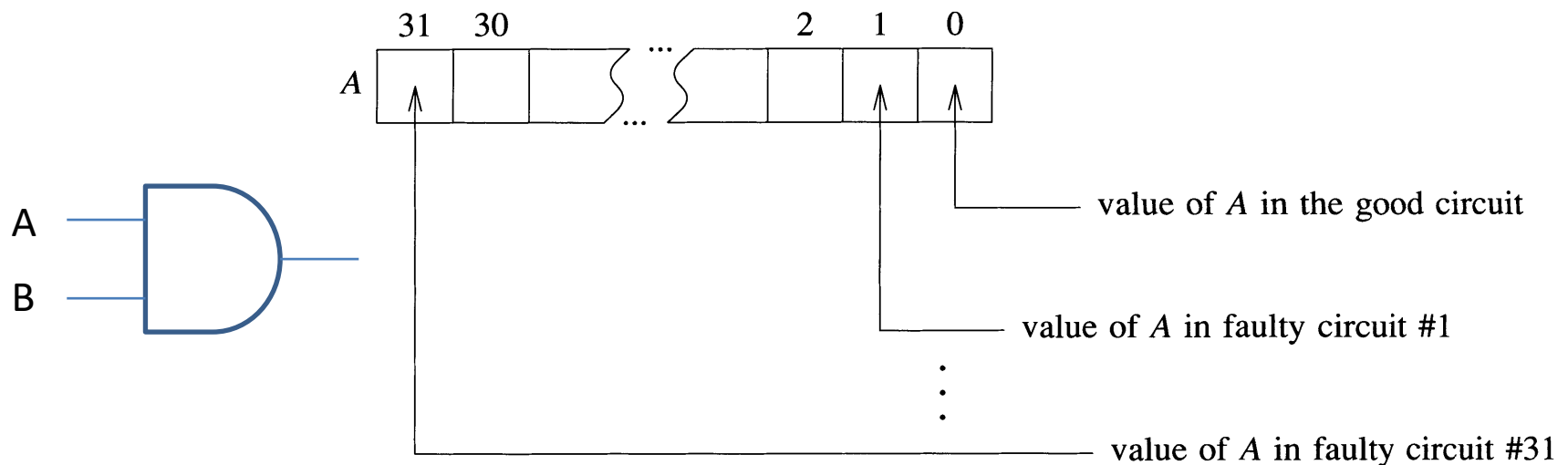


Figure 5.4 Value representation in parallel simulation

Function Evaluation

- Words for A and B are bitwise ANDed (for eg.) for logic AND.
- Similar for other Boolean operations.
- Sequential circuit: For eg., JK FF

$$Q^+ = J\bar{Q} + \bar{K}Q$$

$$Q = clk \uparrow ? Q^+ : Q$$

The above expression is a Boolean expression consisting of AND, OR, and NOT


Bit Value Computation

- Let v_i be the value on line i in the faulty circuit N_f where f is the fault j s-a-c
- Then,

$$v_i' = v_i \overline{\delta_{ij}} + c \delta_{ij}$$


$$\text{where } \delta_{ij} = \begin{cases} 0 & i \neq j \\ 1 & i = j \end{cases}$$

Fault insertion for one fault

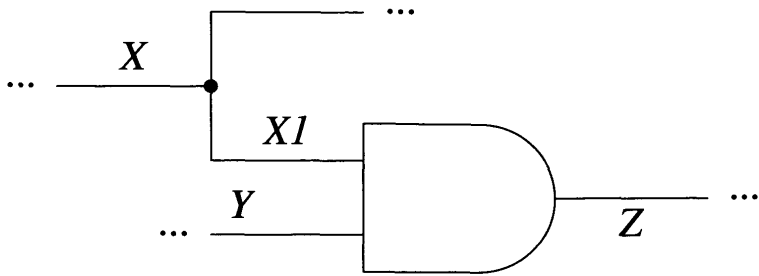


$$Z = X_1 \cdot Y$$

$$Z' = Z\overline{I_Z} + S_Z I_Z$$

 

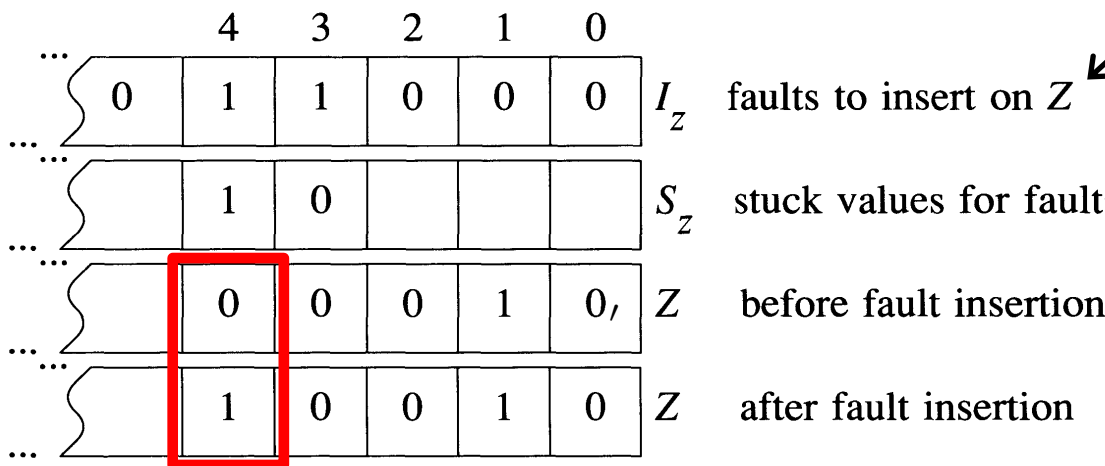To discard a fault simply make the it's mask bit = 0



Mask

Stuck Values

Parallel FS - Limitations

- Parallel simulation is limited for functional level modeling
 - For example if we have to examine for a word value, we need to extract the bits and then re-pack
- Impractical for multi-valued logic
- Event on one bit position results in entire word evaluation => wasted computation
- Cannot take advantage of fault dropping
 - Even if all but one faults are dropped, we still evaluate W copies!

Deductive Fault Simulation

- Simulates good circuit and deduces the behavior of *all* faulty circuits (limited by memory)
- Maintains **Fault List**, L_i for each signal line i .
- L_i = List of all faults f that cause the values on i in N and N_f to be different at the current simulation time
- Difference with Parallel Simulation:

F	9	8	7	6	5	4	3	2	1	0	
i	1		...		1	1	0	1	1	1	1

$$L_i = \{4,7\}$$

Figure 5.8 Fault-effects representation in parallel and deductive fault simulation

How Deductive Simulation Works

→ Given

- Fault-free input values, and
- Fault lists on inputs of an element

→ Compute:

- Fault-free output
- Output fault list (i.e., fault list propagation)

Two Valued Deductive Simulation


→ Any fault that causes A or $B = 0$ will lead to $Z = 0$

→ Therefore:

$$L_Z = L_A \cup L_B \cup \{Z \text{ s-a-} 0\}$$

$$L_A = \{A \text{ s-a-} 0\}$$

$$L_B = \{B \text{ s-a-} 0\}$$

 


Use Ax to denote $A \text{ s-a-} x$

Two Valued Deductive Simulation

- Any fault that causes $A = 1$ without changing B , will cause an error on Z
- Note -- A fault that propagates on both A and B will not affect Z
- Therefore:
 
$$\begin{aligned}L_Z &= (L_A \cap L_B) \cup \{Z_1\} \\ &= (L_A - L_B) \cup \{Z_1\}\end{aligned}$$



General Formulae

→ Let I = set of inputs of gate Z

C = set of inputs with control value c

Then Fault List L_Z on Z is given by

if $C = \Phi$ then

$$L_Z = \left\{ \bigcup_{j \in I} L_j \right\} \cup \{Z \text{ s-a-} (c \oplus i)\}$$

else

$$L_Z = \left\{ \bigcap_{j \in C} L_j \right\} - \left\{ \bigcup_{j \in I-C} L_j \right\} \cup \{Z \text{ s-a-} (\bar{c} \oplus i)\}$$

Example

After Fault Collapsing, the fault set is

$$F = \{ a_0, a_1, b_1, c_0, c_1, d_1, e_0, g_0, h_0, h_1 \}$$

Assume $T = 00110$ to $abcde$

 


Figure 5.10

$F = \{ a_0, a_1, b_1, c_0, c_1, d_1, e_0, g_0, h_0, h_1 \}$

$L_a = \{a_1\}, L_b = \{b_1\}, L_c = \{c_0\}, L_d = \emptyset, L_e = \emptyset$

 


Figure 5.10

$$F = \{ a_0, a_1, b_1, c_0, c_1, d_1, e_0, g_0, h_0, h_1 \}$$

$$L_a = \{ a_1 \}, L_b = \{ b_1 \}, L_c = \{ c_0 \}, L_d = \emptyset, L_e = \emptyset$$

$$L_f = L_a \cap L_b = \emptyset,$$

 


Figure 5.10

$$F = \{ a_0, a_1, b_1, c_0, c_1, d_1, e_0, g_0, h_0, h_1 \}$$

$$L_a = \{ a_1 \}, L_b = \{ b_1 \}, L_c = \{ c_0 \}, L_d = \emptyset, L_e = \emptyset$$

$$L_f = L_a \cap L_b = \emptyset, L_g = L_c \cup \{ g_0 \} = \{ c_0, g_0 \}$$

$$L_h = L_c \cup \{ h_0 \} = \{ c_0, h_0 \}$$

 


Figure 5.10

$$F = \{ a_0, a_1, b_1, c_0, c_1, d_1, e_0, g_0, h_0, h_1 \}$$

$$L_a = \{ a_1 \}, \quad L_b = \{ b_1 \}, \quad L_c = \{ c_0 \}, \quad L_d = \emptyset, \quad L_e = \emptyset$$

$$L_f = L_a \cap L_b = \emptyset, \quad L_g = L_c \cup \{ g_0 \} = \{ c_0, g_0 \}$$

$$L_h = L_c \cup \{ h_0 \} = \{ c_0, h_0 \}, \quad L_j = L_g \cup L_f = \{ c_0, g_0 \}$$

$$L_i = L_d \cup L_h = \{ c_0, h_0 \} \quad L_k = L_i - L_e = \{ c_0, h_0 \}$$

 


Figure 5.10

$$F = \{ a_0, a_1, b_1, c_0, c_1, d_1, e_0, g_0, h_0, h_1 \}$$

$$L_a = \{ a_1 \} \quad L_b = \{ b_1 \} \quad L_c = \{ c_0 \} \quad L_d = \emptyset \quad L_e = \emptyset$$

$$L_f = L_a \cap L_b = \emptyset \quad L_g = L_c \cup \{ g_0 \} = \{ c_0, g_0 \}$$

$$L_h = L_c \cup \{ h_0 \} = \{ c_0, h_0 \}. \quad L_j = L_g - L_f = \{ c_0, g_0 \}$$

$$L_i = L_d \cup L_h = \{ c_0, h_0 \} \quad L_k = L_i - L_e = \{ c_0, h_0 \}$$

$$L_m = L_k - L_j = \{ h_0 \}$$

 


Figure 5.10

Now assume that next test vector is 11110. Redo the example.

$L_a =$ $L_b =$ $L_c =$ $L_d =$ $L_e =$


$L_f =$ $L_g =$

$L_h =$

$L_j =$ $L_i =$

$L_k =$ $L_m =$

 $F = \{ a_0, a_1, b_1, c_0, c_1, d_1, e_0, g_0, h_0, h_1 \}$



Solution:

$$L_a = \{a_0\} \quad L_b = \emptyset$$

$$L_c = \{c_0\} \quad L_d = \emptyset \quad L_e = \emptyset$$

$$L_f = L_a \cup L_b = \{a_0\}$$

$$L_g = L_c \cup \{g_0\} = \{c_0, g_0\}$$

$$L_h = L_c \cup \{h_0\} = \{c_0, h_0\}$$


$$L_j = L_f \cap L_g = \emptyset$$

$$L_i = L_d \cup L_h = \{c_0, h_0\}$$

$$L_k = L_i - L_e = \{c_0, h_0\}$$

$$L_m = L_k - L_j = \{c_0, h_0\}$$

Fault c_0 is detected!

 

DS - Limitations

- Compatible only in part with functional level modeling
 - Applicable only to models with Boolean eqns.
- Limited to two or three logic values
- Cannot handle timing models
- Fault propagation mechanism cannot take full advantage of the concept of activity-directed simulation

Concurrent Fault Simulation

- Observation – Most of the time, most values in most fault circuits agree with those in the good circuit.
- Concurrent Method
 - simulates the good circuit N
 - For every faulty circuit N_f *simulate only those elements that differ with corresponding ones in N*
 - The differences of an element x in N is stored as a **concurrent fault list** (CL_x)

Concurrent List Example


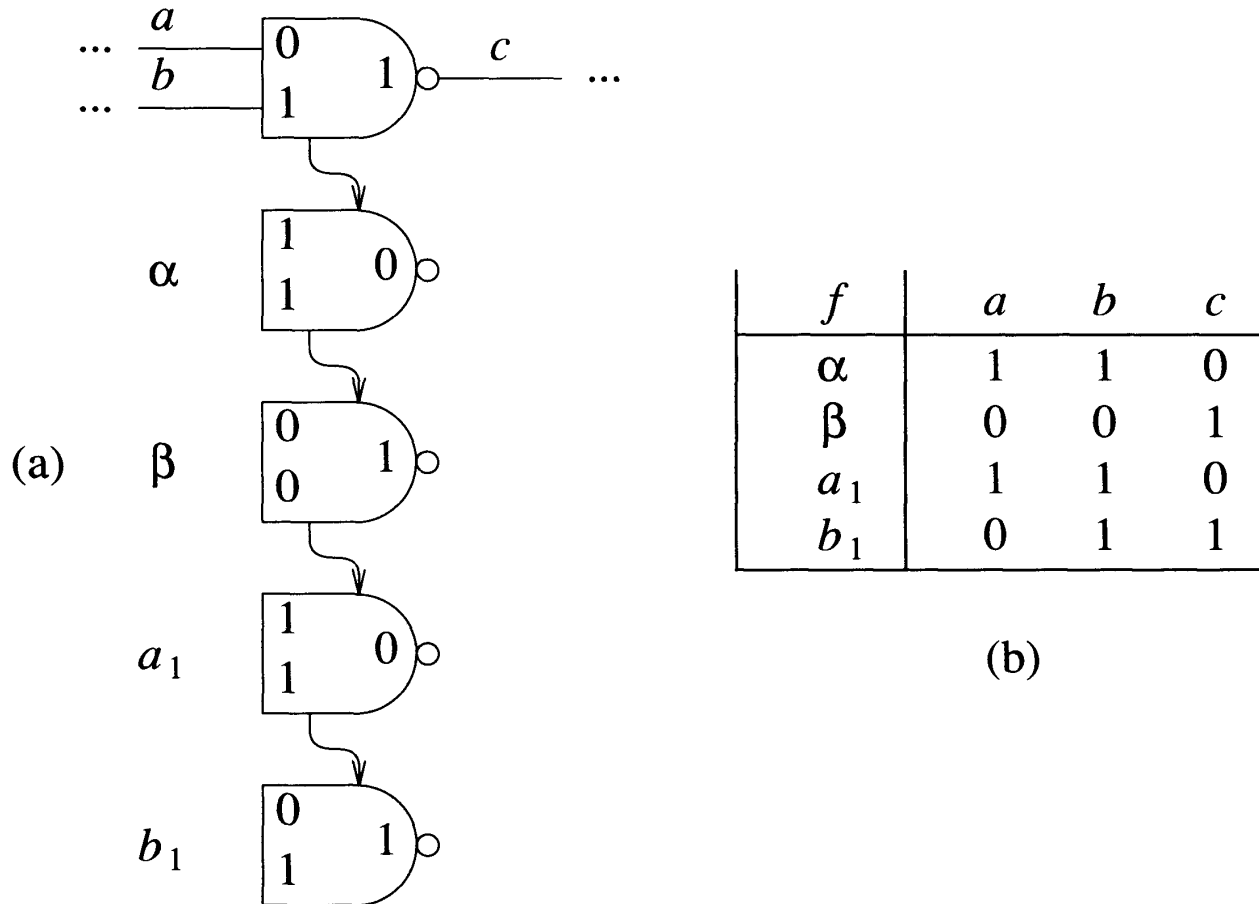


Figure 5.15 Concurrent fault list for gate c (a) Pictorial representation (b) Tabular representation

Two Cases of Differences

 

Let x_f be replica of x in N_f

V_{x_f} and V_x be <inputs, output>

Case 1: $V_{x_f} \neq V_x$


This happens when fault effect of f propagates to x

Case 2: $V_{x_f} = V_x$

This happens when f is a local fault (i.e., input/output fault)

Note: Even if the V_x and V_{x_f} are equal, the elements are different because of the local fault.


Visible Faults

 

A fault is **visible** on line i when the values of i in N and N_f are different.



A deductive fault list includes all visible faults, which is subset of the concurrent fault list.

CFS - Example

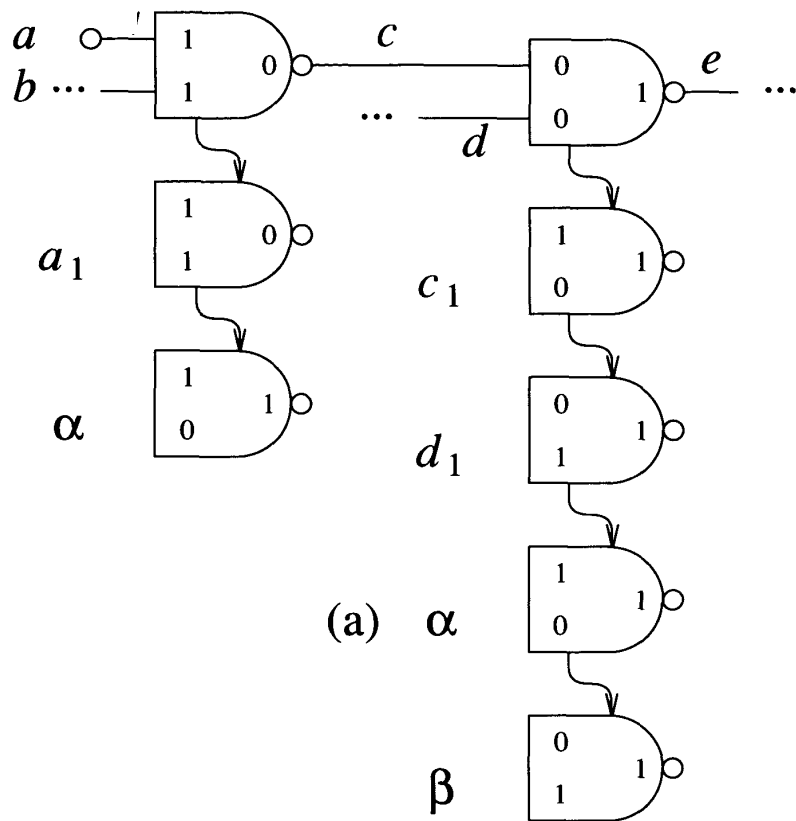


What are those faults in the initial state?


CFS - Example

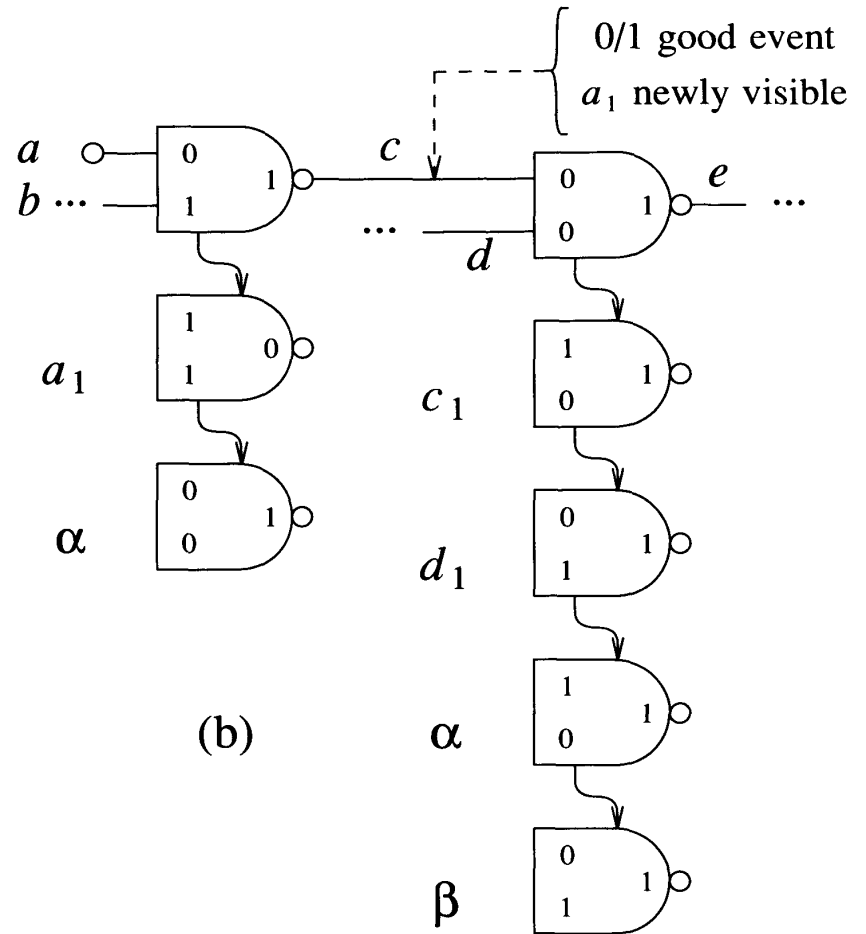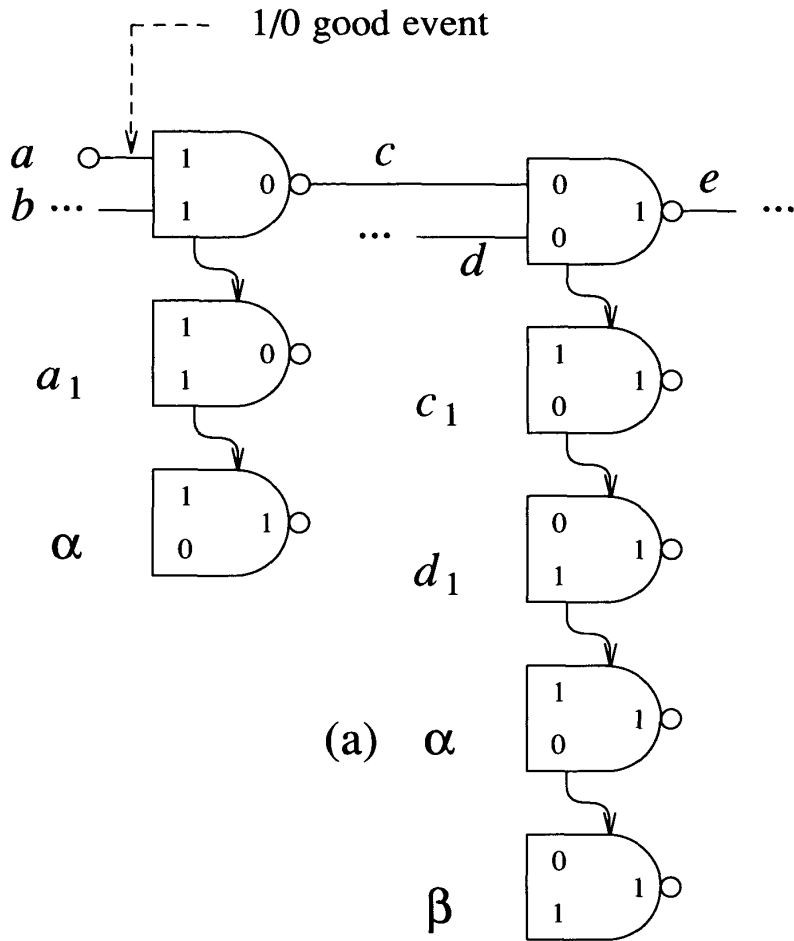

CFS Example – Contd.

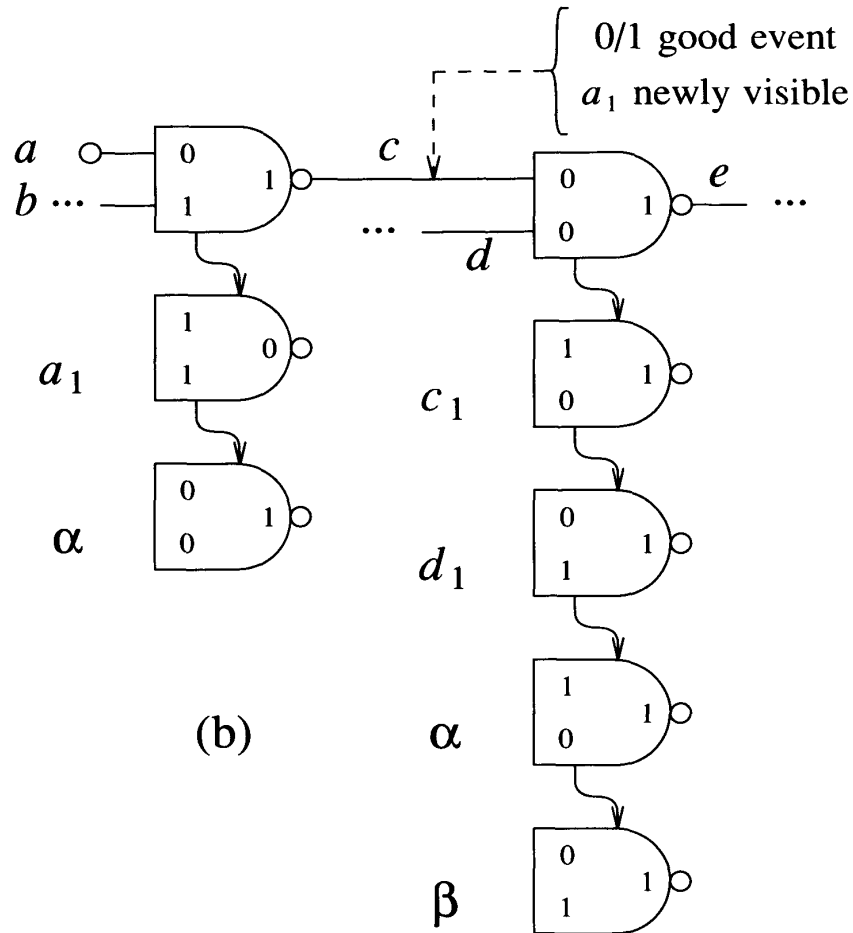

(b)

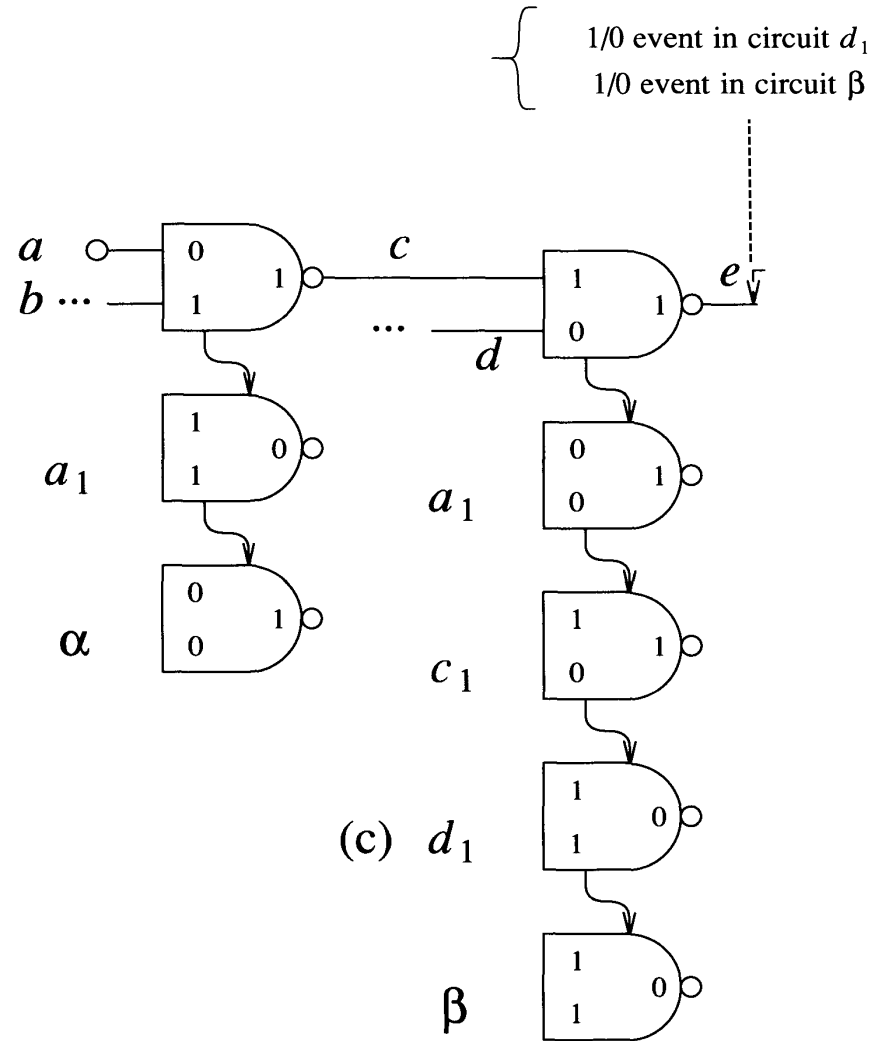

(c)

Concurrent Simulation

- Individually evaluates elements in both good and faulty circuits
- A line i may change even if i is stable in good circuit (see gate d_1 in previous example)
- A line i in the good circuit and some faulty circuits may also have simultaneous but different events

 


Figure 5.17

Composed Event

- For a given input event on A, we compute the outputs in all copies of A in the fault list
- Let the output list be $L = \langle (f_0, v'_{f0}), (f_1, v'_{f1}), \dots (f_n, v'_{fn}) \rangle$
- Composed Event:
 - A set of simultaneous events occurring on a line
 - Represented as (i, L)

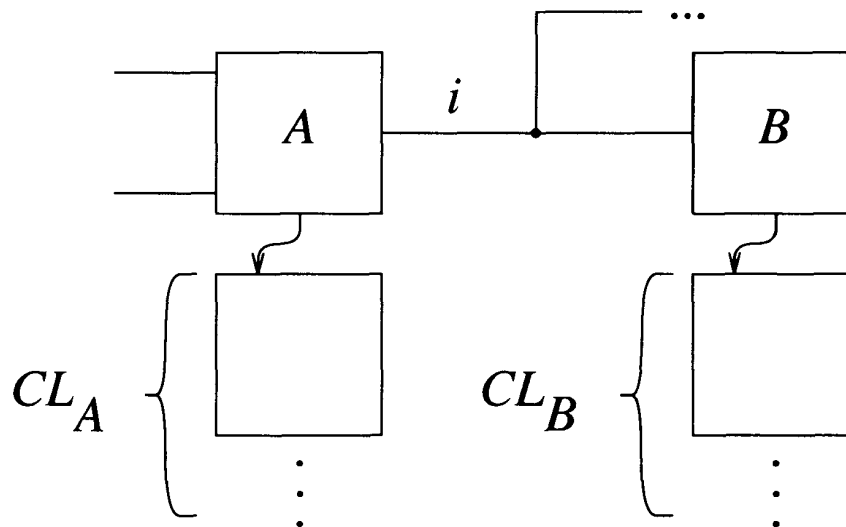


Figure 5.18

Processing of a composed event (i , L) at element A


$NV = \emptyset$

```
if  $i$  changes in the good circuit then  
  begin  
    set  $i$  to  $v'$  in the good circuit  
    for every  $f \in CL_A$   
      begin  
        if  $f \in L$  then  
          begin  
            set  $i$  to  $v_f'$  in circuit  $f$   
            if  $V_{A_f} = V_A$  then delete  $f$  from  $CL_A$   
          end  
        else /* no event in circuit  $f$  */  
          if  $v_f = v$  then add newly visible fault  $f$  to  $NV$   
          else if  $V_{A_f} = V_A$  then delete  $f$  from  $CL_A$   
        end  
      end  
    end  
  else /* no good event for  $i$  */  
    for every  $f \in L$   
      begin  
        set  $i$  to  $v_f'$  in circuit  $f$   
        if  $V_{A_f} = V_A$  then delete  $f$  from  $CL_A$   
      end  
    end
```

NV : newly visible faults

Processing of element $B_f \in CL_B$

→ After updating the CL_A of source element A , we need to update values and CL_B of every element B on the fanout list of i and evaluate activated elements

 

Case 1: $f \in CL_B, f \notin L, f \notin NV$

		$f \in CL_B$		
	—	4	5	1
3	—	—	—	2
		$f \in NV$		$f \in L$


Remark: B_f exists in CL_B and no independent event on i occurs in N_f

Action

If good event exists and can propagate in N_f then activate B_f

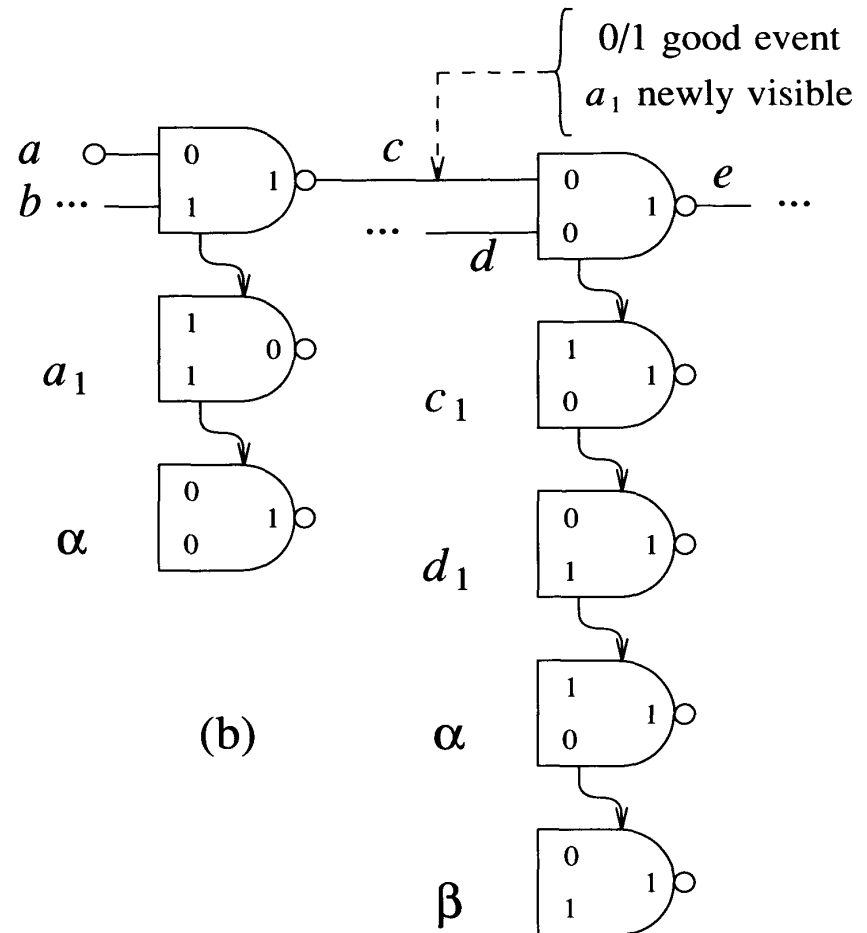Example:

Change c 0/1 propagates in d_1 and β but not in c_1 and α



(b)

Case 2: $f \in CL_B, f \in L, f \notin NV$

		$f \in CL_B$			
—	4	5	1		
3	—	—	2	$f \in L$	
		$f \in NV$			

Remark: B_f exists in CL_B and an independent event on i occurs in N_f

Action

Activate B_f

Example:

f in CL_B

 


Figure 5.17

Case 3: $f \notin CL_B, f \in L, f \notin NV$

		$f \in CL_B$		
—	4	5	1	
3	—	—	2	$f \in L$
	$f \in NV$			

Remark: An independent event on i occurs in N_f


but f does not appear in CL_B

Action: Add an entry for f to CL_B and activate B_f

Case 3: $f \notin CL_B, f \in L, f \notin NV$

		$f \in CL_B$		
—	4	5	1	
3	—	—	2	$f \in L$
		$f \in NV$		

Example:

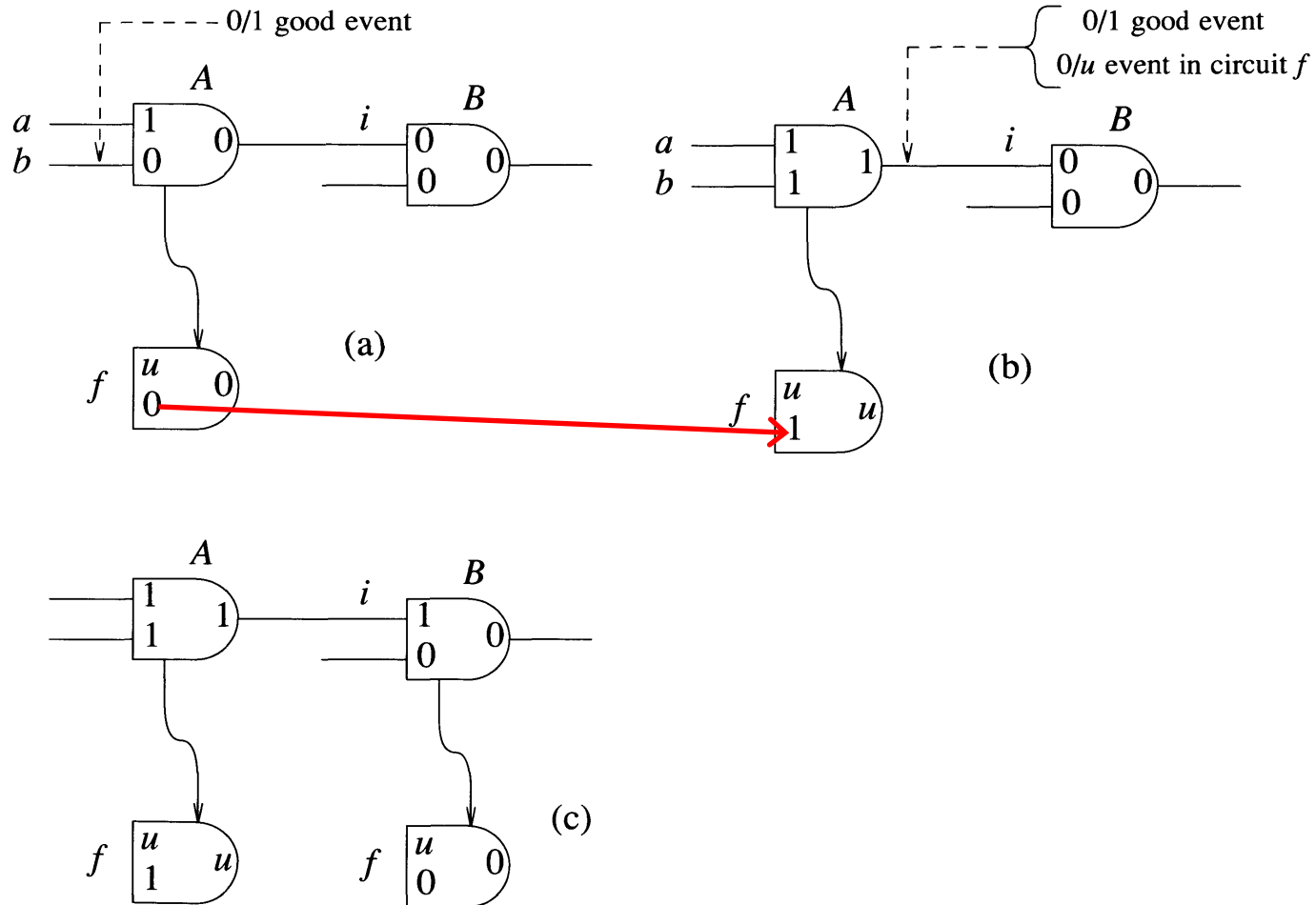

Case 4: $f \notin CL_B, f \notin L, f \in NV$


		$f \in CL_B$		
—	4	5	1	
3	—	—	2	$f \in L$
	$f \in NV$			

Remark: f is newly visible on line i and does not appear in CL_B

Action: Add an entry for f to CL_B

Example:

Add a_1 to CL_e

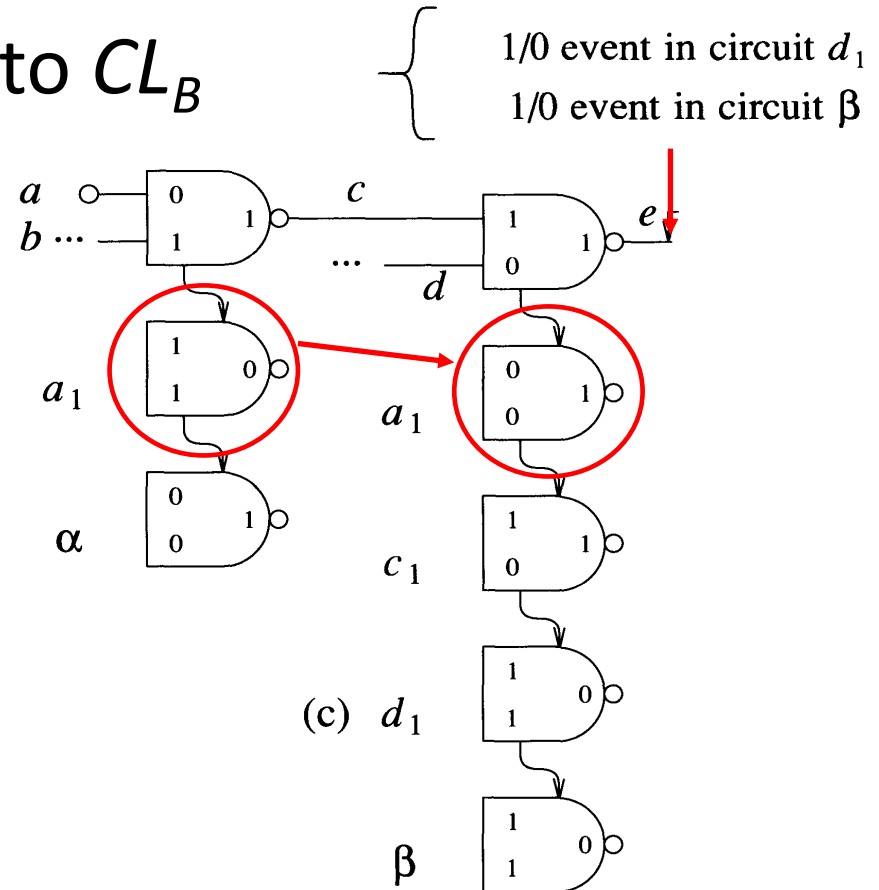

Case 5: $f \in CL_B, f \notin L, f \in NV$



		$f \in CL_B$		
—	4	5	1	
3	—	—	2	$f \in L$
		$f \in NV$		

Remark: f is newly visible

on line i but an entry is already present in CL_B

Action: No Action.

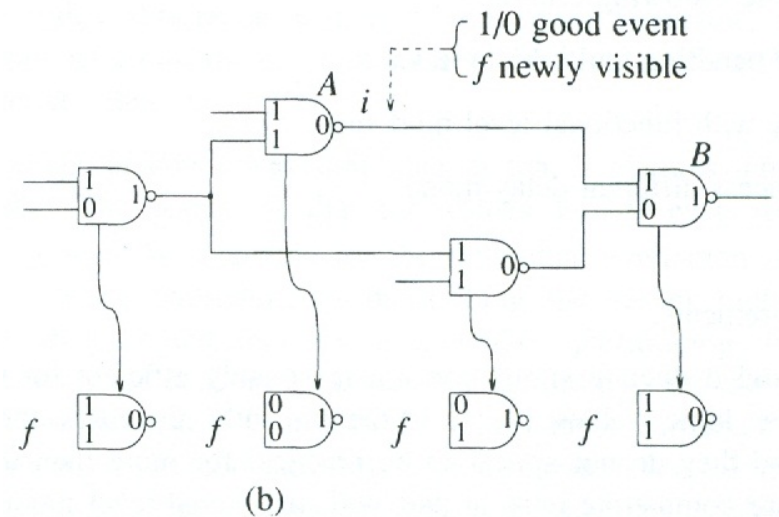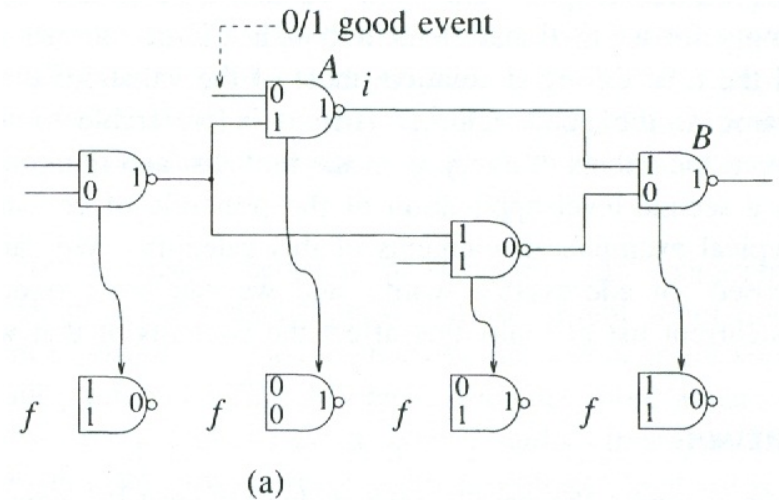Example: In a comb. circuit this occurs with reconv. fanout



Comparison

Criteria	Parallel	Deductive	Concurrent
Multiple Logic Values	Impractical for more than 3 logic values	Impractical for more than 3 logic values	No limit
Functional level Modeling	Partially compatible	Partially compatible	Fully compatible
Different Delay Models	No	No	Yes
Speed*	n^3	n^2	faster?
Storage Reqs.	Medium	Medium	Large

* Comparison for large combinational circuit with n gates. No comparison between deductive and concurrent reported.

Backup

Fault Storage

Characteristic Vector


- Fault insertion Bit = 1
- Fault deletion Bit = 0
- Union – Bit-wise OR
- Intersection – Bit-wise AND
- Memory Intensive

$$L_a = \{3, 9, 12\}$$



(a)

(b)

 

(c)

 
 


Figure 5.12 Three storage structures for lists (a) Fault list (b) Linked list (c) Sequential table (d) Characteristic vector