

CIS 4930 Digital System Testing

Testing for Single Stuck-at Faults (SSFs)

Dr Hao Zheng
Comp. Sci. & Eng.
U of South Florida


Testing Generation

Testing Generation (TG) is a complex problem

We are interested in:

- The **cost of generating** the test
- The **quality** (fault coverage) of the test
- The **cost of applying** the test

Types of Test Generation

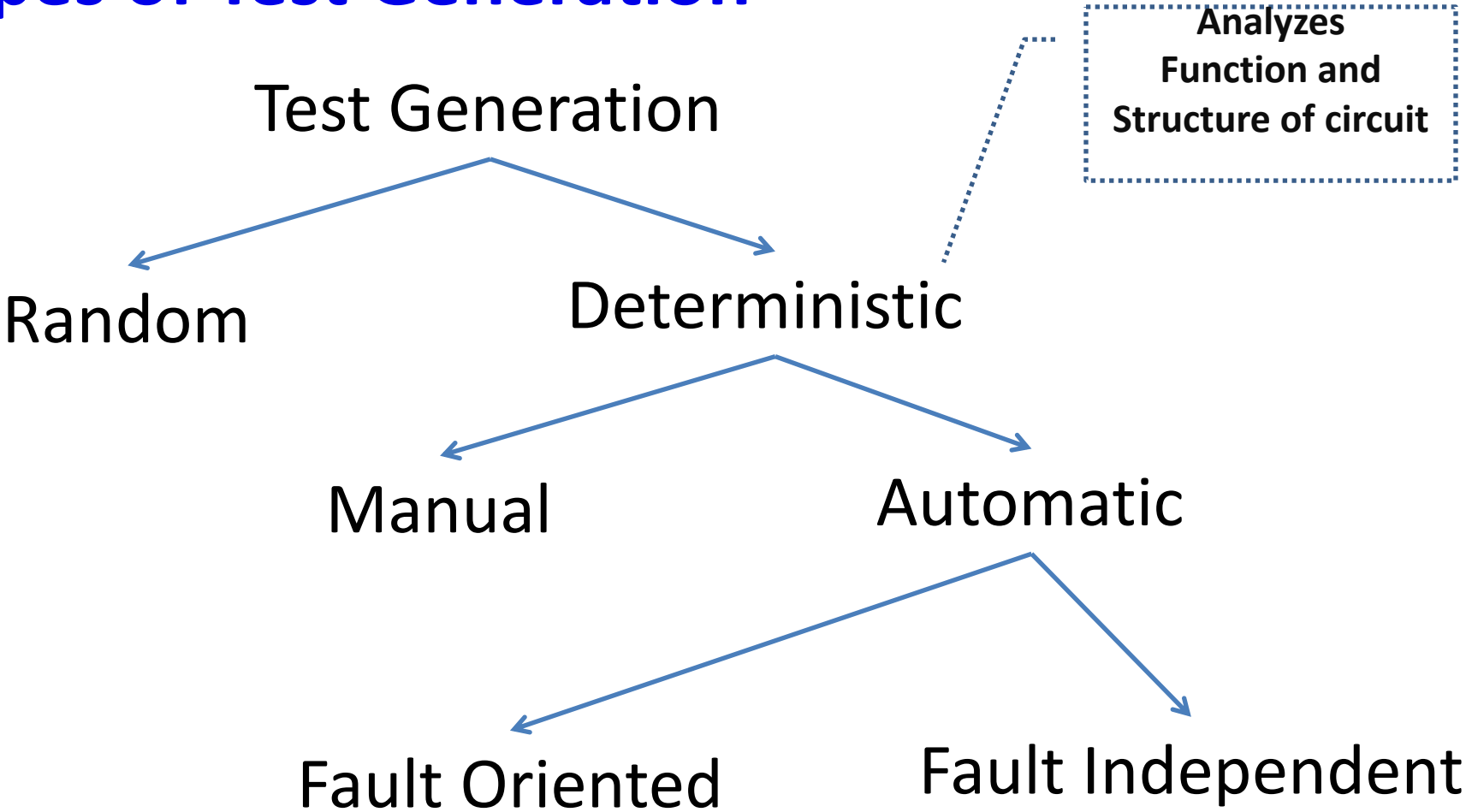

Deterministic TG System

- Model is analyzed to generate test & expected responses
- Diagnostic data can be saved for fault location

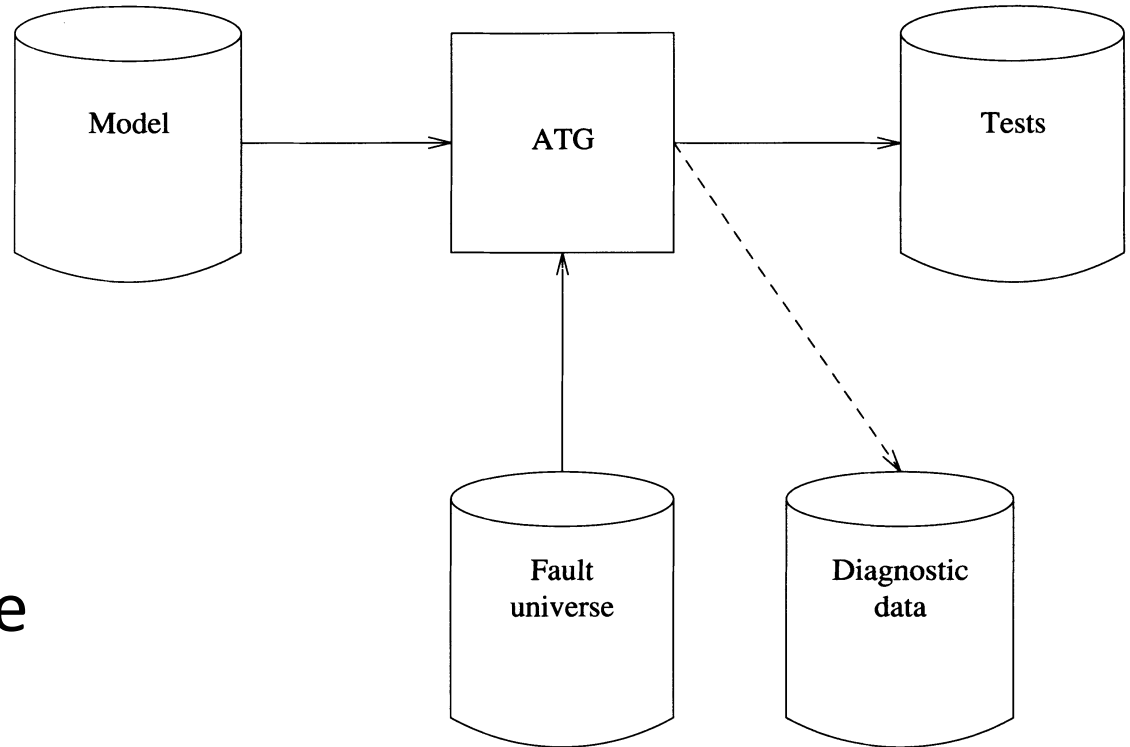


Figure 6.1 Deterministic test generation system

6.2.1 Fault-oriented ATG

- Circuit model – gate-level combinational circuit
- Basic Algorithm – Fanout Free
- Backtracking Algorithm
- *D* Algorithm
- PODEM (Path Oriented Decision Making)
- FAN extends PODEM

Line Justification

- To detect a fault
 - **Activate** the fault
 - **Propagate** the fault to a PO

Activating a fault a l *s-a-v*:

- Determine PI values that force value on line l to \bar{v}

This is known as the **line-justification** problem

Composite Logic Values

Let D represent 1/0 and \bar{D} represent 0/1

v/v_f	
0/0	0
1/1	1
1/0	D
0/1	\bar{D}

AND	0	1	D	\bar{D}	X
0	0	0	0	0	0
1	0	1	D	\bar{D}	X
D	0	D	D	0	X
\bar{D}	0	D'	0	\bar{D}	X
X	0	X	X	X	X

OR	0	1	D	\bar{D}	X
0	0	1	D	D'	0
1	1	1	1	1	1
D	D	1	D	1	X
\bar{D}	\bar{D}	1	1	\bar{D}	X
X	X	1	X	X	X

Fig 6.3 TG for l - s - a - v in Fanout Free circuit

begin

set all values to x // initialization of all wires to X



Justify(l, \bar{v}) // justification of line l

if $v = 0$ **then** *Propagate* (l, D)

else *Propagate* (l, \bar{D})

end

Line Justification

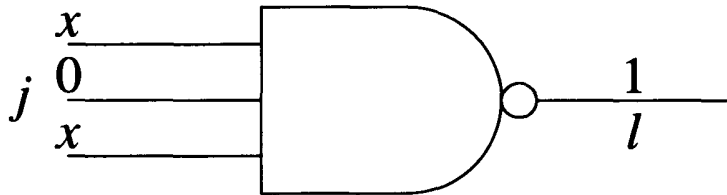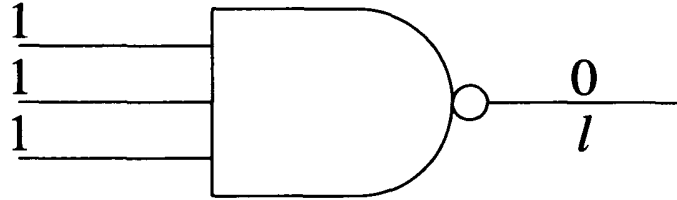

Justify (l, val)

begin

set *l* to *val*

if *l* is a PI **then return**

/ l is a gate (output) */*

c = controlling value of *l*

i = inversion of *l*

inval = $val \oplus i$

if (*inval* = \bar{c})

then for every input *j* of *l*

Justify (j, inval)

else

begin

select one input (*j*) of *l*

Justify (j, inval)

end

end

Error Propagation – Fanout Free circuit

Propagate (l, err)
/* err is D or \bar{D} */

begin

set l to err

if l is PO **then return**

k = the fanout of l

c = controlling value of k


i = inversion of k

for every input j of k other than l


Justify (j, \bar{c})

Propagate (k, $err \oplus i$)

end

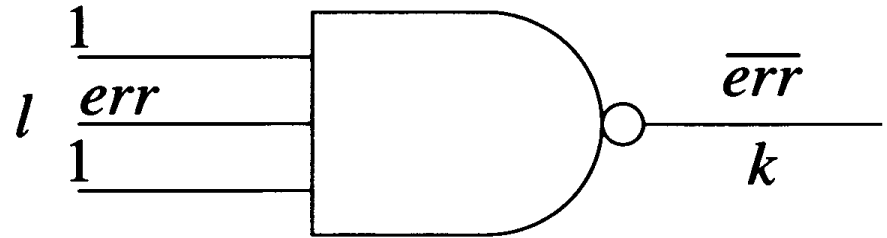


Example 6.1

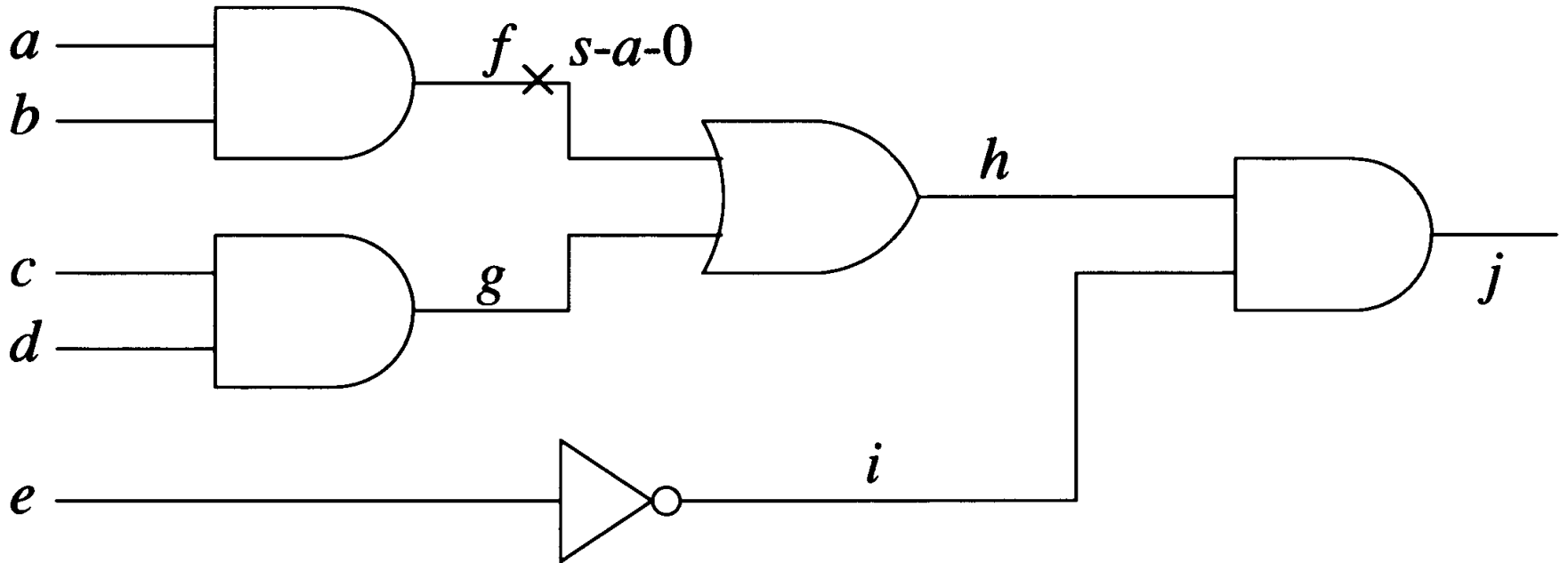


Find an input vector such that f $s-a-0$ is observable on j


Example 6.1

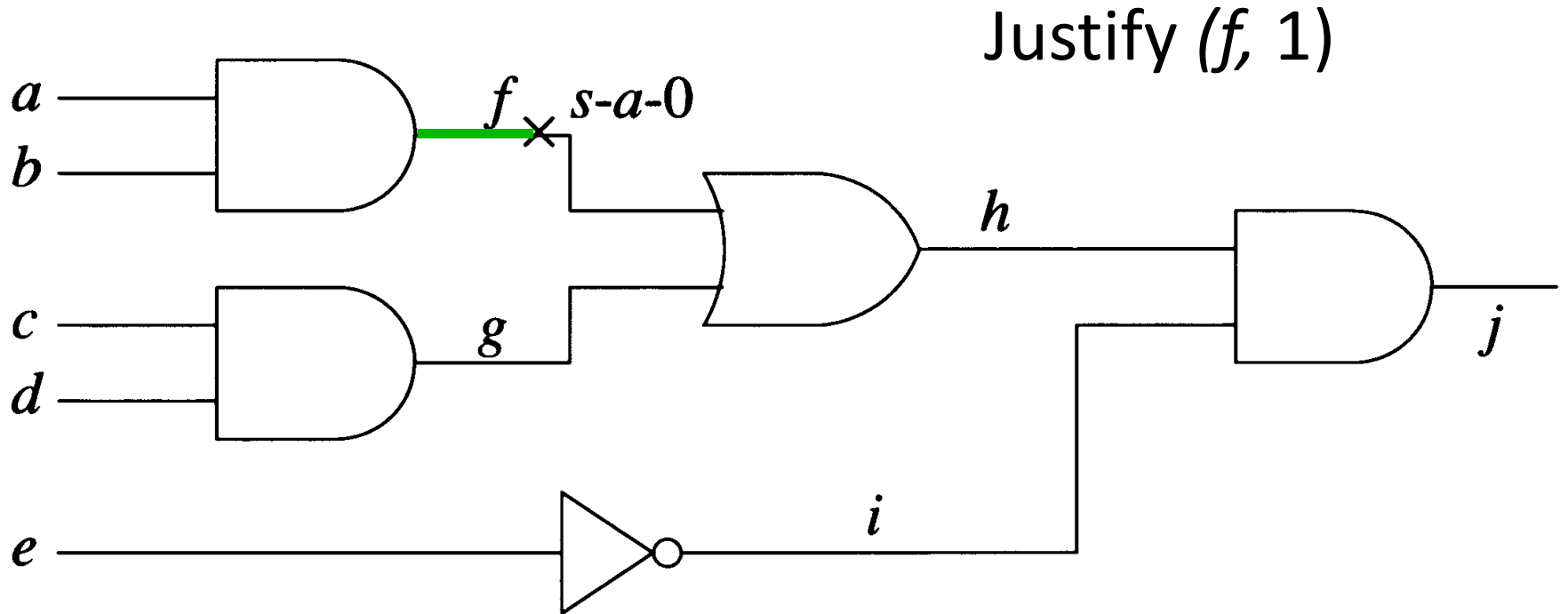


Example 6.1

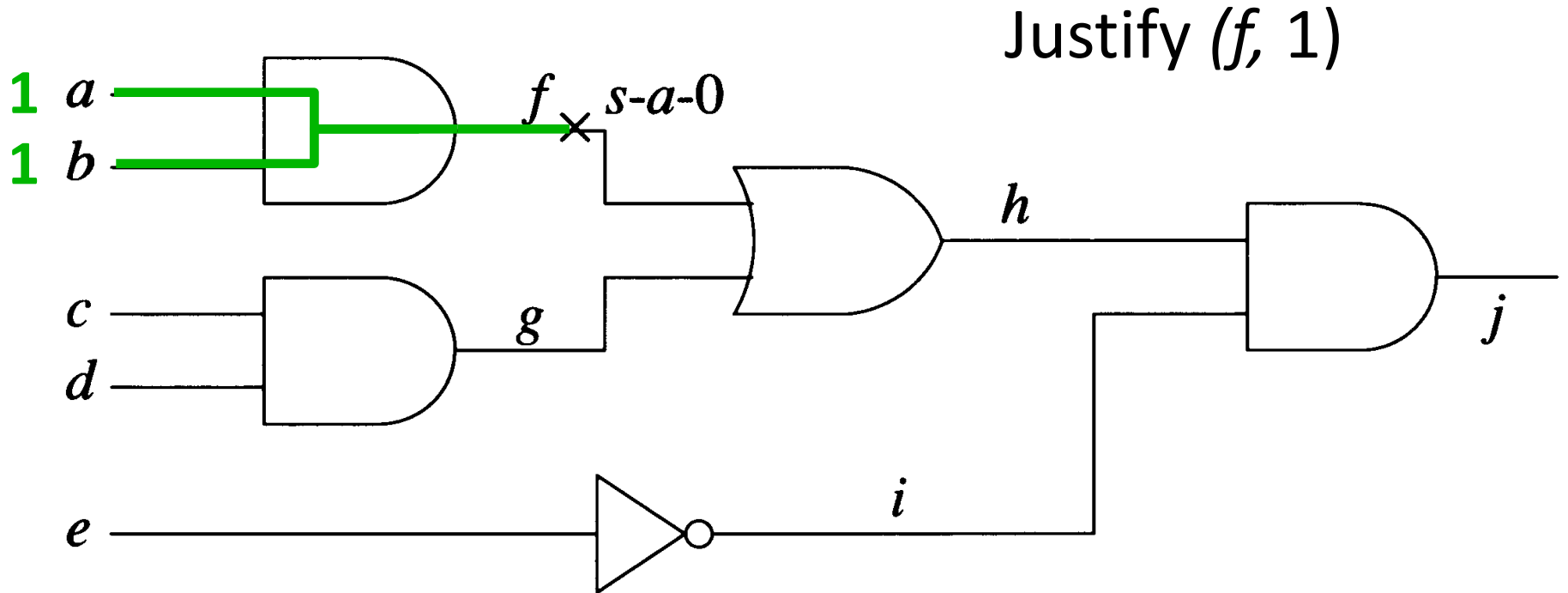

Example 6.1

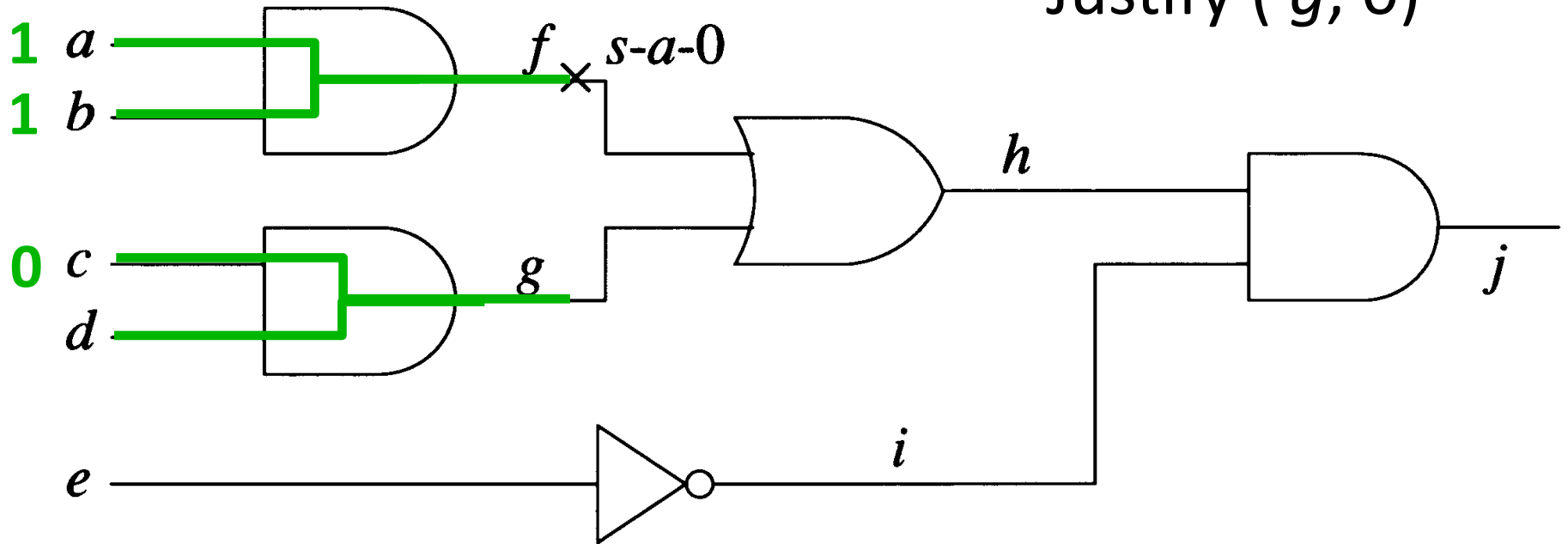


Example 6.1

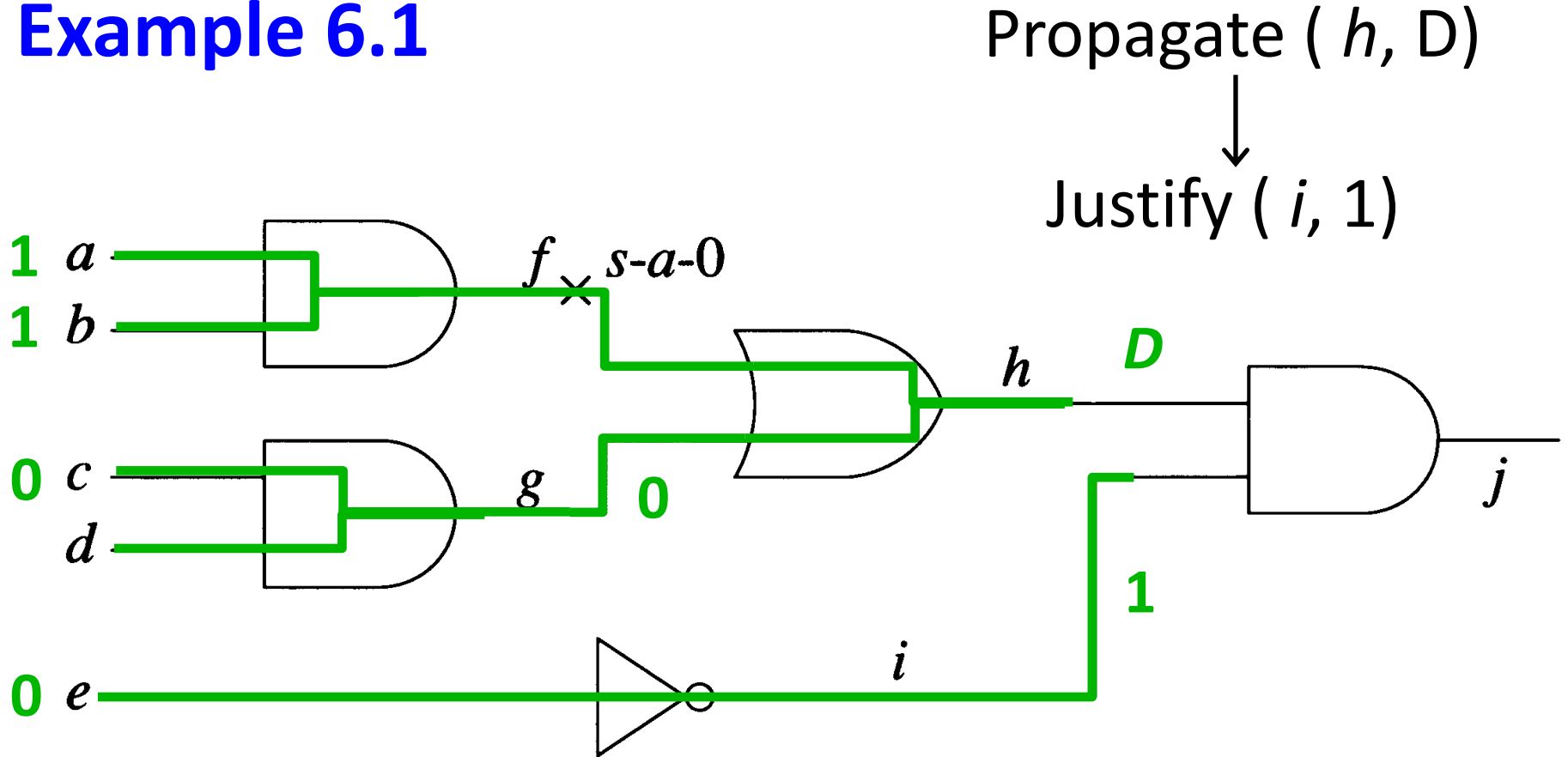


Example 6.1

Propagate (j, D)

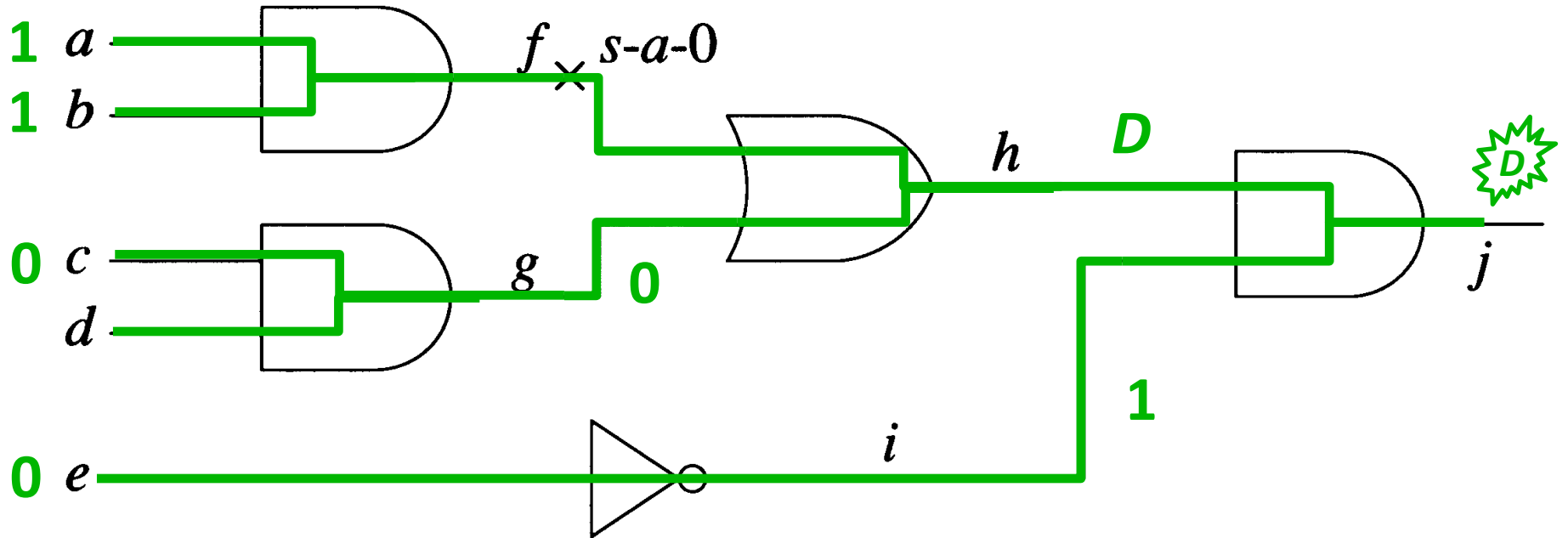

Example 6.1

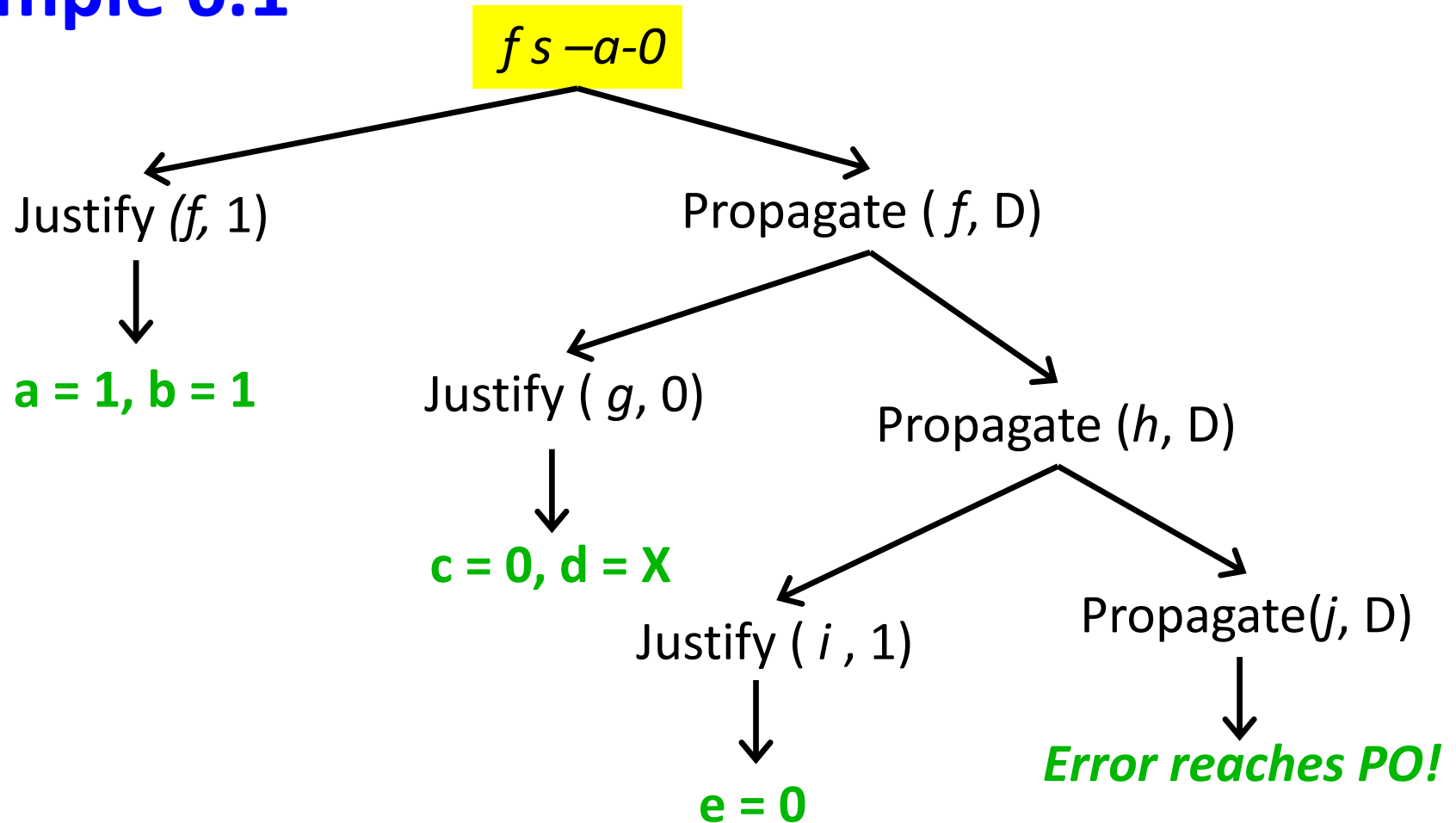

Fanout Free vs. Fanout


→ For Fanout Free circuit

- Line justification problems are independent
- Sets of PI's assigned to justify required values are mutually disjoint


→ Circuits with Fanout

- Several ways to propagate error to PO
- Fundamental difficulty: see following examples
resulting line justification problems are no longer independent


Example 6.2

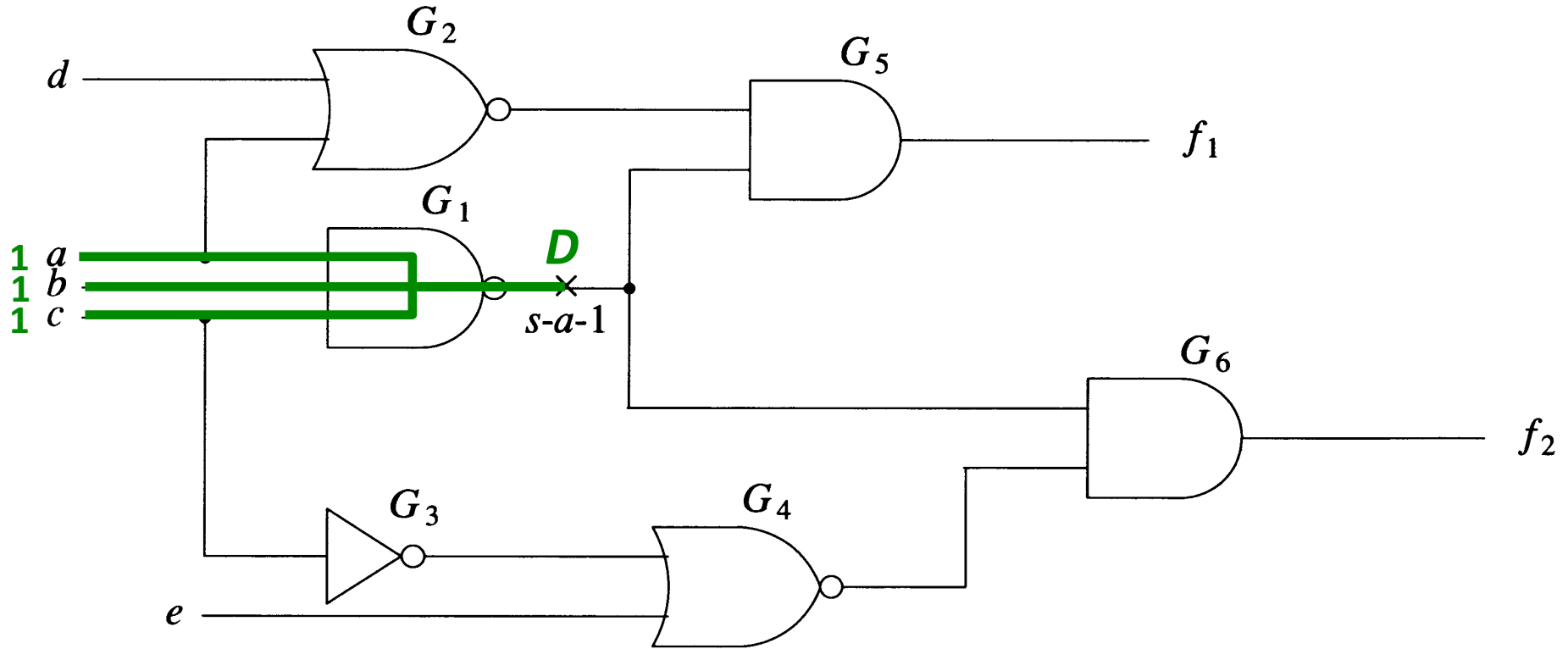


Example 6.2

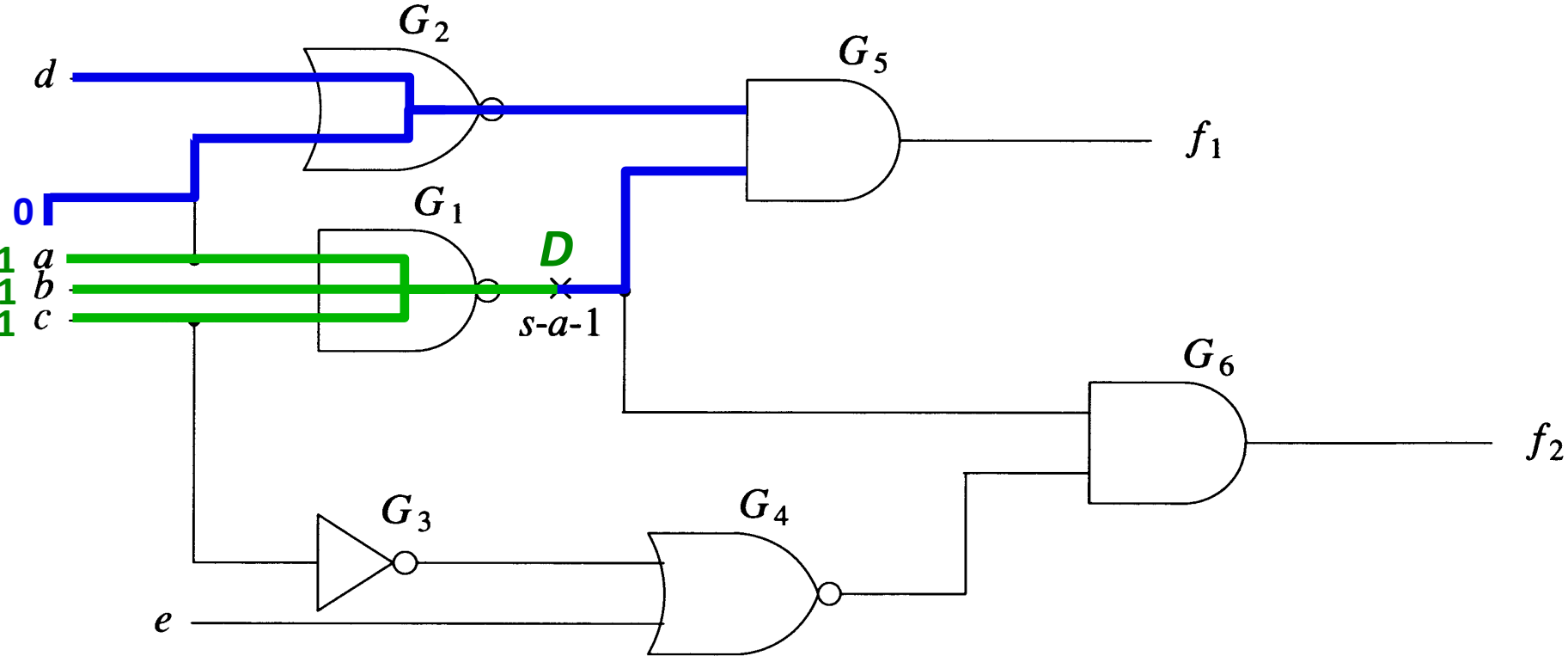


Example 6.2

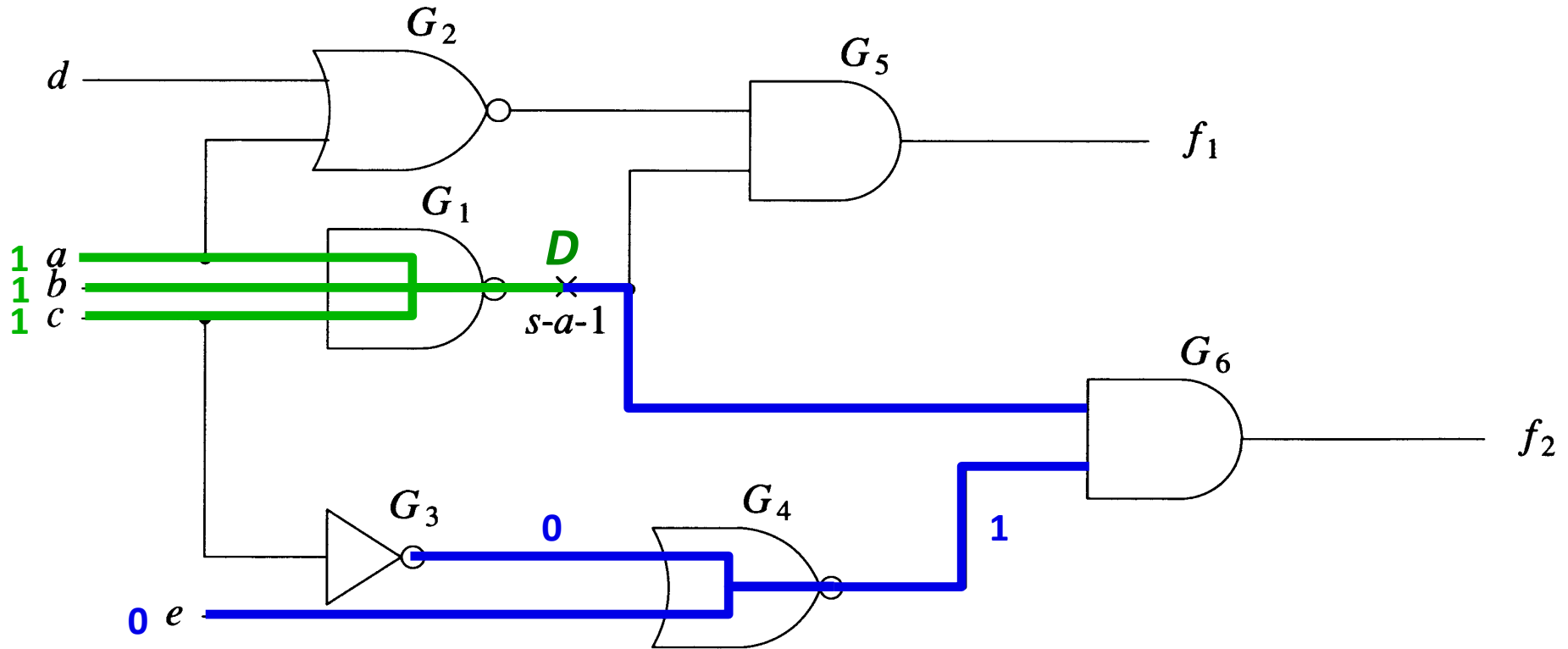


Example 6.2

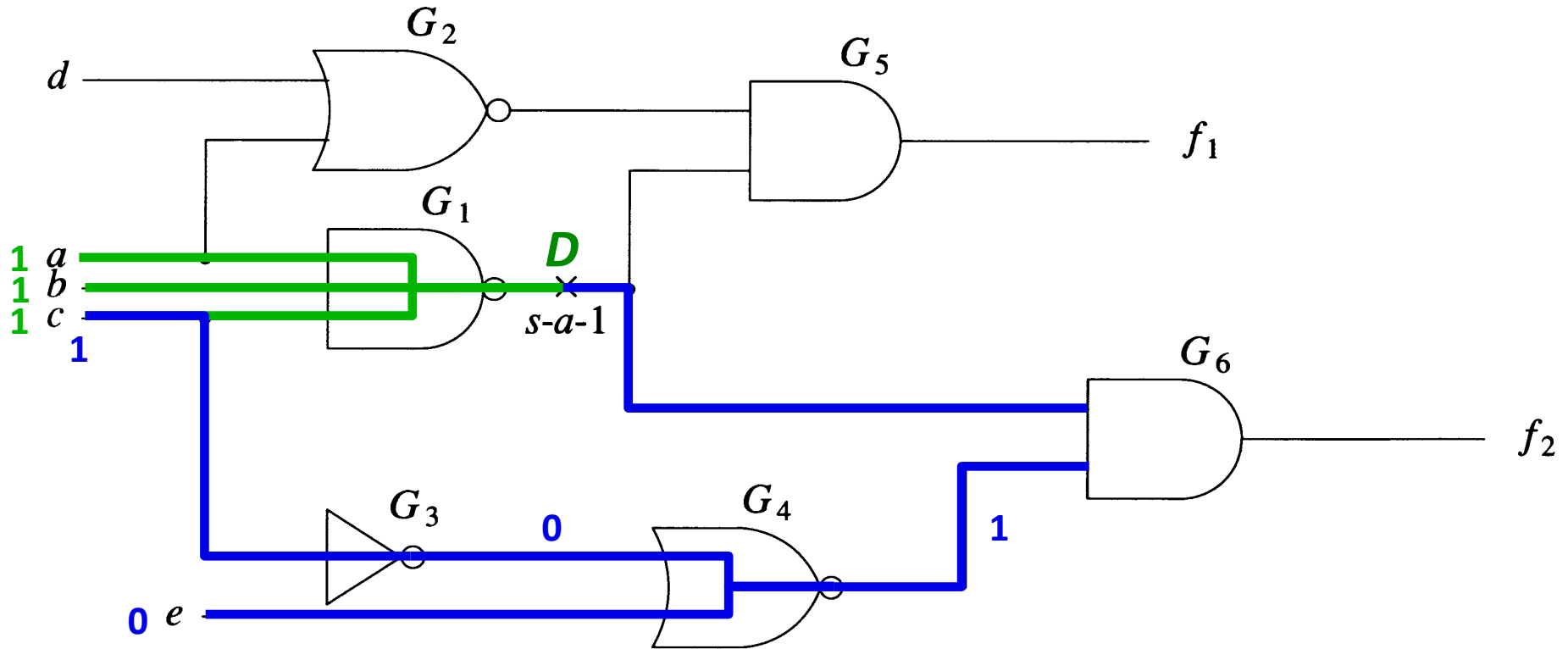


Example 6.2

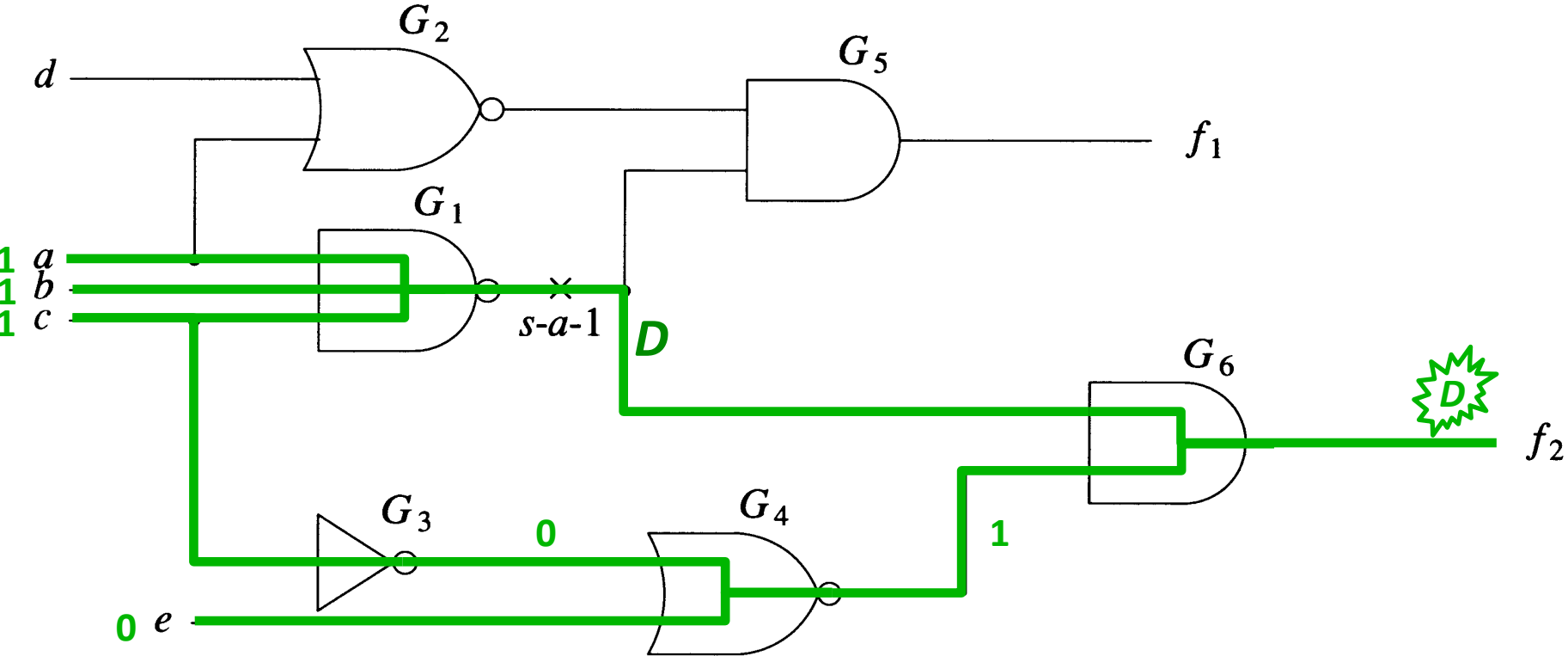

Example 6.2

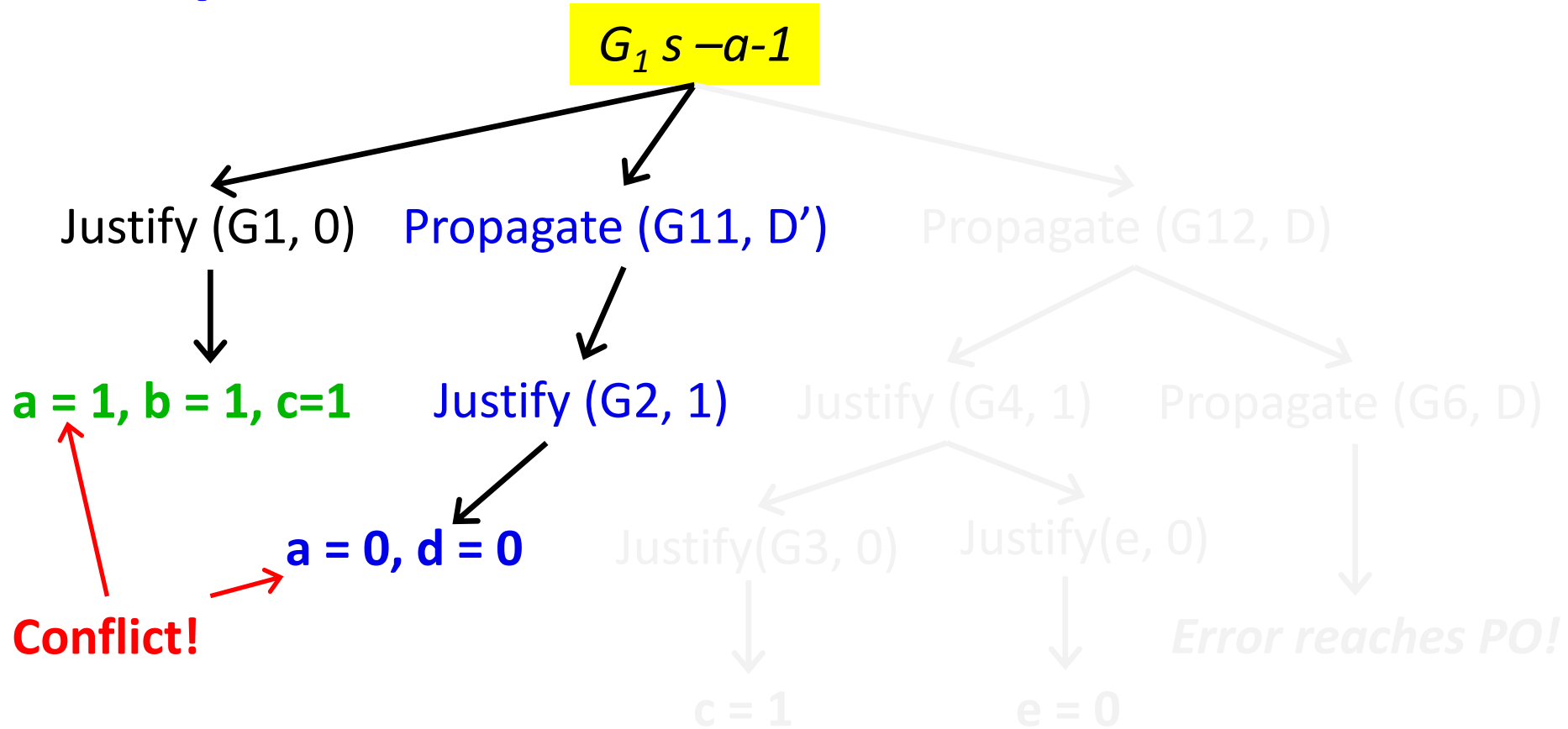


Example 6.2

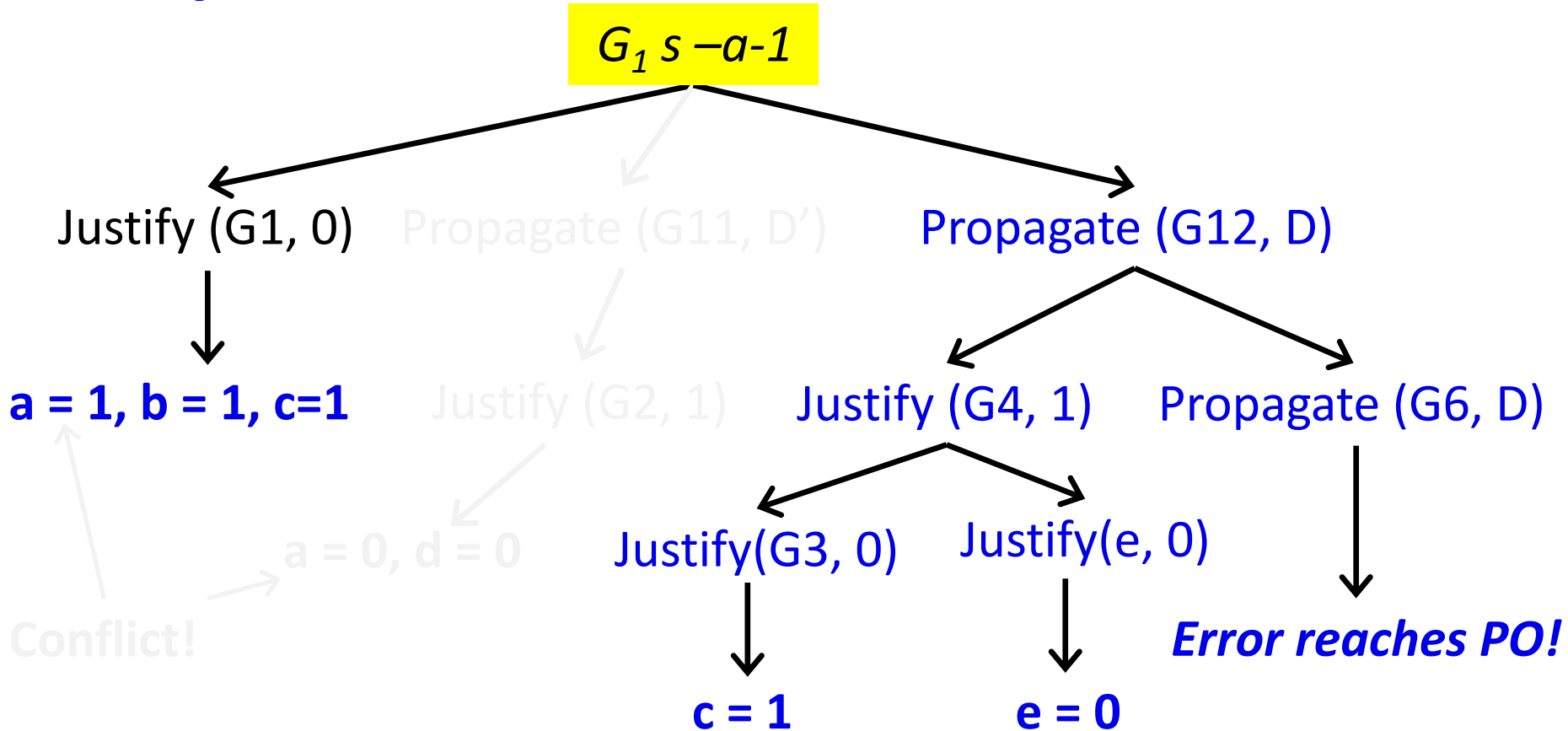


Backtracking Strategy

- Search for a test vector → decision process
- Several alternatives for a line justification problem
 - Pick one alternative
 - If it leads to an inconsistency, then backtrack!
- Backtracking Strategy
 - Systematic exploration
 - Recovery from incorrect decisions
 - Invert all values assigned since last decision


Example 6.3

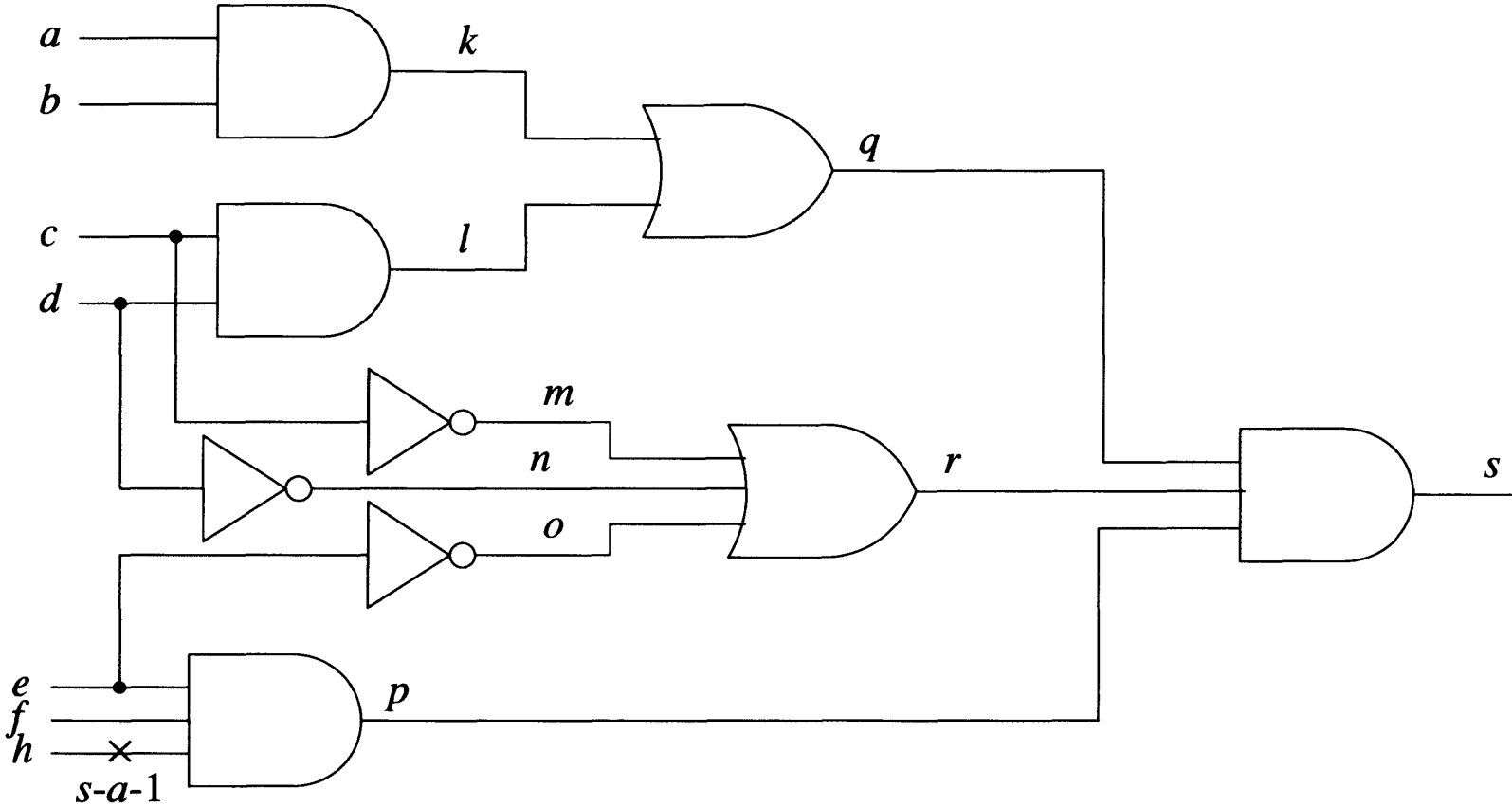


Example 6.3

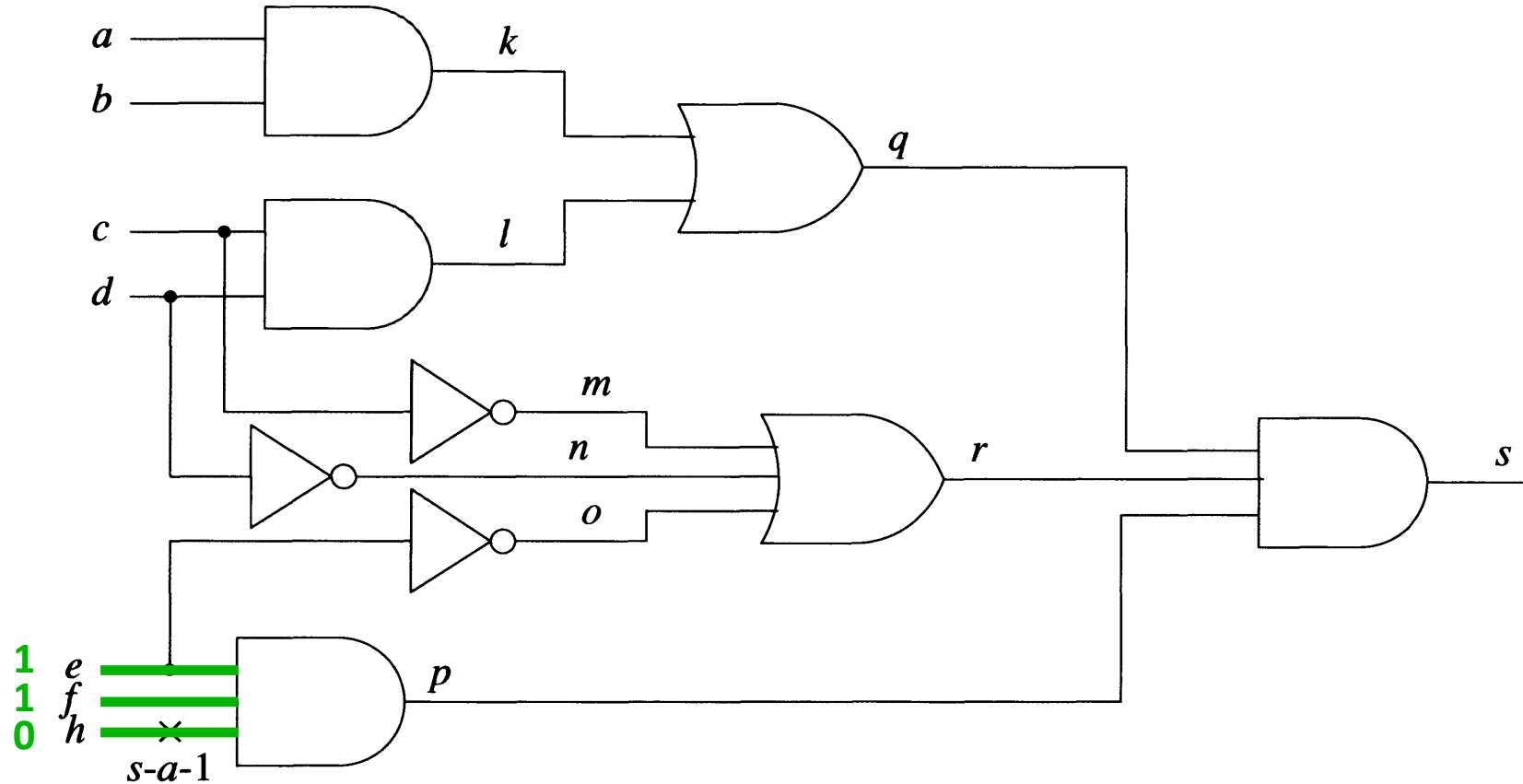


Example 6.3

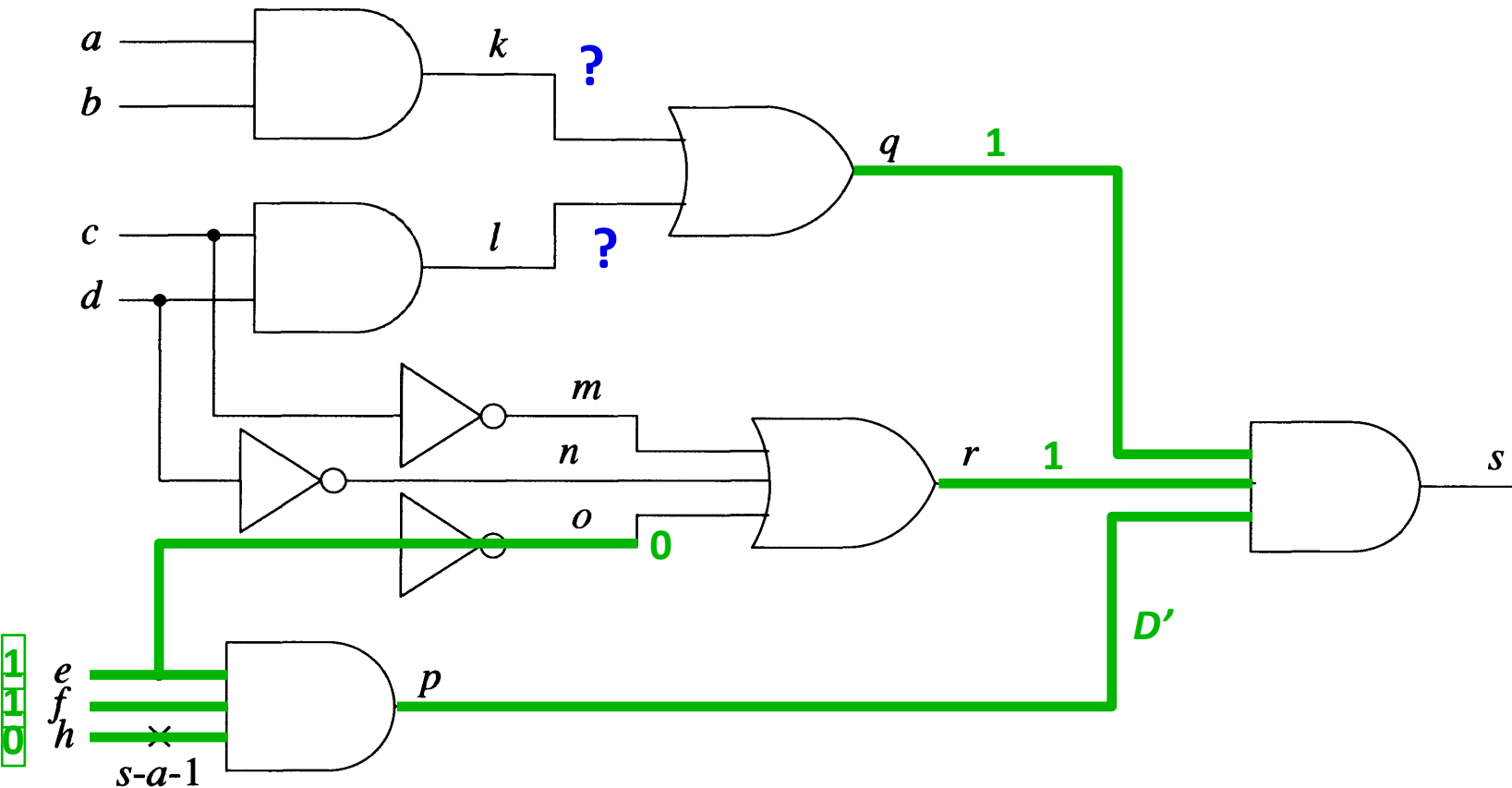


Example 6.3

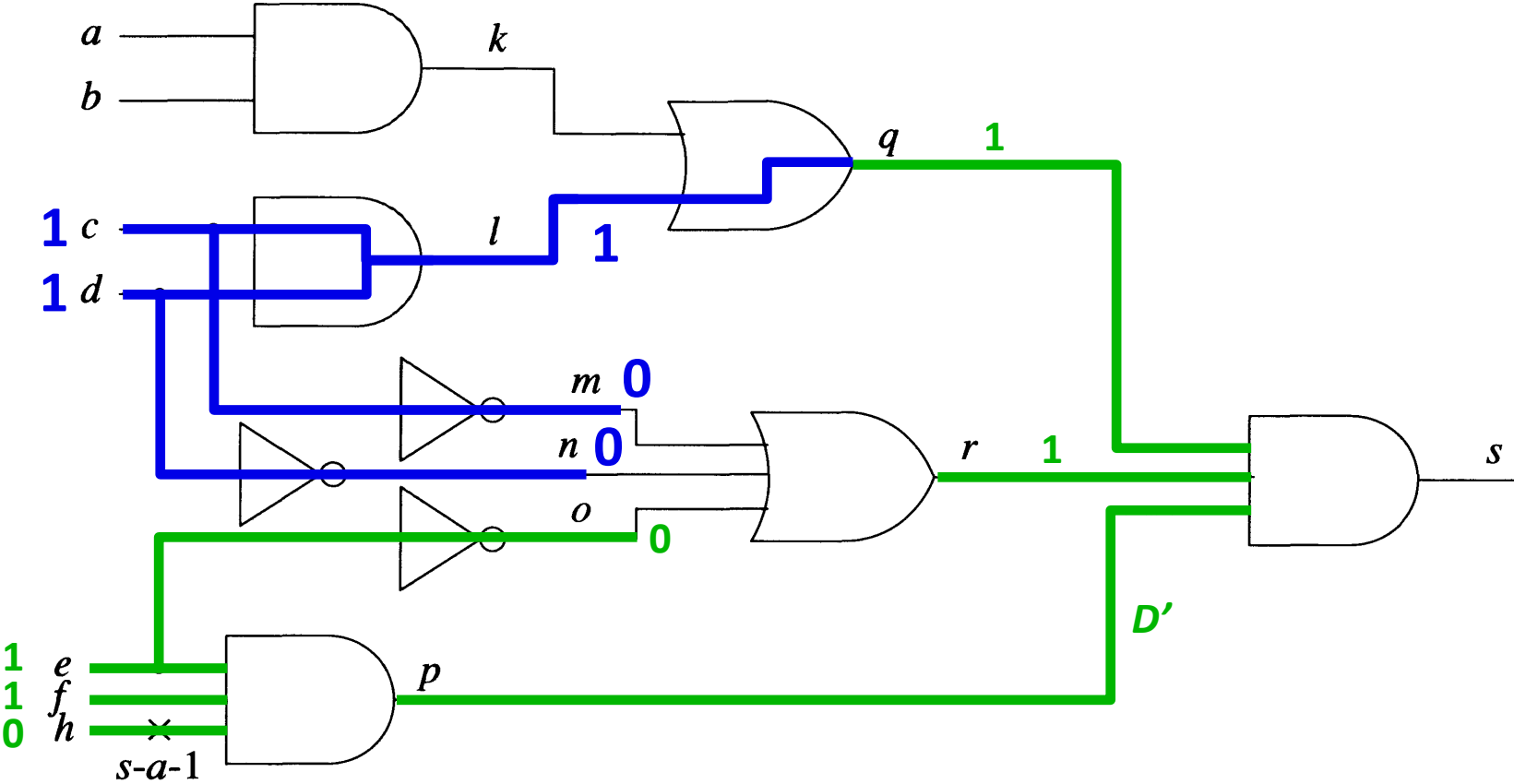


Example 6.3

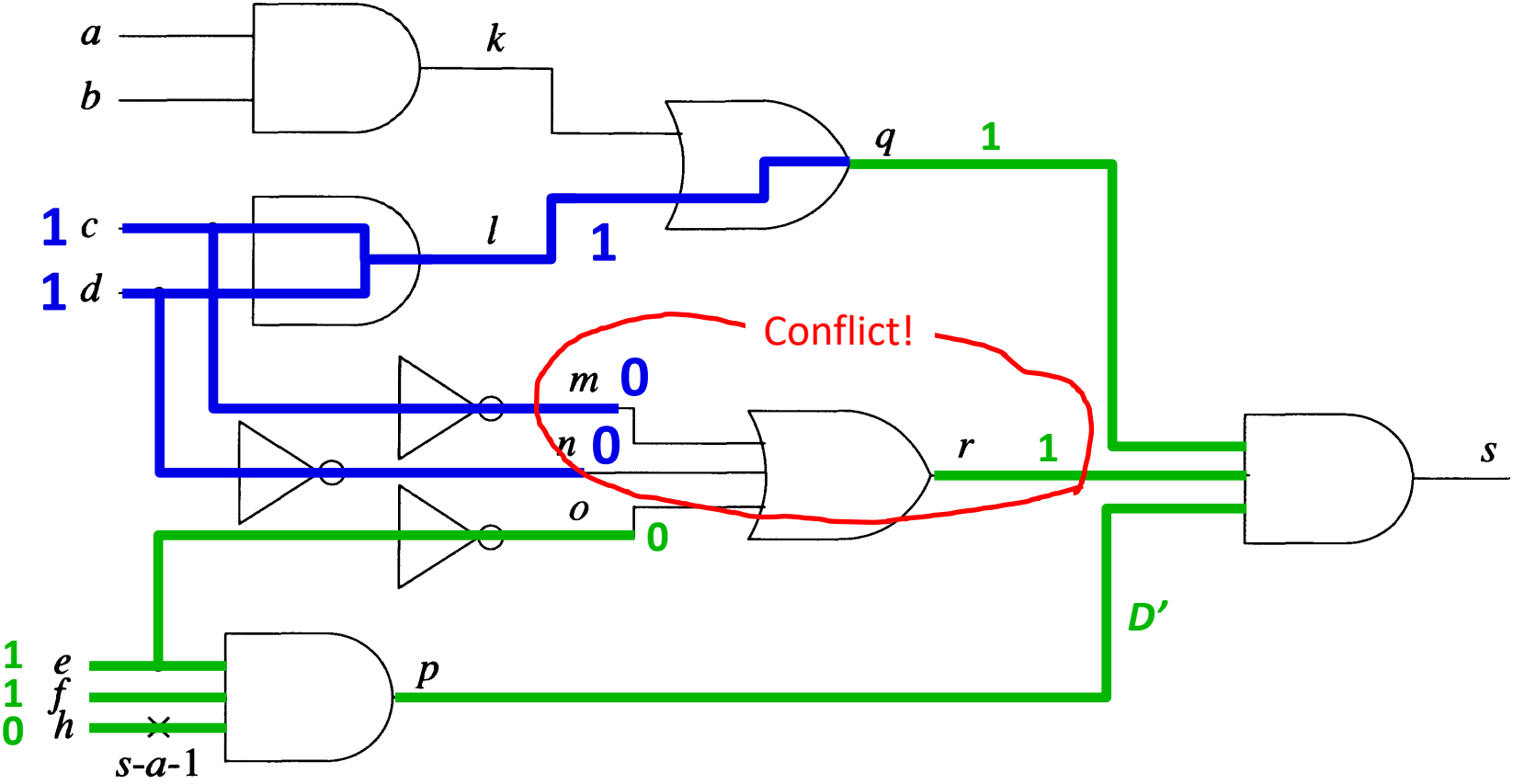


Example 6.3

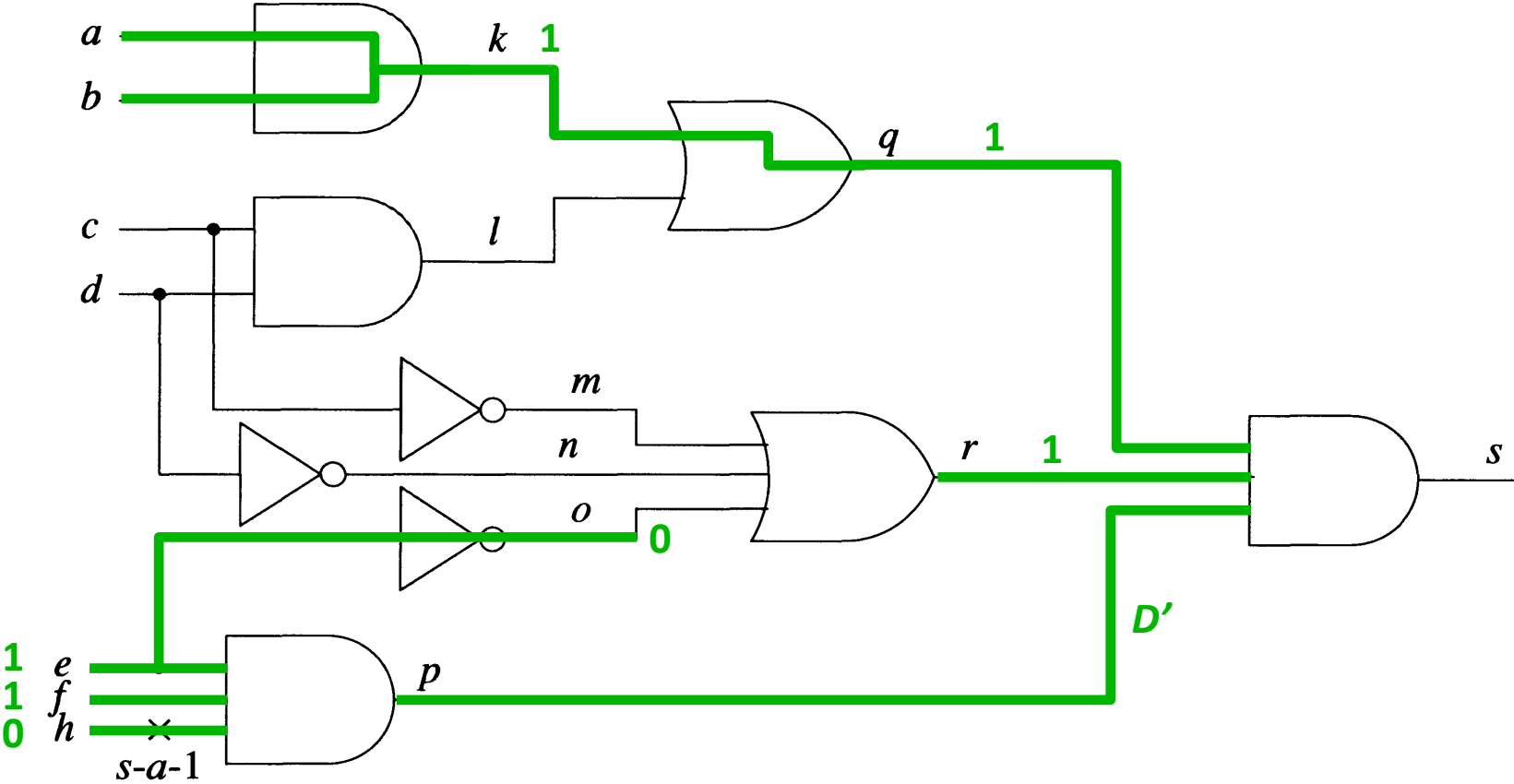

Example 6.3

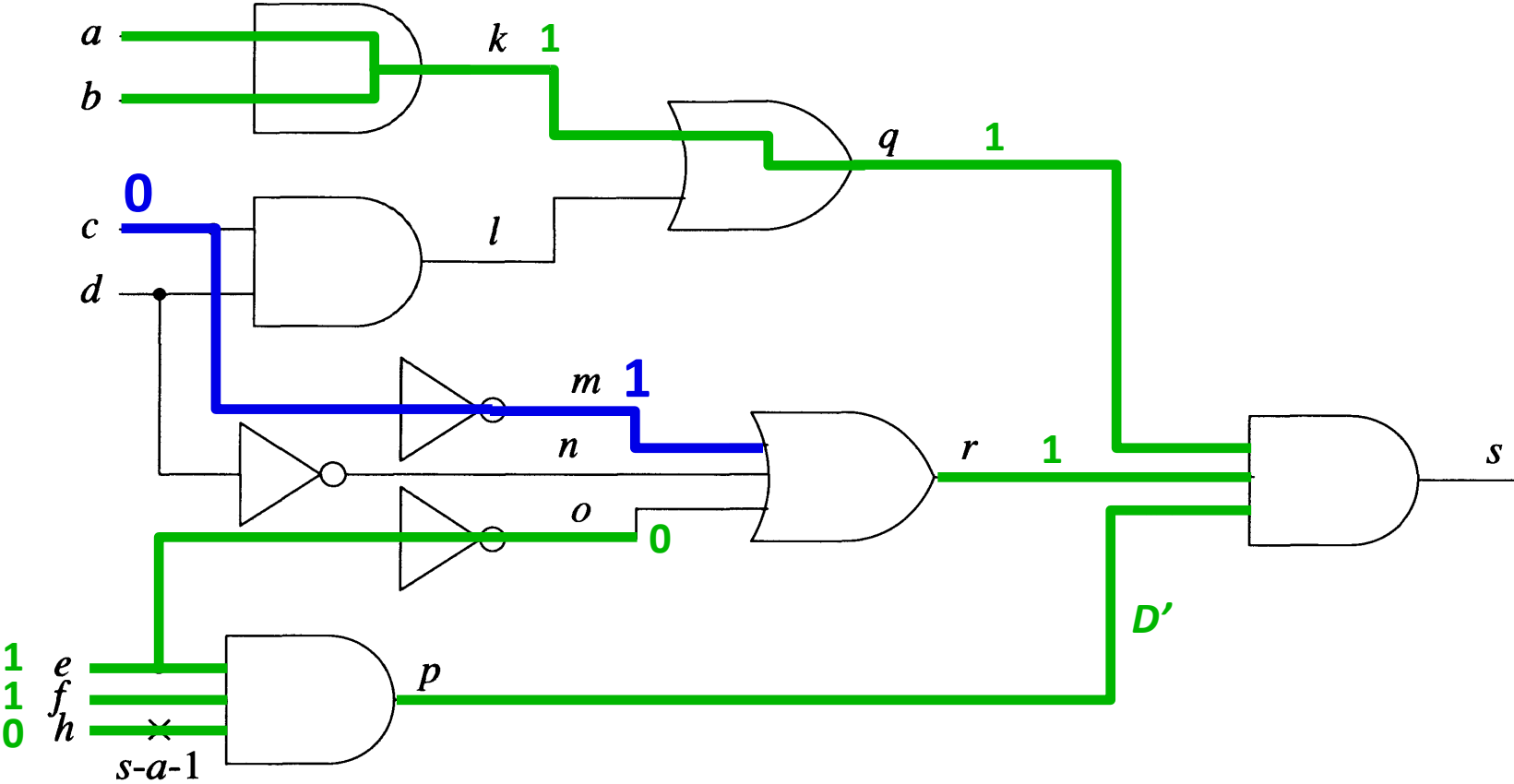

Example 6.3

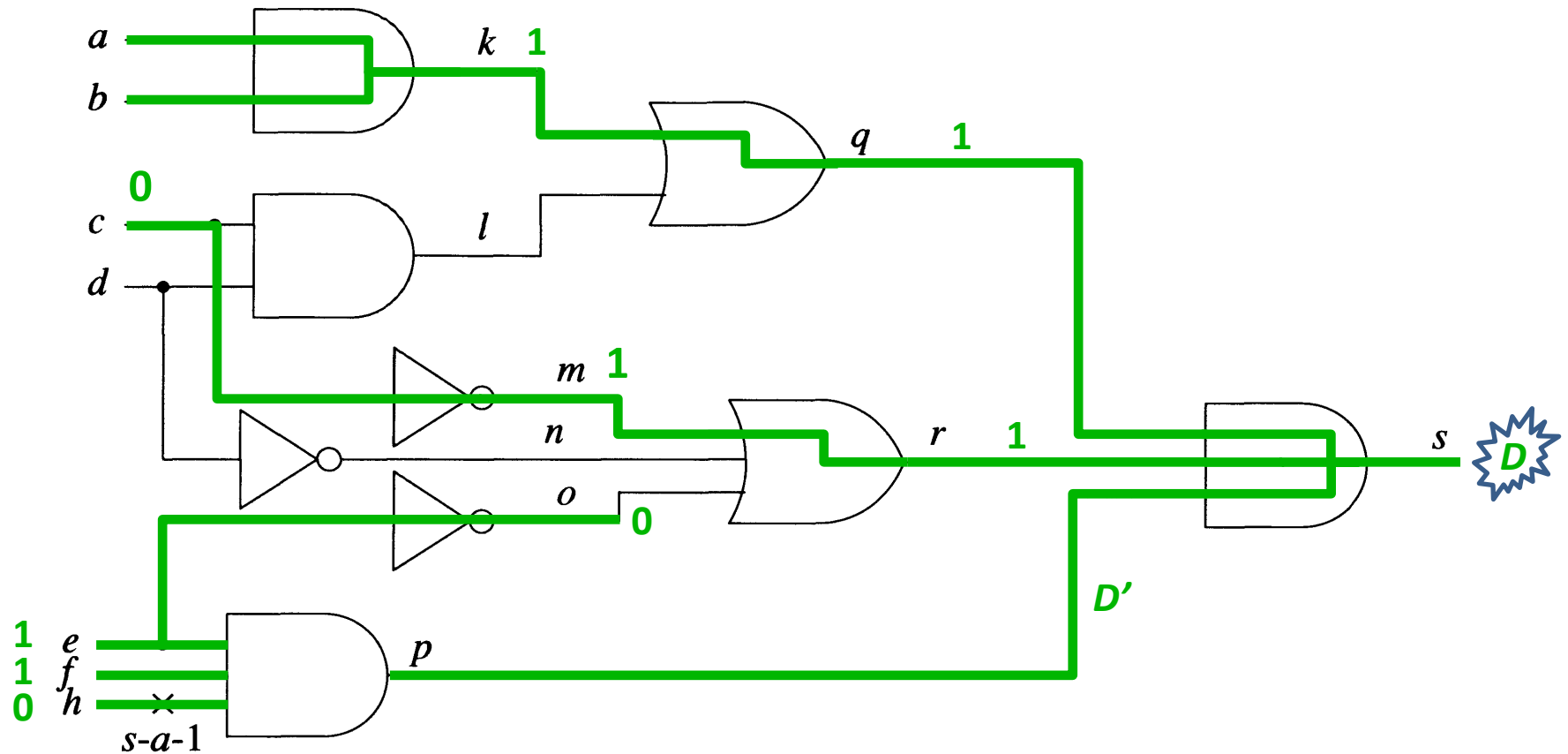

Decision: choose one alternative if there are multiple alternatives to justify() or propagate()


Implication: compute new values as a result of **decision**, and check inconsistencies.

Decisions	Implications	Remarks
	$h = D'$ $e = 1$ $f = 1$ $p = D'$ $r = 1$ $q = 1$ $o = 0$ $s = D'$	Initial Implications
$l = 1$	$c = 1$ $d = 1$ $m = 0$ $n = 0$ $r = 0$	To justify $q=1$ Contradiction
$k = 1$	$a = 1$ $b = 1$	To justify $q = 1$
$m = 1$	$c = 0$ $l = 0$	To justify $r=1$


Fig 6.10 TG Algorithm Outline

```
Solve()
begin
  if Imply_and_check() = FAILURE then return FAILURE
  if (error at PO and all lines are justified)
    then return SUCCESS
  if (no error can be propagated to a PO)
    then return FAILURE
  select an unsolved problem
  repeat
    begin
      select one untried way to solve it
      if Solve() = SUCCESS then return SUCCESS
    end
  until all ways to solve it have been tried
  return FAILURE
end
```

Decision Tree

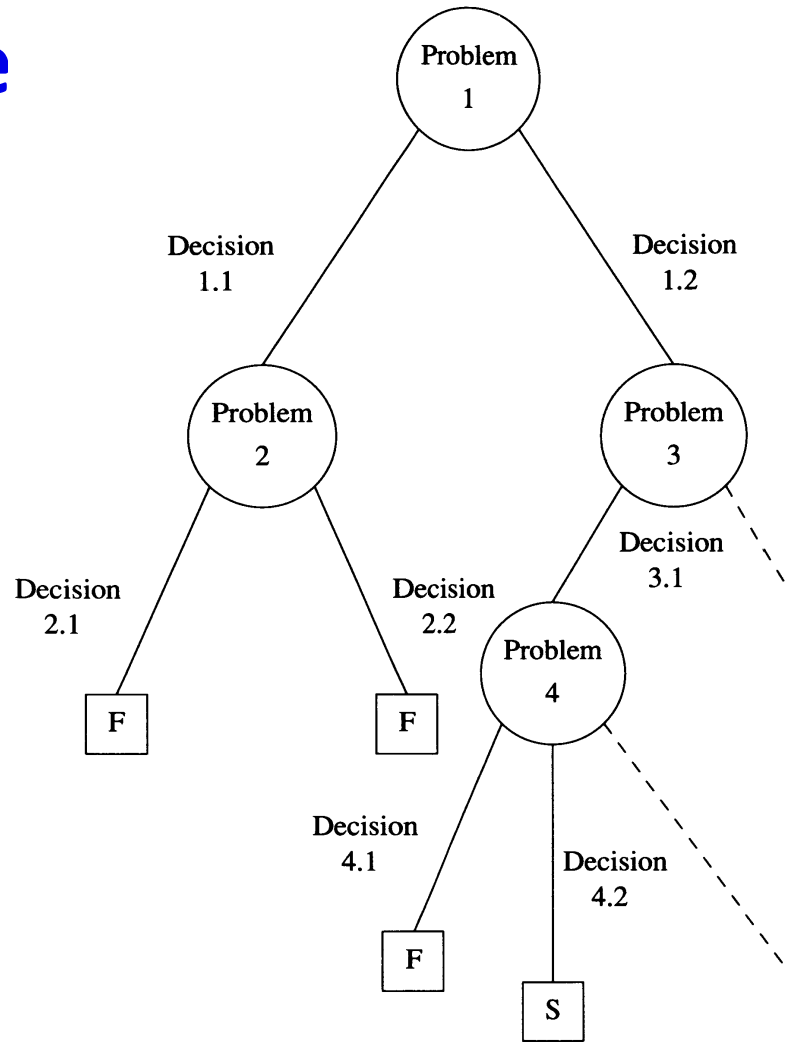

(a)

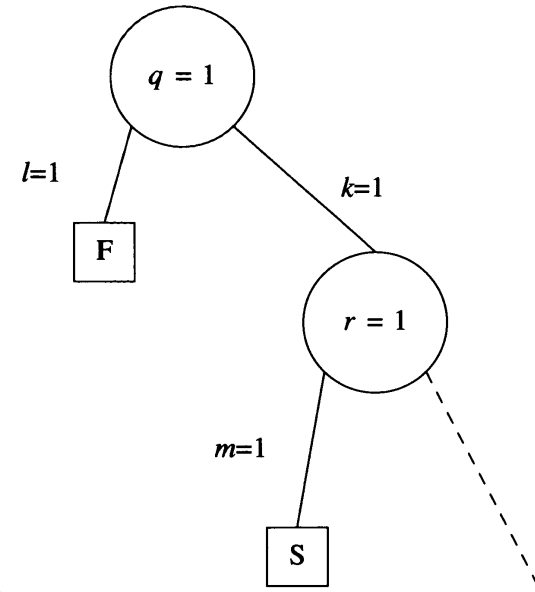

(b)

TG Failure for an Undetectable Fault

- Solve() is exhaustive – guarantee to find a test if one exists.
- worst case complexity is exponential


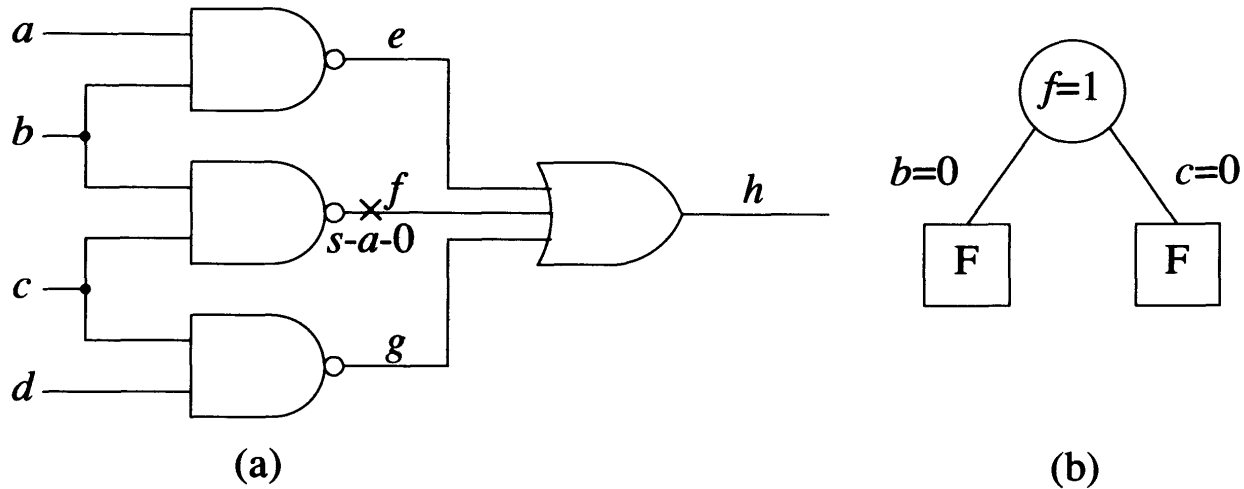


Figure 6.12 TG failure for an undetectable fault (a) Circuit (b) Decision tree

D-Frontier

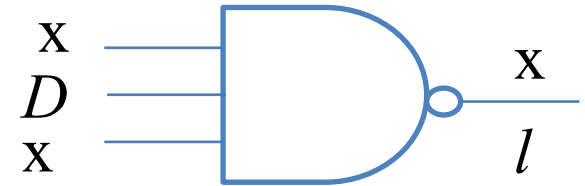
- **D-frontier** – all gates whose output value is currently x but have one or more error signals on their inputs.
- *D-drive* operation –
 - Pick a gate and try to propagate error
- If **D-frontier** becomes empty
 - ⇒ No error can be propagated to PO
 - ⇒ Backtracking should occur




Gates in D-frontier indicate necessary decisions in order to proceed.

J-Frontier

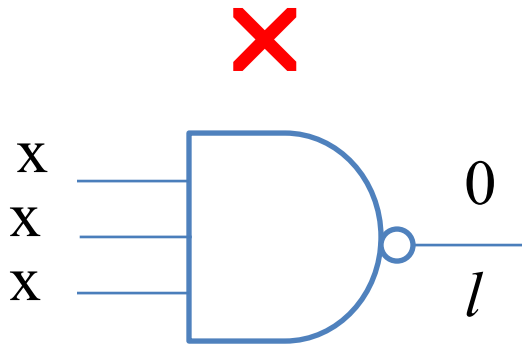- **J-frontier** – all gates whose output value is known, but not implied by its input values
- Helps keep track of *currently unsolved* line-justification problems



All inputs are implied to be 1.

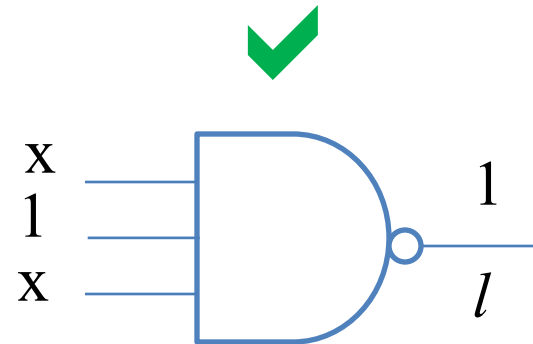

No implications on x-inputs.

Implication Process





3 Steps:

1. Compute all values that can be uniquely determined by implication
2. Check for consistency and assign values
3. Maintain the *D-frontier* and *J-frontier*





Implication can be **forward** or **backward**.

Backward Implication Propagation

Before

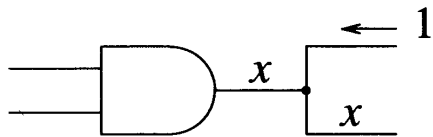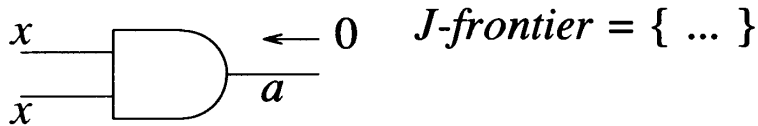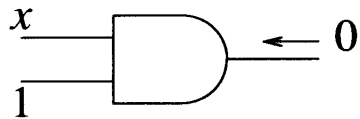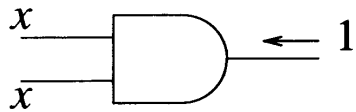

After

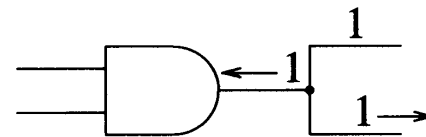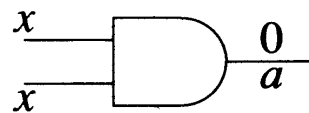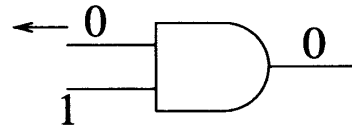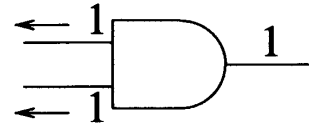

Gate a gets added to J -frontier after $a = 0$

(a)

(b)


J -frontier = { ..., a }

(c)

(d)


Forward Implication Propagation

Figure 6.15

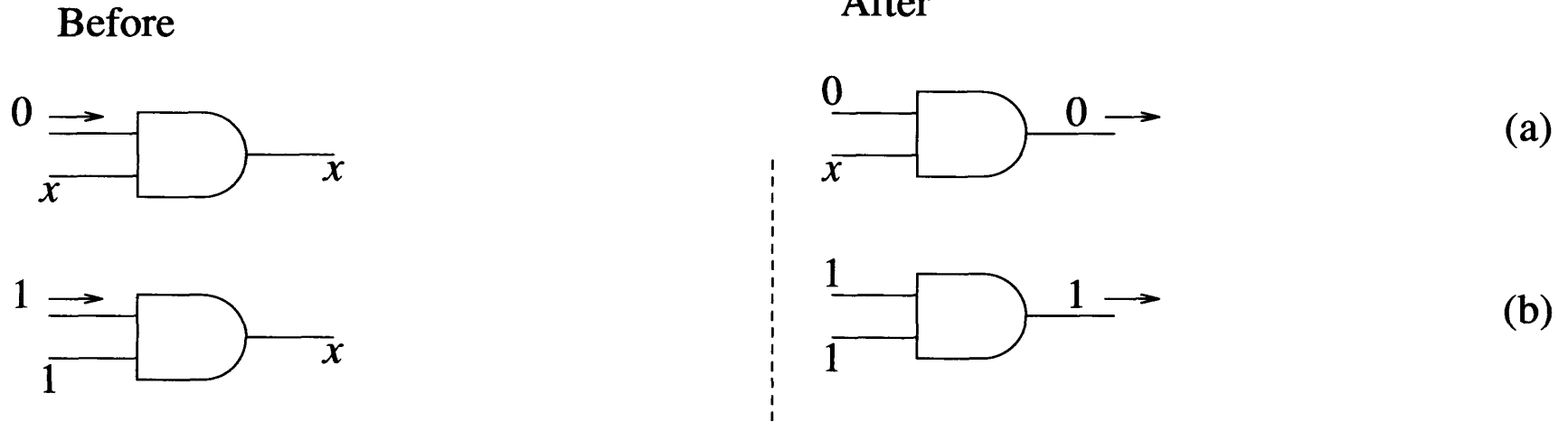

Forward Implication Propagation

Figure 6.15

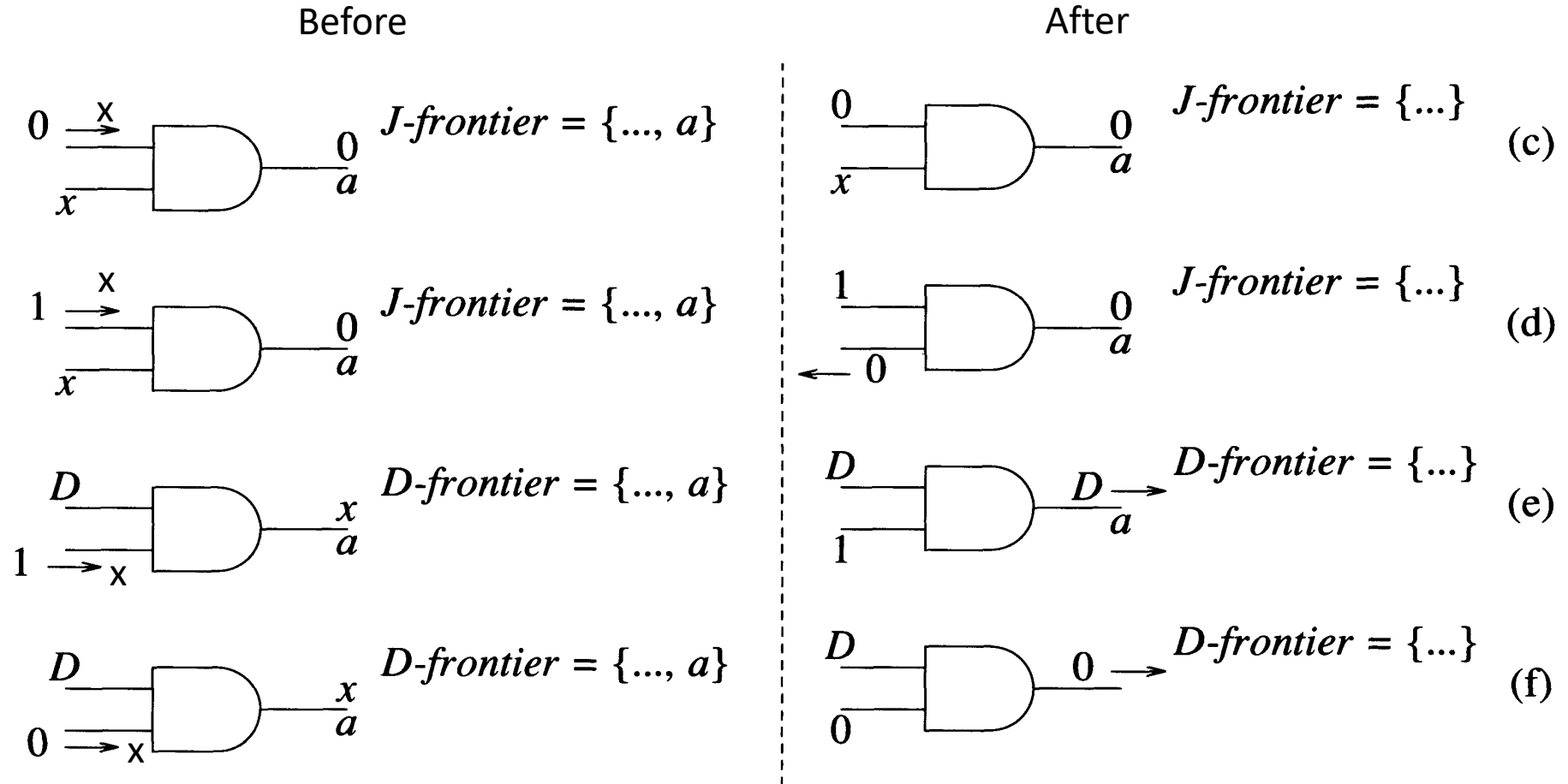

Forward Implication Propagation – cont'd

Figure 6.16


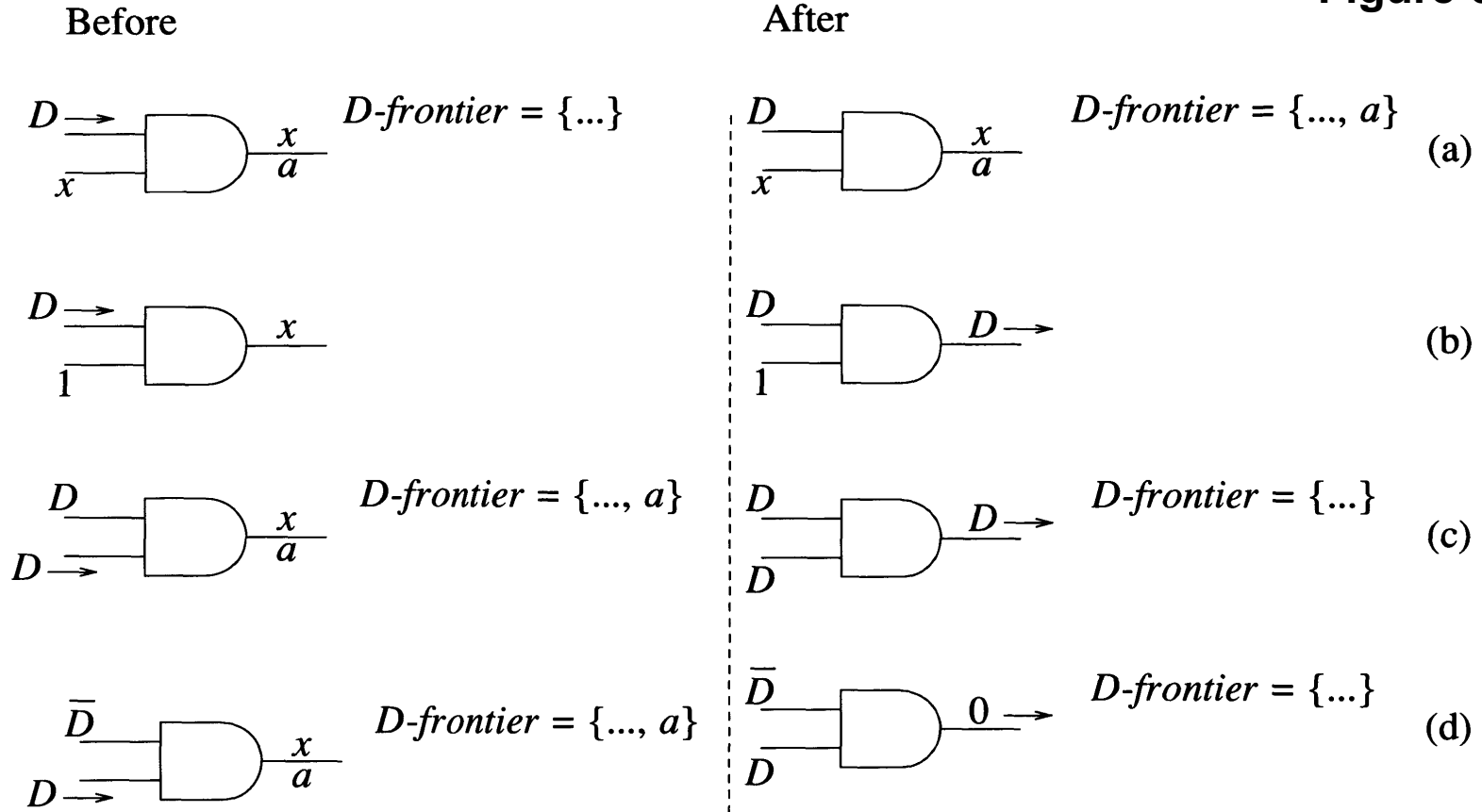


Figure 6.17 Unique D -Drive


- When only gate remains in the D -frontier.
- There is only one way to propagate D .

Before

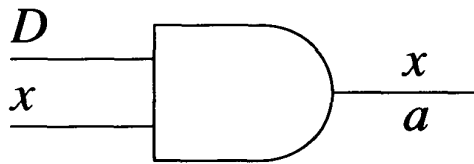

D -frontier = $\{a\}$


After

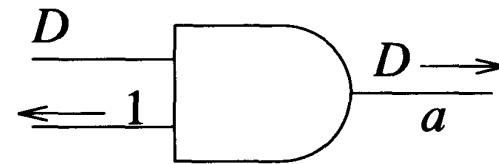

D -frontier = $\{ \}$

Figure 6.18 Future Unique D -drive

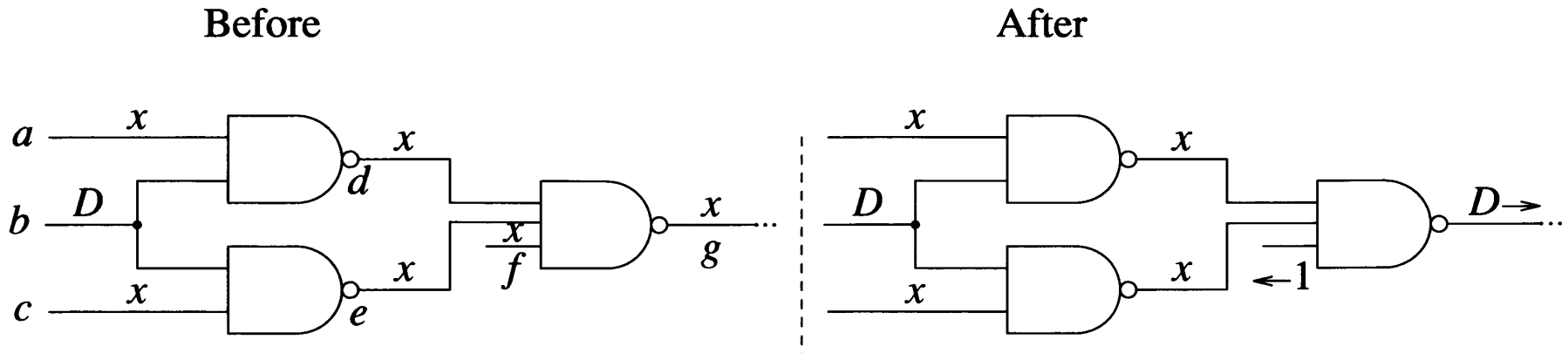- D -frontier = {d, e}
- Eventually we end up unique D -drive with gate g only



This type of propagations is *global implication*.

Reversing Incorrect Decisions

→ Assume that $a = 0$ failed *irrespective* of b and c
⇒ a must be 1 !


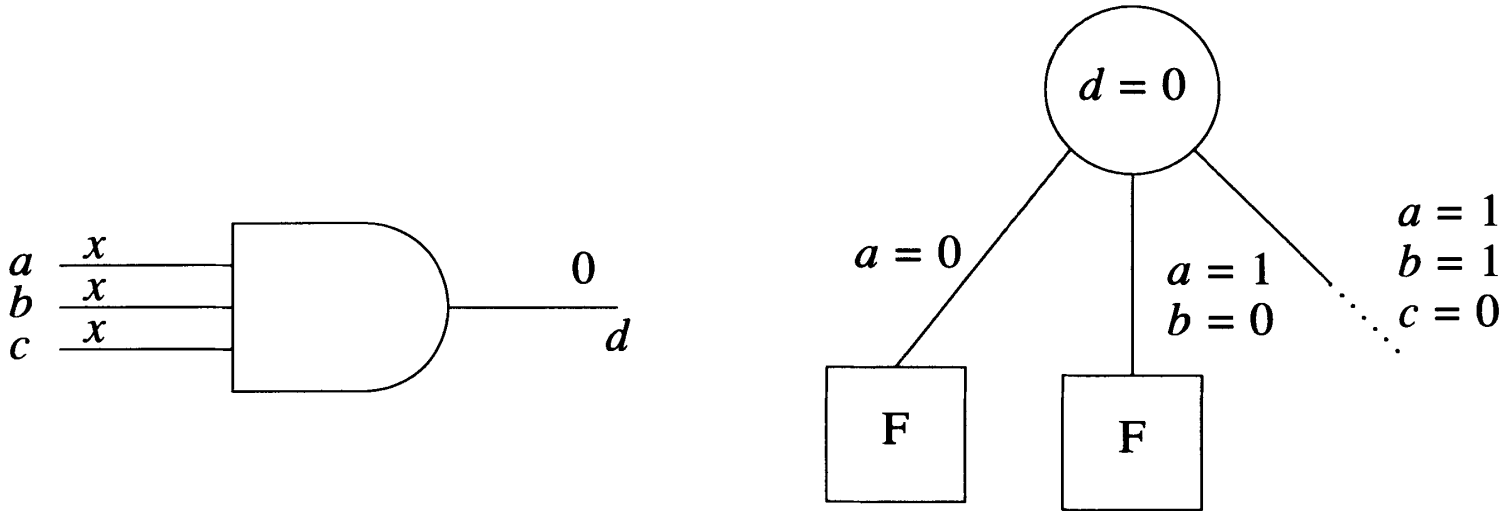


Figure 6.21 Reversing incorrect decisions

Look-Ahead in Error Propagation

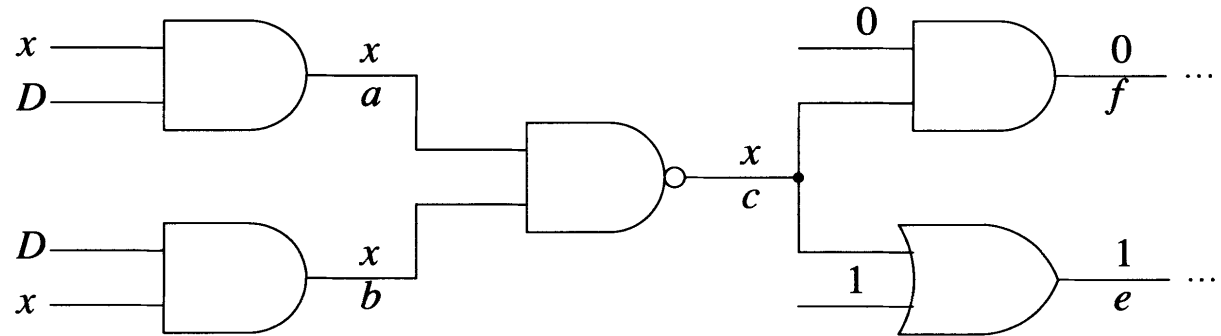- No matter how we propagate, D-frontier will be empty!
- Look-ahead: Error propagation is possible only if there is at least one ***x-path*** from gate G in D -frontier to at least one PO. (a necessary condition)
- X-paths used to avoid failed decisions.




D-Algorithm

- Ability to propagate errors on several reconvergent fanouts
- We assume error propagation is given priority over justification problems (simplifying assumption)
- “assign” means “add the value to the assignment queue”
- *Imply_and_check()* handles the assignments


```
1.  D-alg()
2.  begin
3.    if Imply_and_check() = FAIL then return FAIL
4.    if (error not at PO) then /* error propagation */
5.      begin
6.        if D-frontier =  $\emptyset$  then return FAIL
7.        repeat
8.          begin
9.            select an untried gate (G) from D-frontier
10.           c = controlling value of G
11.           assign c' to every input of G with input x
12.           if D-alg() = SUCCESS then return SUCCESS
13.         end
14.       until all gates from D-frontier have been tried
15.       return FAIL
16.     end
```

Continued...


```
17. /* error propagated to a PO */
18. if  $J\text{-frontier} = \emptyset$  then return SUCCESS
19. select a gate (G) from the  $J\text{-frontier}$ 
20.  $c$  = controlling value of G
21. repeat
22.   begin
23.     select an input ( $j$ ) of G with value  $x$ 
24.     assign  $c$  to  $j$ 
25.     if  $D\text{-alg}()$  = SUCCESS then return SUCCESS
26.     assign  $c'$  to  $j$  /* reverse decision */
27.   end
28.   until all inputs of G are specified
29.   return FAIL
30. end
```

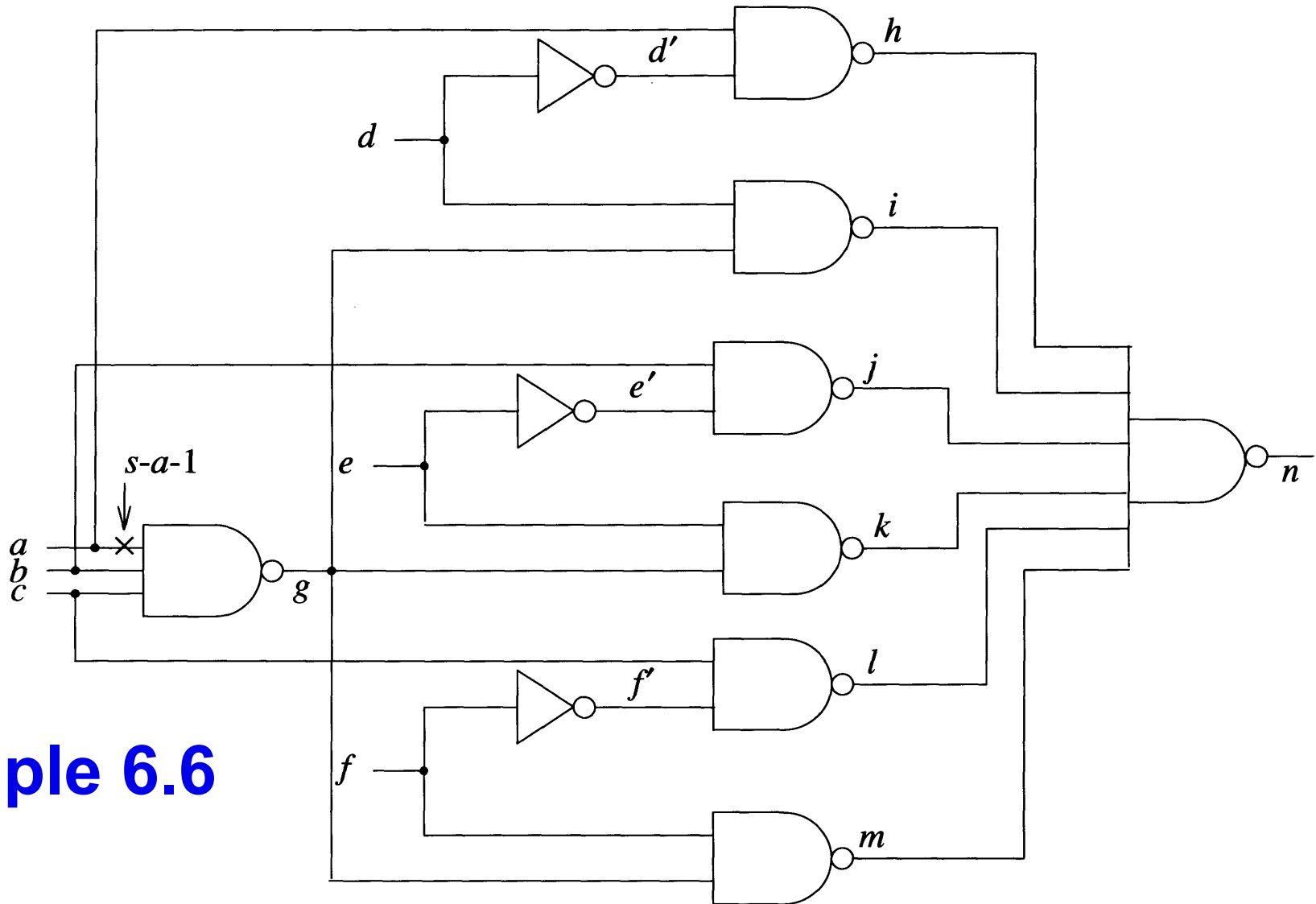


Example 6.6

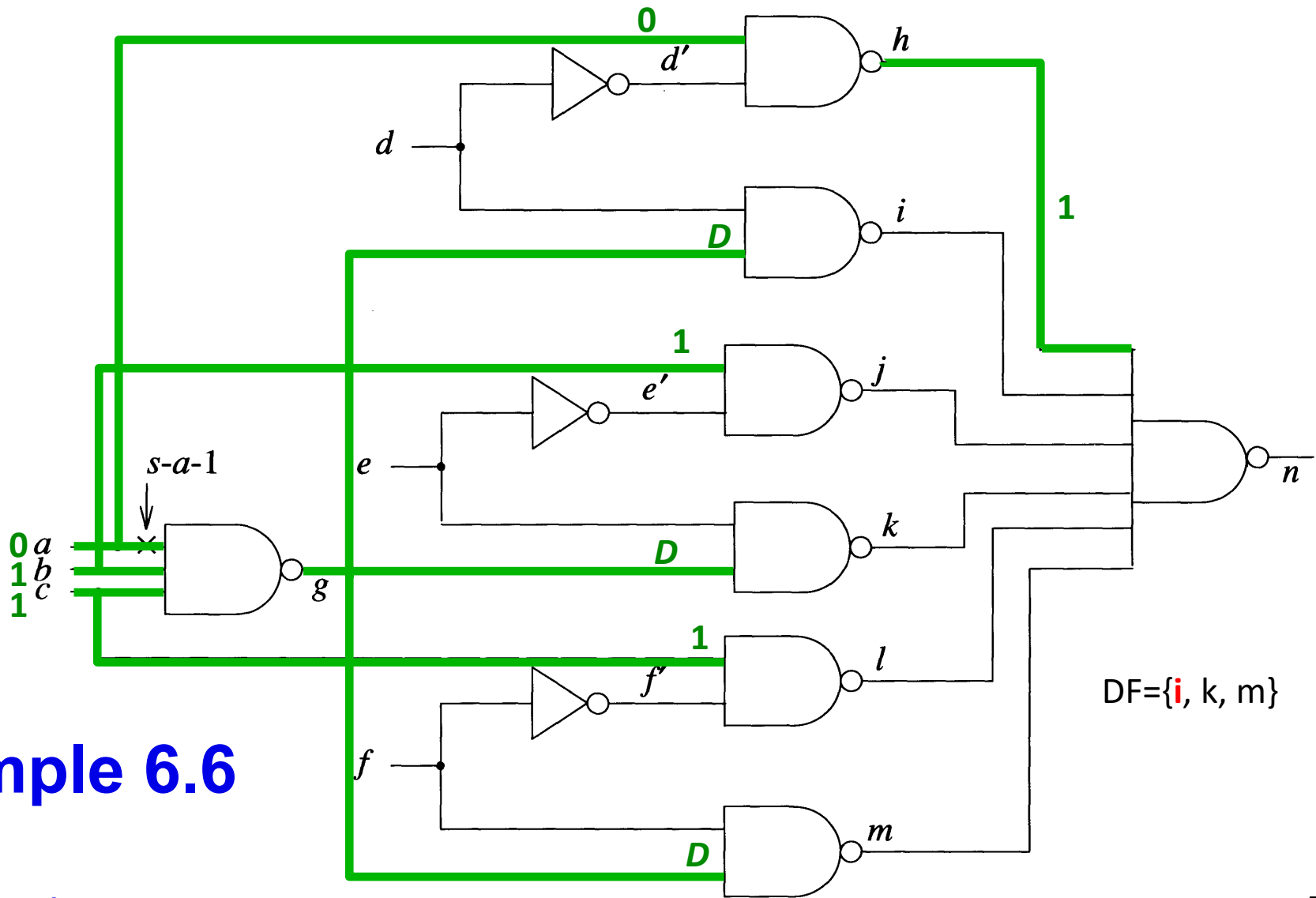


Example 6.6

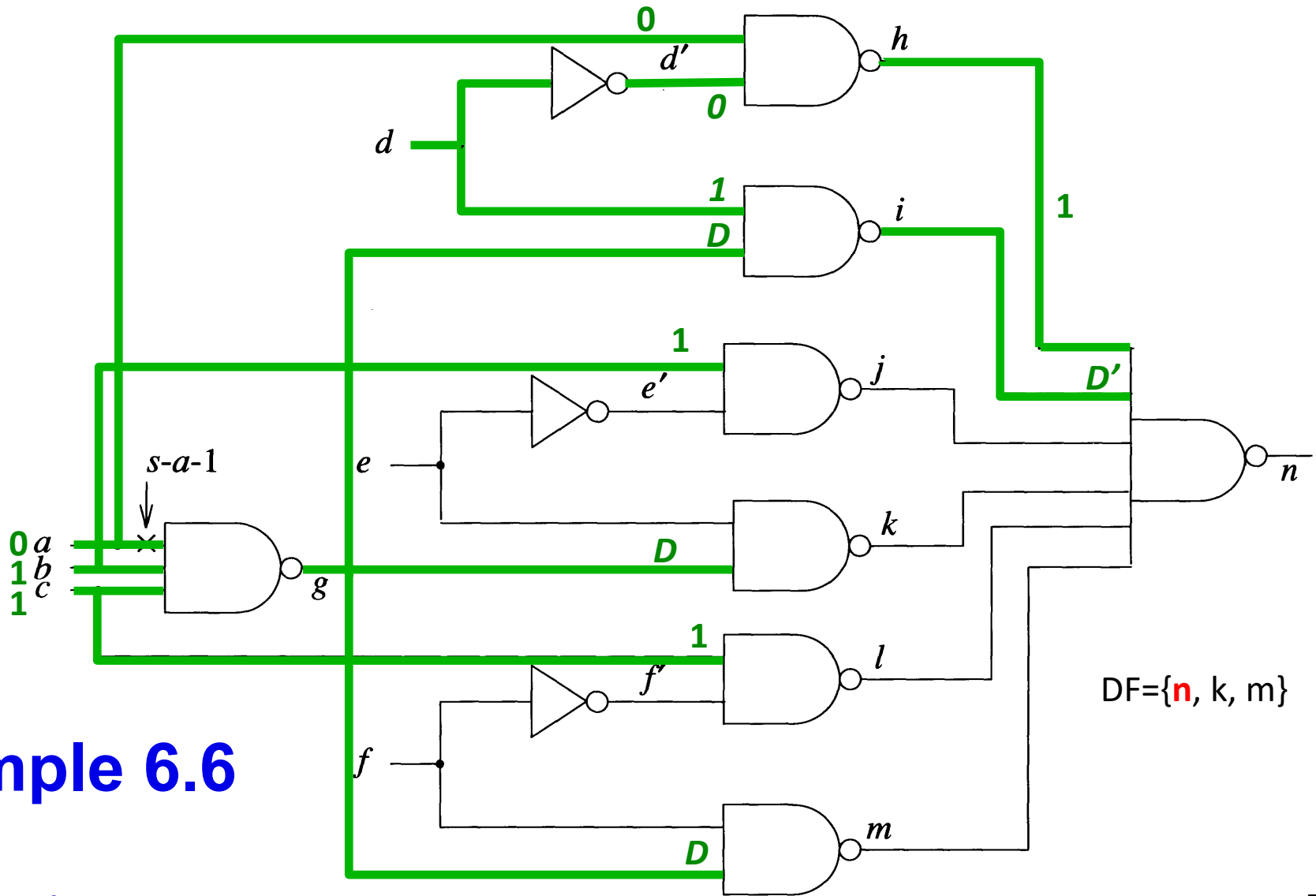


Example 6.6

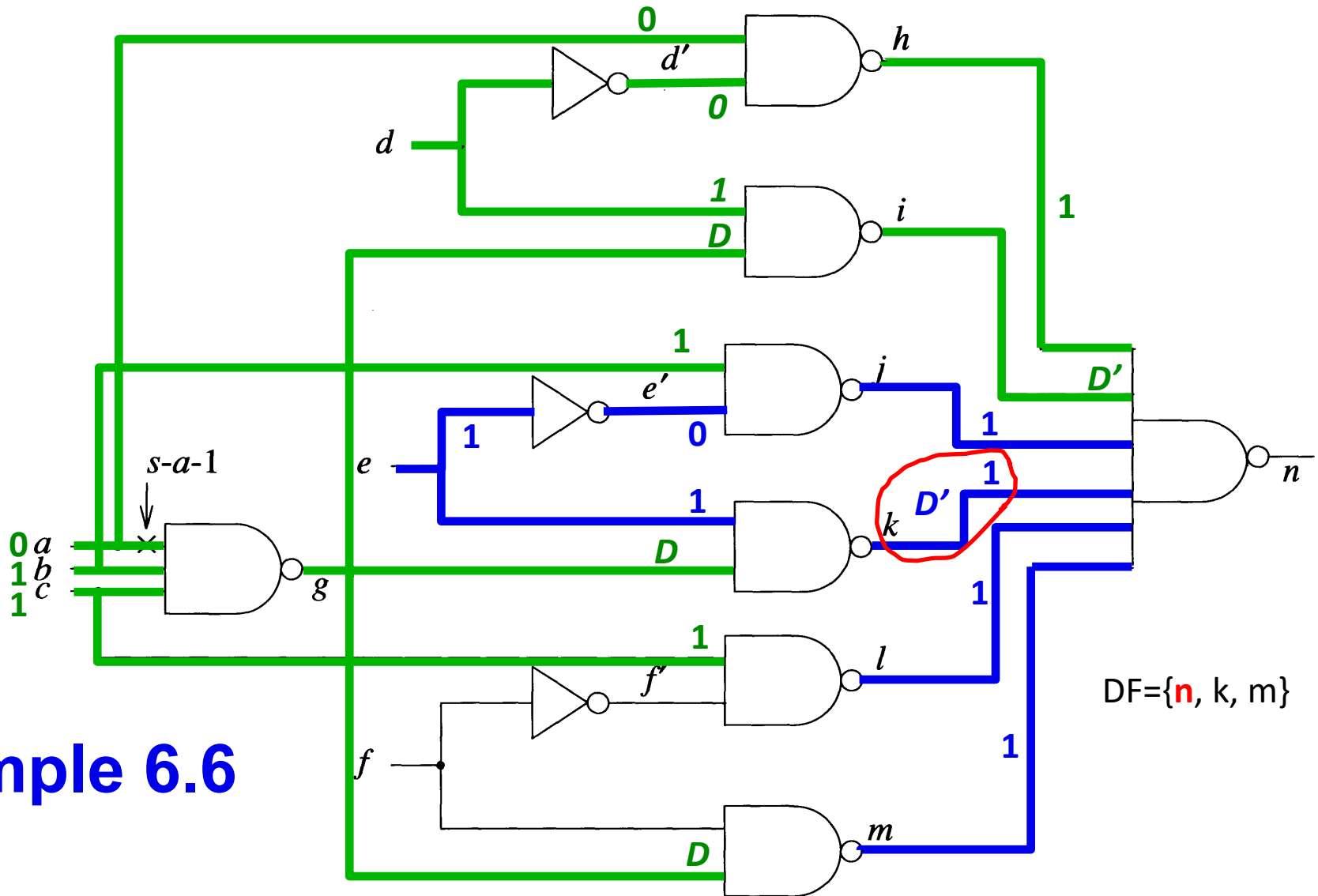


Example 6.6

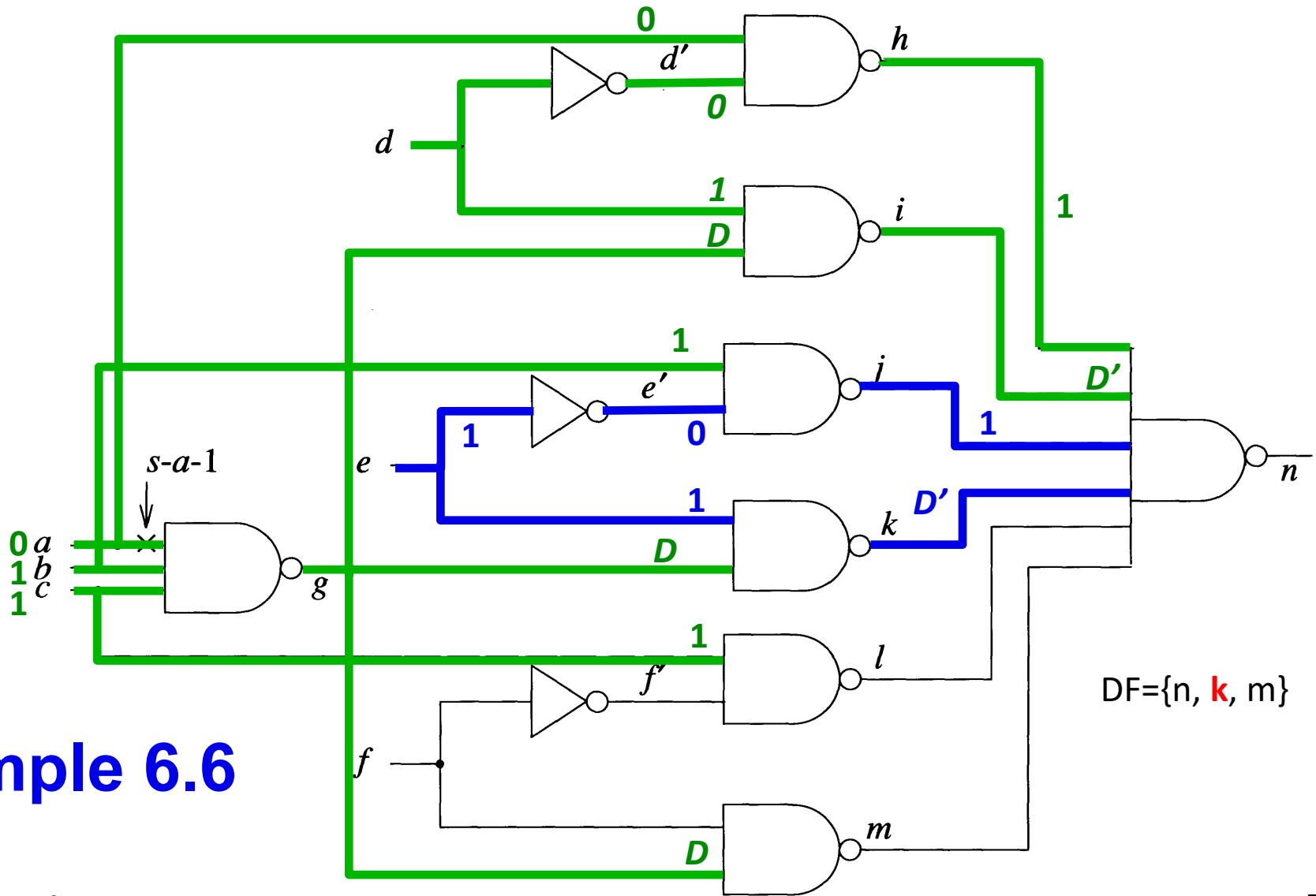


Example 6.6

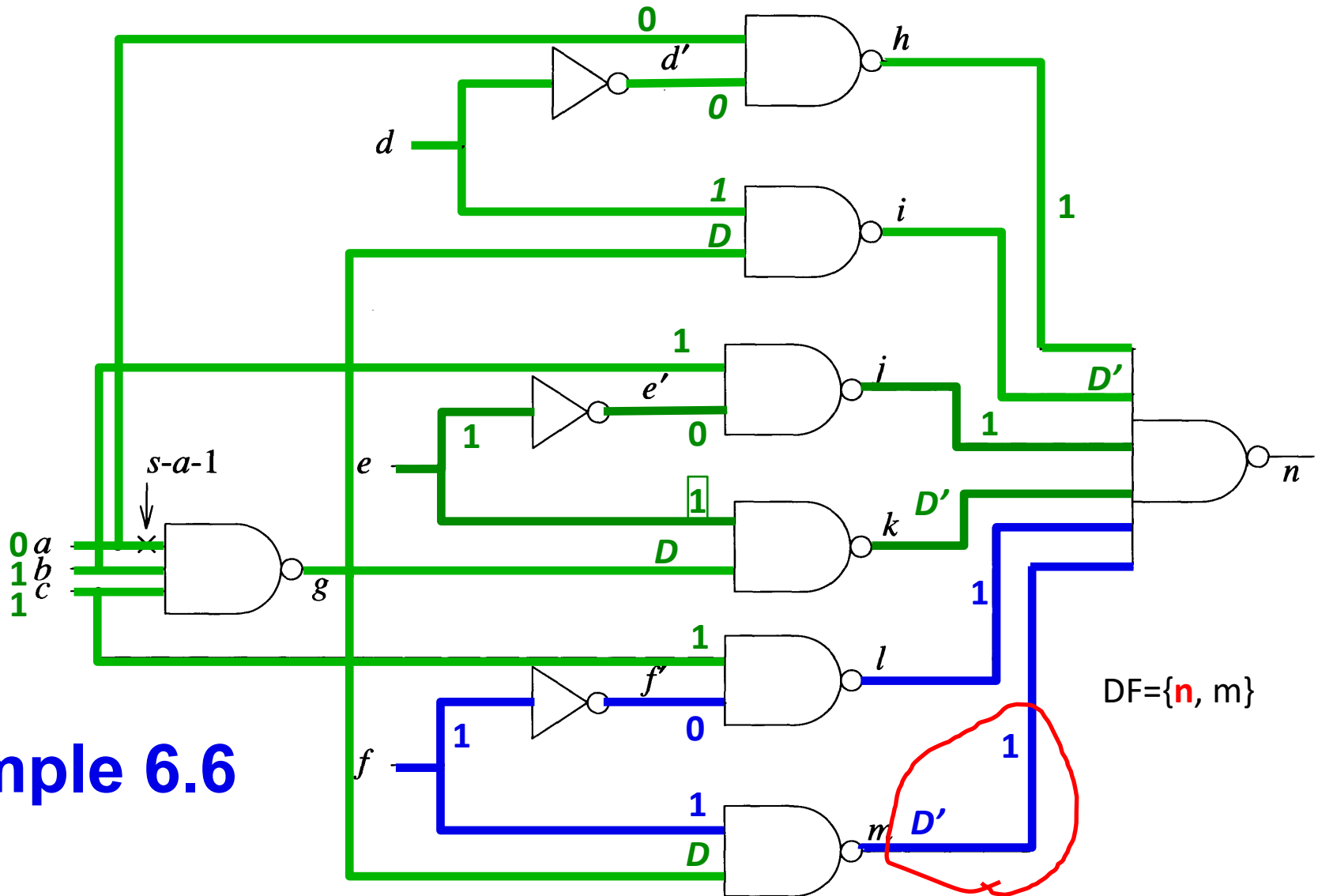

Example 6.6

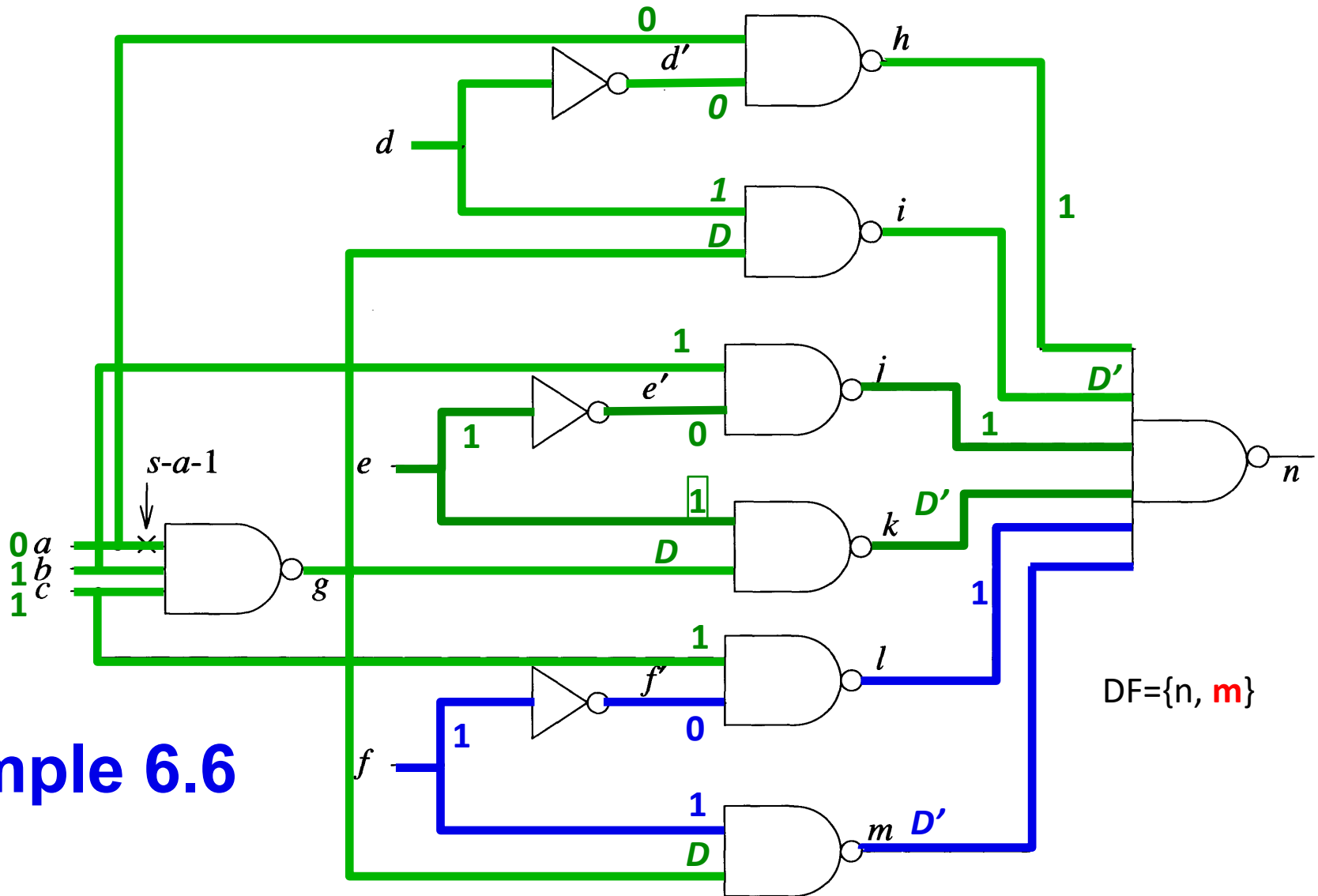


Example 6.6

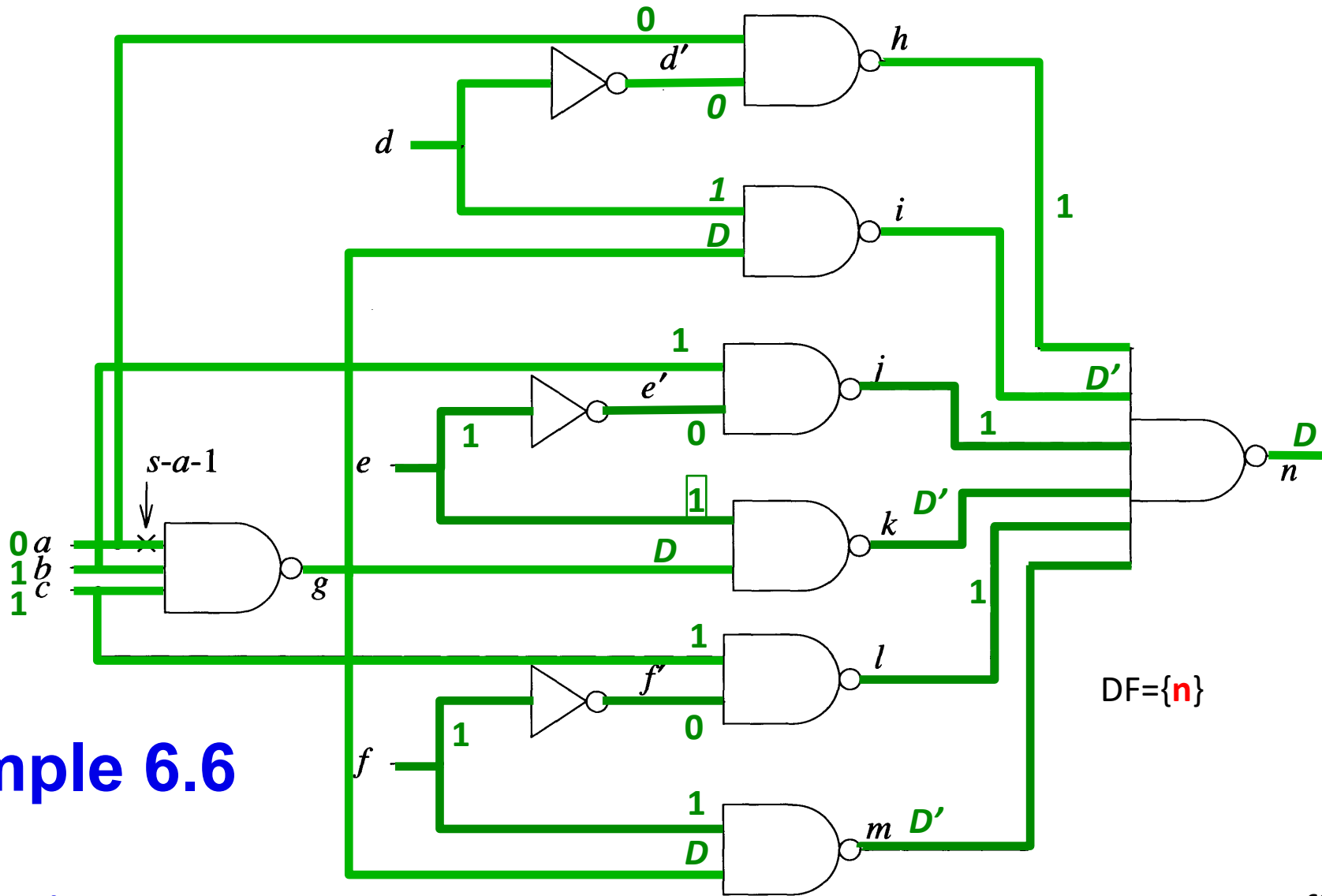

Example 6.6

Decisions	Implications	
	$a=0$ $h=1$ $b=1$ $c=1$ $g=D$	Activate the fault Unique D -drive through g
$d=1$	$i=\bar{D}$ $d'=0$	Propagate through i
$j=1$ $k=1$ $l=1$ $m=1$	$n=D$ $e'=0$ $e=1$ $k=\bar{D}$	Propagate through n Contradiction
$e=1$	$k=\bar{D}$ $e'=0$ $j=1$	Propagate through k
$l=1$ $m=1$	$n=D$ $f'=0$ $f=1$ $m=\bar{D}$	Propagate through n Contradiction
$f=1$	$m=\bar{D}$ $f'=0$ $l=1$ $n=D$	Propagate through m

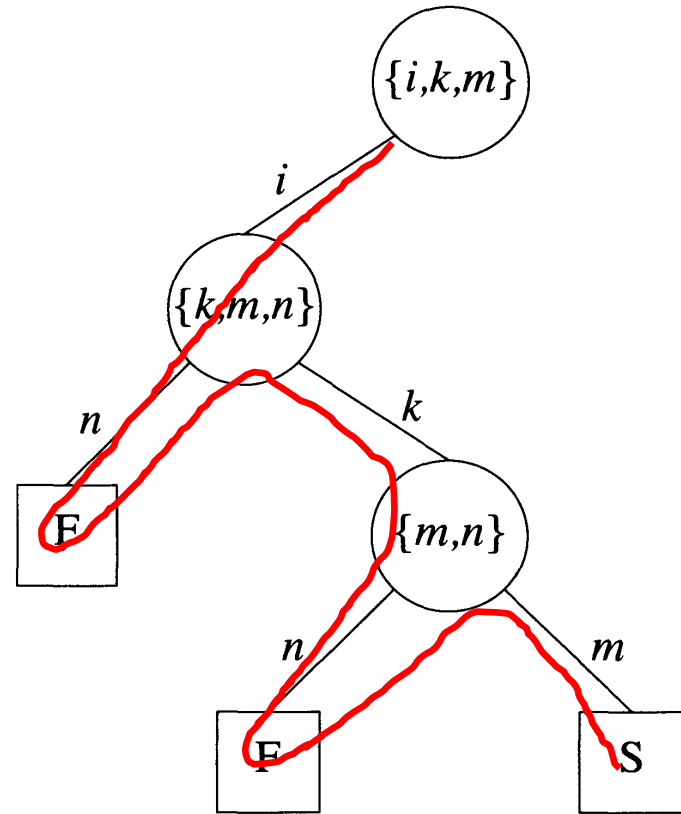

Each node is a D-frontier.

PODEM – *Path Oriented Decision Making*

- Direct search process
 - Decisions only about PI assignments.
 - In *D*-algorithm, decisions on PIs are indirect.
- Value v_k to be justified on line k
 - = *Objective* (k, v_k) to achieve via PI assignments.
- Backtracing of an objective
 - Maps a desired objective into a PI assignment
- Note that no values are assigned during backtracing

Backtrace (k, v_k)

/ map objective into PI assignment */*

begin

$v = v_k$

while k is a gate output

// Recursive generating

begin

// objectives until it reaches PI

$i =$ inversion of k

select an input (j) of k with value x

$v = v \oplus i$

$k = j$

end

/ k is a PI */*

return (k, v)

end

Backtrace – An Example

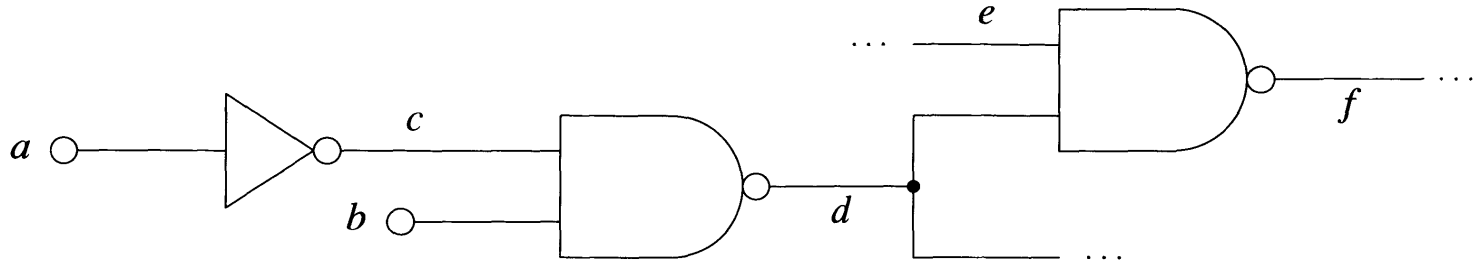


Figure 6.28

- Objective($f, 1$)
- First Backtrace ($f, 1$) call:
 - Path (f, d, b) is tried with $b=1$ as PI assignment
 - But $b=1$ is not enough to achieve objective ($f, 1$)
- Second Backtrace ($f, 1$) call:
 - Path (f, d, c, a) is tried with $a = 0$
 - Now with $a=0$, we can achieve *objective* ($f, 1$)

Selecting an Objective

Objective()

begin

/ the target fault is l s-a-v */*

if (the value of l is x) **then return** (l, \bar{v})

select a gate (G) from the *D-frontier*

select an input (j) of G with value x

c = controlling value of G

return (j, \bar{c})

end

Activate fault



Find the
necessary
inputs to
propagate fault

PODEM() // All lines are initialized to *x*

begin

if (error at PO) **then return SUCCESS**

if (test not possible) **then return FAILURE**

(k, v_k) = Objective()

(j, v_j) = Backtrace(k, v_k) / j is a PI */*

Imply (j, v_j) // 5-value simulation with PI assignments

if *PODEM()* = **SUCCESS** **then return SUCCESS**

/ reverse decision */*

Imply (j, \bar{v}_j)


if *PODEM()* = **SUCCESS** **then return SUCCESS**

Imply (j, x)

return FAILURE // *D-frontier becomes empty*

end

Objective:
 $d=1$

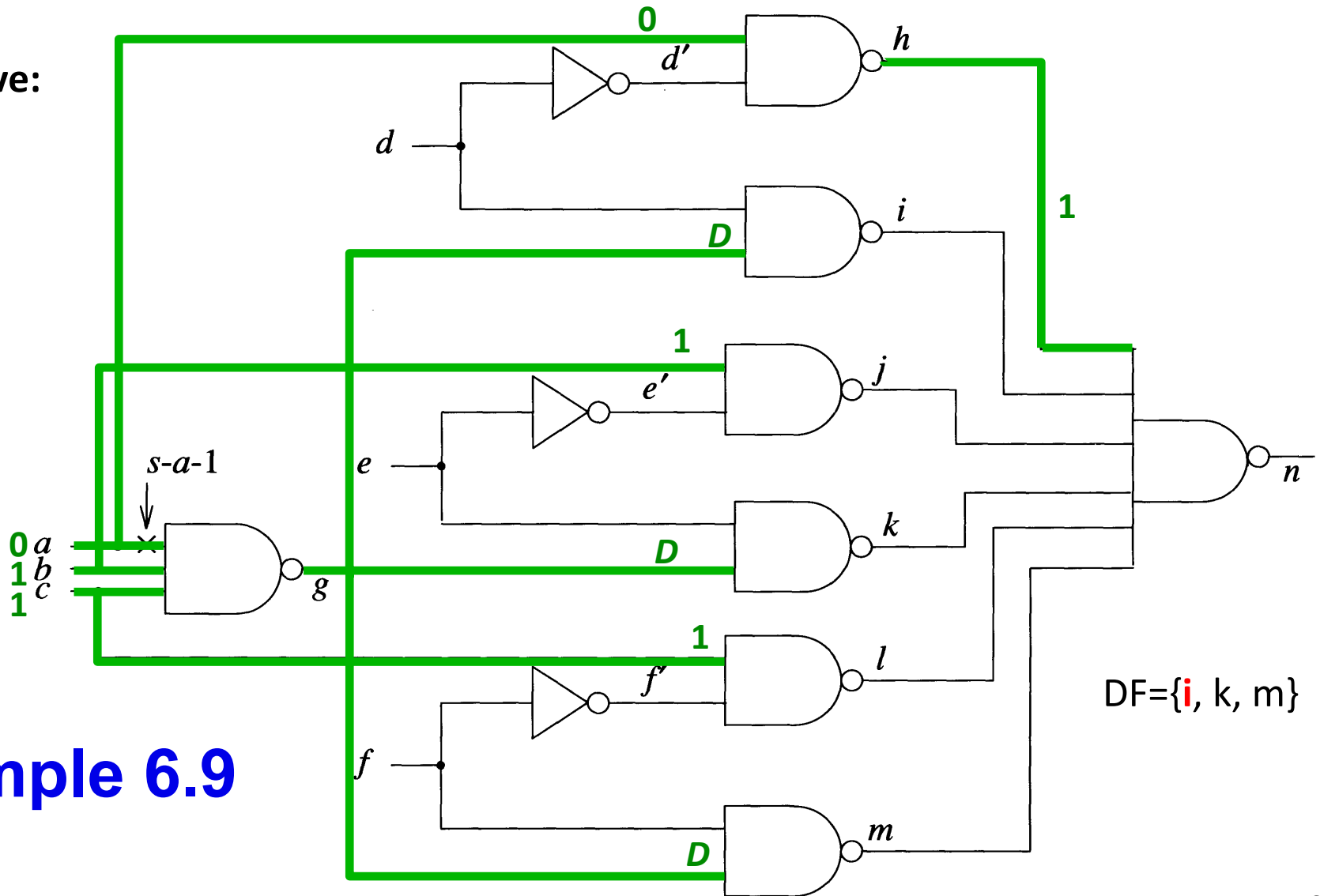


Example 6.9

Objective:


$k=1$

X-path check
Failed!

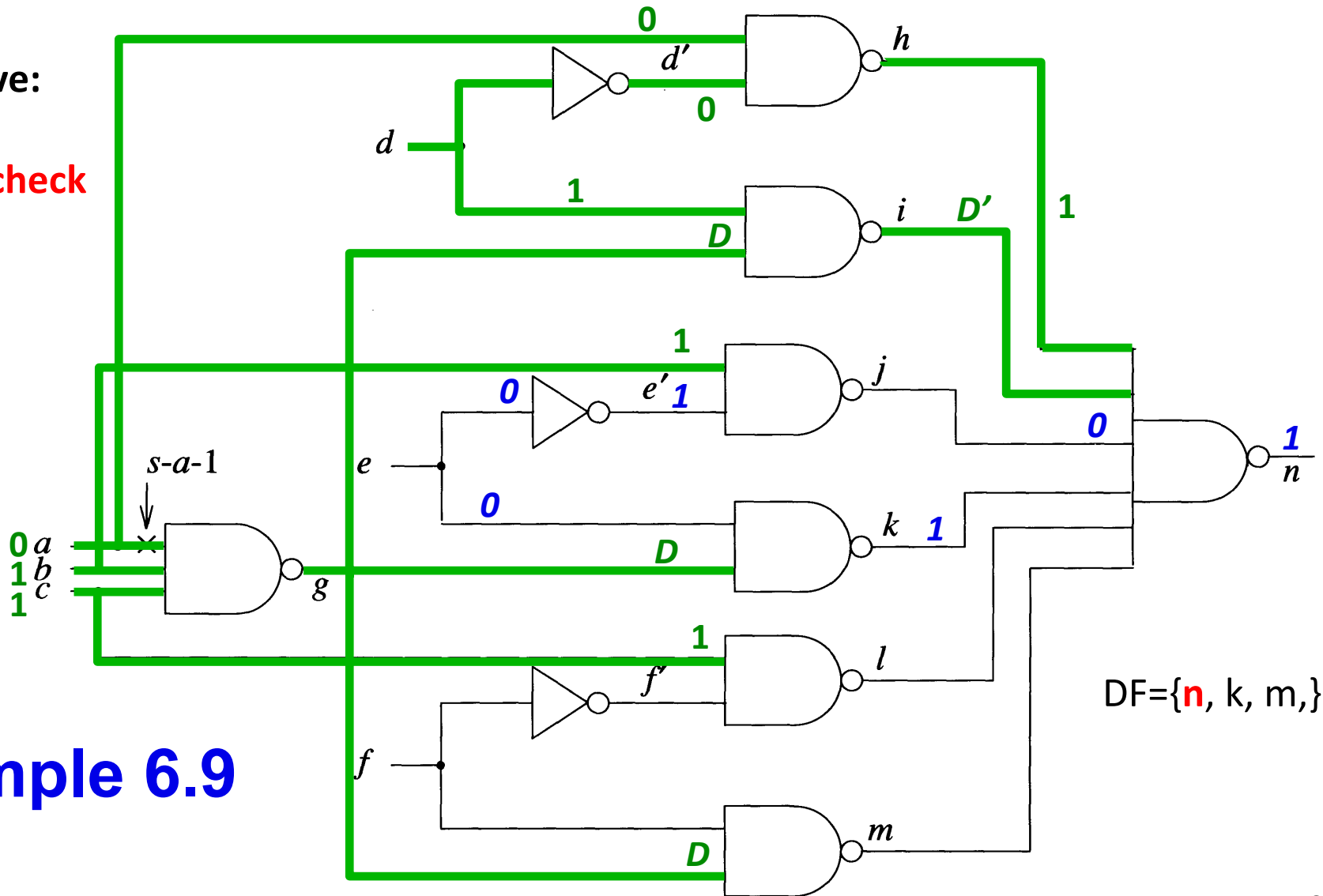


Example 6.9

Backtrack

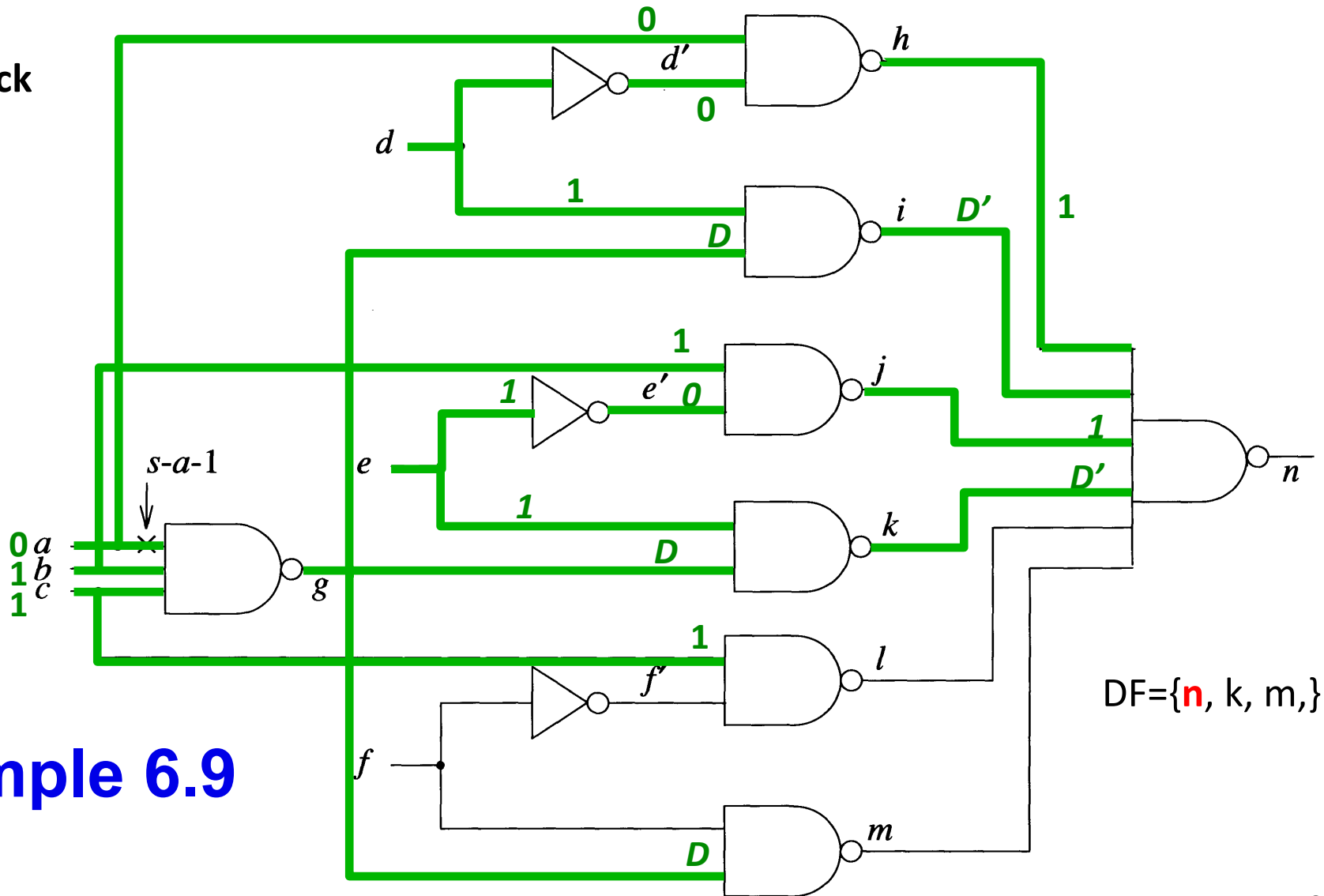


Example 6.9

Objective:
 $l=1$
 Success!

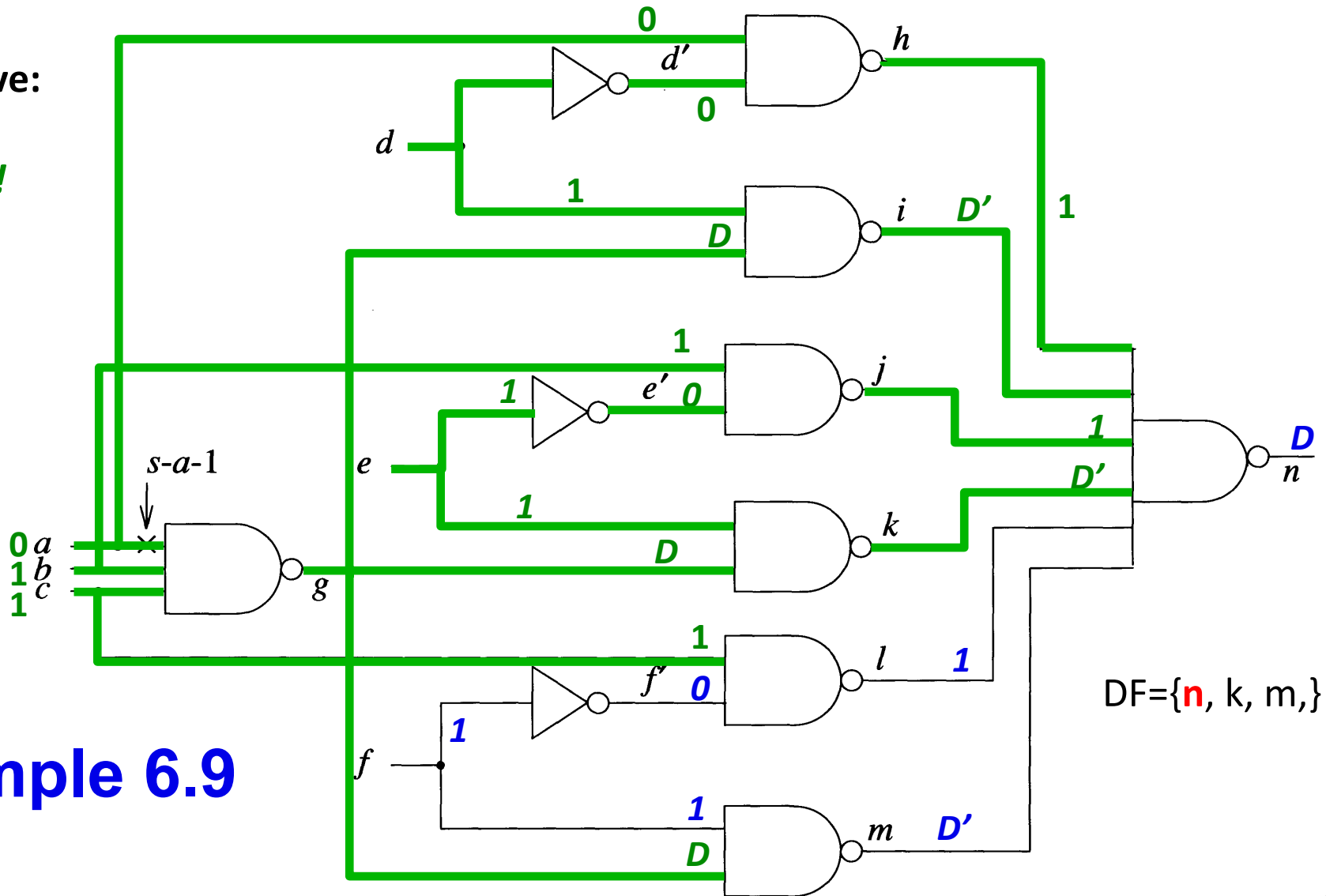

Example 6.9

Objective	PI Assignment	Implications	<i>D</i> -frontier	
$a=0$	$a=0$	$h=1$	g	<i>x</i> -path check fails reversal
$b=1$	$b=1$		g	
$c=1$	$c=1$	$g=D$	i,k,m	
$d=1$	$d=1$	$d'=0$ $i=\bar{D}$	k,m,n	
$k=1$	$e=0$	$e'=1$ $j=0$ $k=1$ $n=1$	m	
	$e=1$	$e'=0$ $j=1$ $k=\bar{D}$ $n=x$	m,n	
$l=1$	$f=1$	$f'=0$ $l=1$ $m=\bar{D}$ $n=D$		

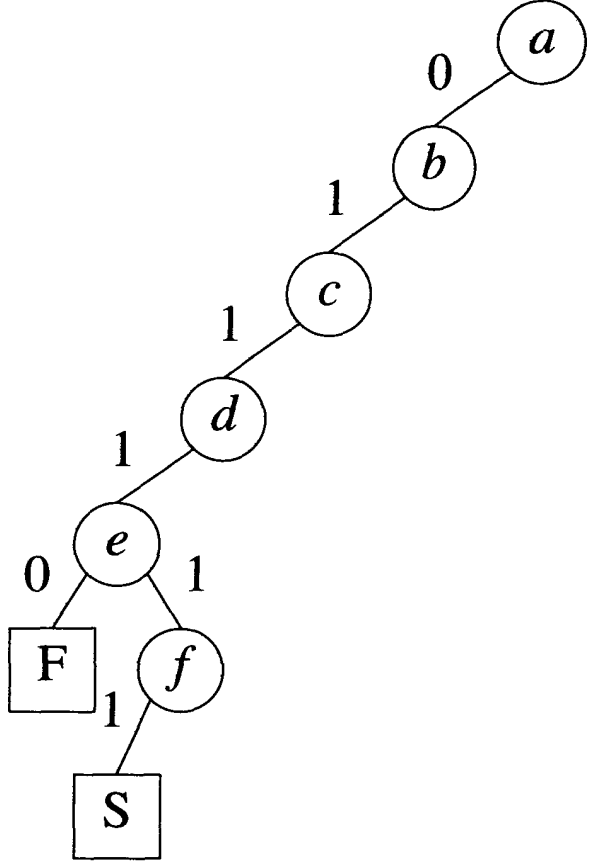

D-Algorithm vs PODEM

- PODEM does not need
 - Consistency check
 - *J*-frontier
 - Backward implication propagation
- Backtracking in PODEM is more simplified.
- Overall, PODEM is more efficient.

Selection Criteria

- Search process involves decisions
- Decisions on how to:
 - Select one of several unsolved problems: *fault propagation/line justification.*
 - Select one *possible* way to solve the selected problem: *several possible inputs to justify output 0 of AND gate.*

What are the selection criteria?

Some principles to speed up the search process.

Selection Criteria - Principles

- Among different unsolved problems, **first attack the most difficult one**
 - Thus avoid useless time spent in solving the easier problems when a harder one cannot be solved
- Among different solutions of a problem, **first try the easiest one**
- Difficulty is measured by *cost functions*.

Cost Functions

→ *Controllability measures*

→ Related to the Line Justification problem

→ Relative difficulty of setting a line to a value

Ex: select most difficult line-justification problem

→ *Observability measures*

→ Related to the Error Propagation problem

→ Relative difficulty of propagating an error from a line to a PO

Ex: select the gate from D -frontier whose input error is easiest to observe

Important: Must be relative measures and easy to compute.

Distance Based Cost Functions

- Any cost function should show that
 - PIs are the easiest to control
 - POs are the easiest to observe
- Therefore
 - Difficulty of controlling a line *increases* with its distance from PIs
 - ⇒ Line Level can be used as a controllability measure!
 - Difficulty of observing a line increases with its distance from POs
 - ⇒ Shortest distance of a line to PO can be used as a observability measure!

Main Drawback: Does not take into account the logic function

Controllability Measure $C(l)$

For every signal we want to compute:

$C0(l)$ = Relative difficulty of setting line l to 0

$C1(l)$ = Relative difficulty of setting line l to 1

Assume we know $C0$ and $C1$ costs of all inputs of the AND gate,


To set X to 0:

$$C0(X) = \min \{C0(A), C0(B), C0(C)\}$$

To set X to 1:

$$C1(X) = C1(A) + C1(B) + C1(C)$$

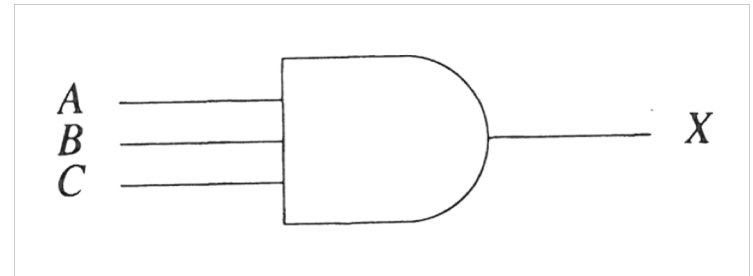assuming A, B, C are independent (i.e., do not depend on common PIs)



We can develop similar cost functions for other gates. OR gate?

Controllability Measure Computation


- Set C_0 and C_1 for every primary input to 1
- Compute C_0 's and C_1 ' level by level
 - Cost are computed only after predecessor costs are known
- Costs can be computed in one forward traversal
- Linear in number of gates

Issues

If inputs of a gate are not independent, it can lead to incorrect results

In (a) cost of controlling B and C is the same

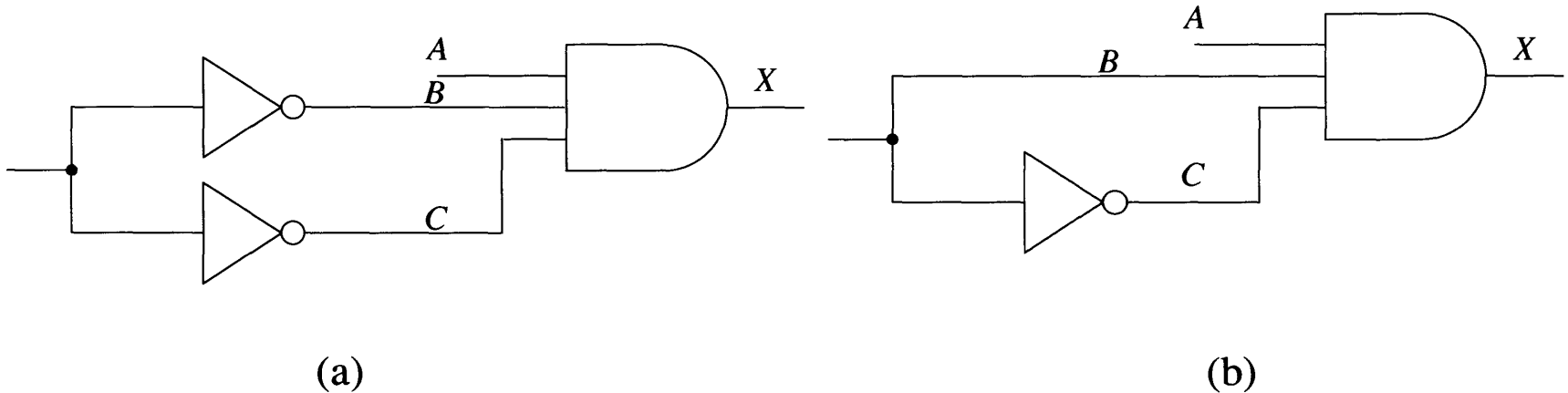
In (b) B and C cannot be set to 1 simultaneously, so $C1(X)$ should show that setting $X=1$ is impossible



Observability Measure $O(I)$

Cost of observing the input A?

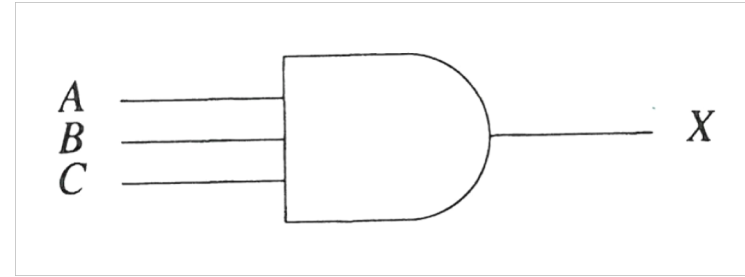- We must set B and C to 1
- Propagate error from X to a PO




$$O(A) = C1(B) + C1(C) + O(X) \dots \text{Eq (3)}$$

Assuming controlling $B=1$, $C=1$, and propagating $\text{Err}(X)$ to PO are independent problems

What about OR gate?

Observability of a Stem X

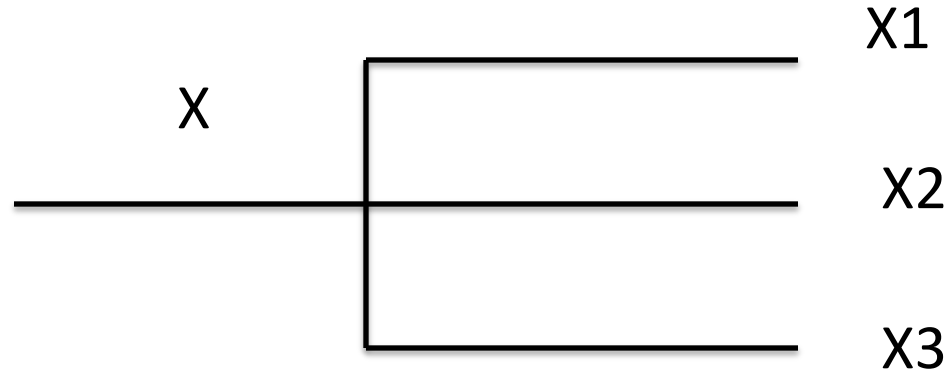

$$O(X) = \min \{ O(X1), O(X2), O(X3) \} \quad \dots \text{Eq (4)}$$


Assuming single path propagation is possible

Observability Measure Computation


- Set observability cost of every PO to 0
- Compute observabilities level by level backward manner using eq 3 and 4.
 - Cost are computed only after successor costs are known
- Costs can be computed in one backward traversal
- Linear in number of lines
- Assume controllability measure is known.

Fanout-Based Cost Functions

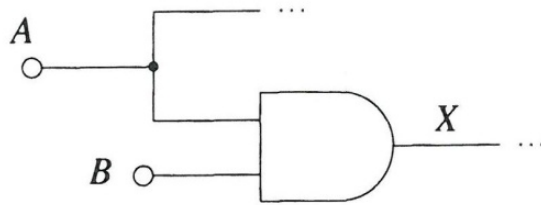- Reconvergent fanout makes TG difficult.
- A line with fanout has high potential causing conflict.



Setting $B = 0$ is better than $A = 0$

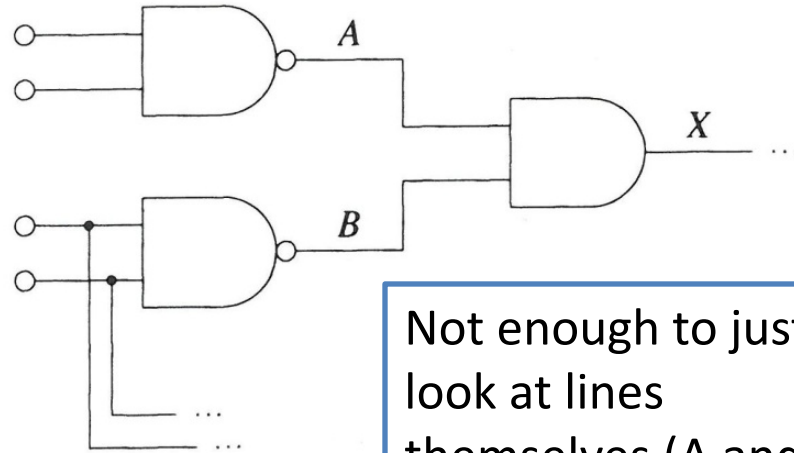

Not enough to just look at lines themselves (A and B)!!

Fanout-Based Controllability Measure

→ $C(l)$ depends on

→ Fanout count of l

→ Fanout count of predecessors of l

$$C(l) = \sum_i C(i) + f_l - 1 \quad (6.5)$$

Where f_l is the fanout count of l

A line l with $C(l) = 0$ means it does not depend on any fanout lines.

Example


$$C(l) = \sum_i C(i) + f_l - 1$$

$$C(A) = 0$$

$$C(B) = 2$$

$$C(X) = 2$$

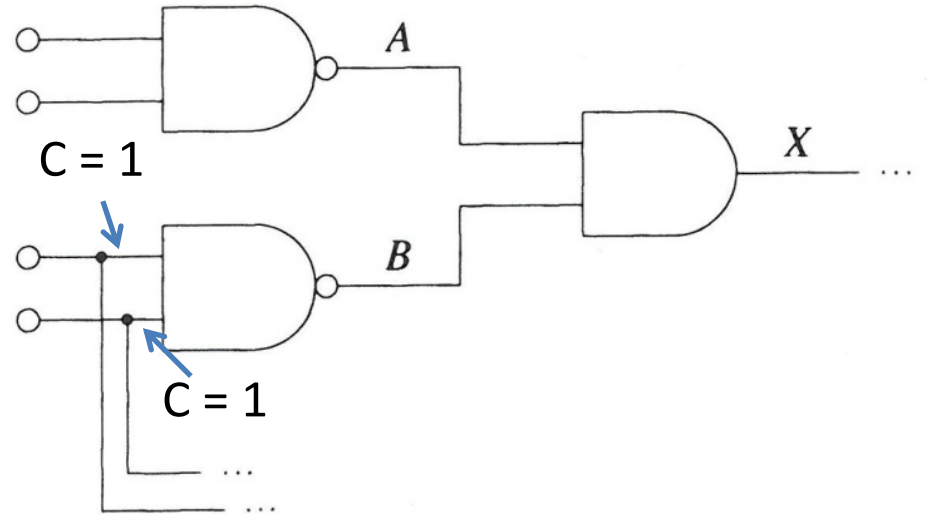Therefore, select $A=0$
to justify $X=0$.



$C0(l)$ and $C1(l)$ – More Accurate Cost Func.

→ Eq (6.5) does not distinguish between setting a line to 0 and to 1

For the AND gate we have:

$$C0(l) = \min \{C0(i)\} + f_l - 1$$

and

$$C1(l) = \sum_i C1(i) + f_l - 1$$

What about OR gate?

Example

$$C0(l) = \min \{C0(i)\} + f_l - 1$$


$$C(l) = \sum_i C(i) + f_l - 1$$

$$C0(A) = C1(A) = 1$$


$$C0(B) = C1(B) = 0$$

$$C0(X) = 0,$$

$$C1(X) = 1.$$

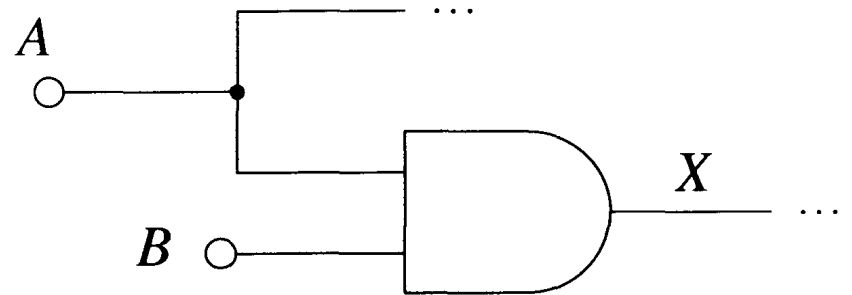

Side Effects – Example

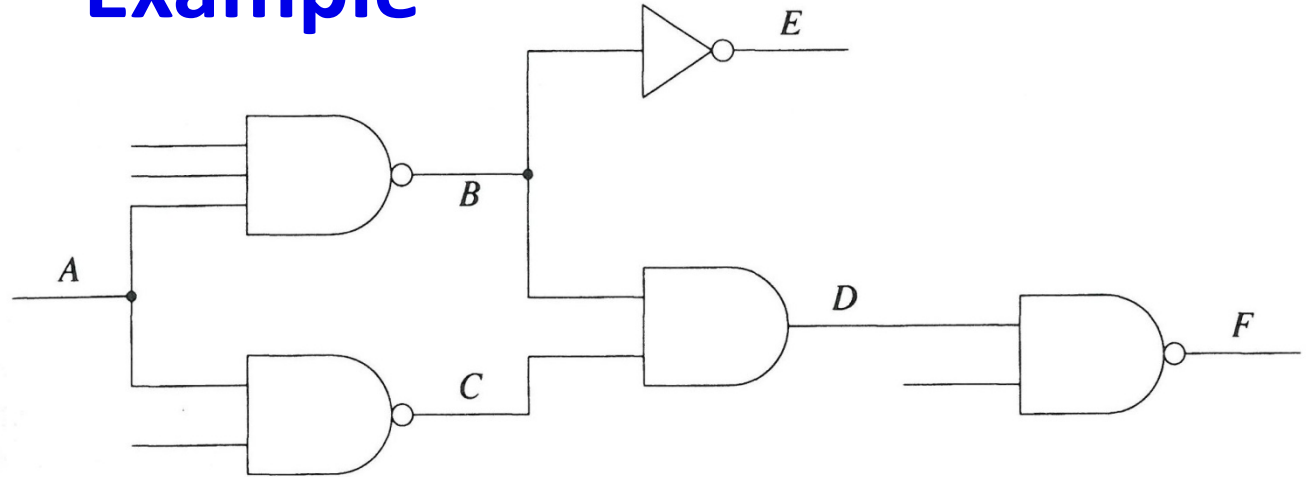


- $C0(A)$ and $C1(A)$ both have corrective terms =1
- $A = 0$ has greater potential of conflicts than $A = 1$
 - $A = 0$ results in B, C, D, E being set to binary values
 - Less x-paths for error propagation.

Side Effects Cost Function

- Side-Effects Cost Functions: $CS0(l)$ and $CS1(l)$ to account for relative potential for conflicts caused by setting l to 0 and 1
- Computed by simulating $l = v$ ($v \in \{0, 1\}$) in a circuit initialized with all- x state, and then
 - A gate whose output is set to a binary value increases cost by 1
 - A gate with n inputs whose output remains at x but which has m inputs set to a binary value, increases the cost by m/n

Side Effect Function – Example

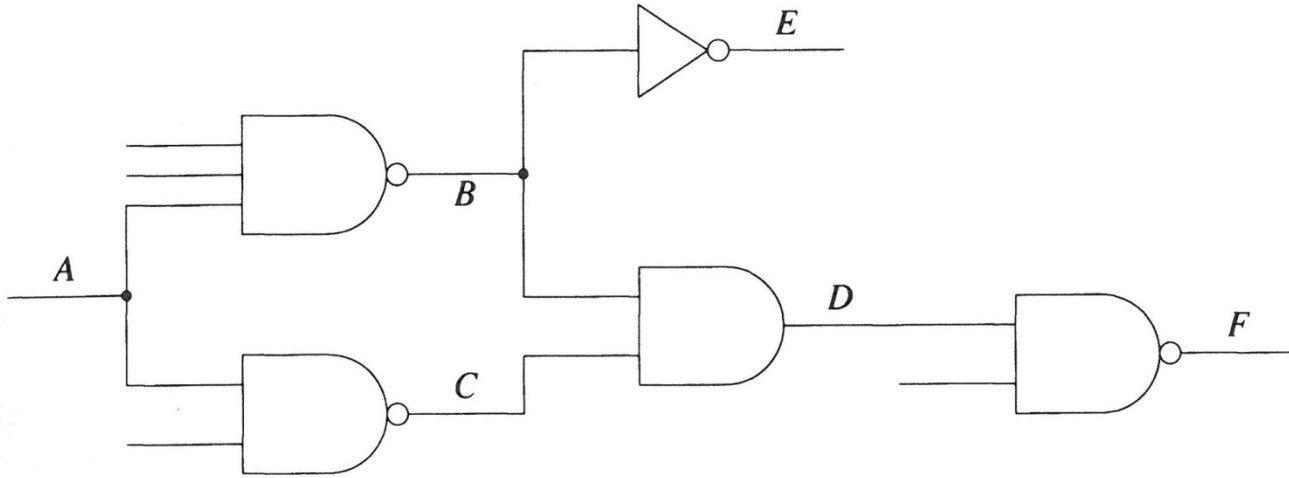

- $CS0(A) = 4(1/2)$
- $CS1(A) = (1/3) + (1/2) = 5/6$

Cost Functions with Side-Effects

$$C0(l) = \min \{C0(i)\} + CS0(l)$$

$$C1(l) = \sum_i C1(i) + CS1(l)$$

- Require circuit simulation after assigning l to 0 or 1
 - Cause additional complexity

Cost Functions: Summary


- Complexity of cost function computation must be low.
- Cost functions are based heuristics.
- Dynamic cost functions may lead to better performance.

Backup

Fault Independent ATG

- Fault-oriented algorithm targets a given fault and generate a test vector
- Fault-independent algorithm's goal:
 - Derive a set of test that detect a large set of SSFs w/o targeting individual faults
- CPT -- Half of the SSFs on a path critical in a test t are detected by t
 - ⇒ Generate tests that produce **long** critical paths
 - ⇒ Critical path TG algorithm

Critical Paths – Basic Concept

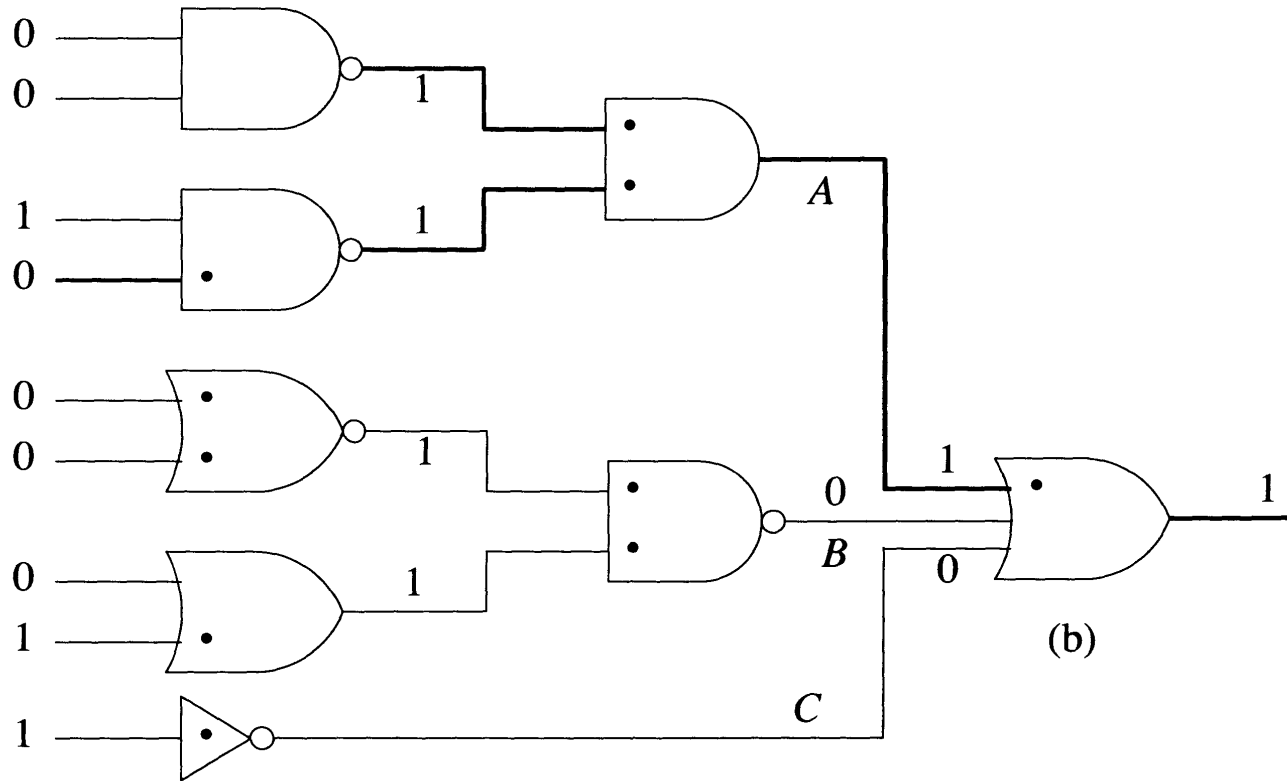

The input vector detects output s-a-0 fault and other faults on the critical path

Critical-path TG Algorithm

Basic Steps

1. Select a PO and assign it a critical 0-value or 1-value (Recall that a PO is always critical)
2. Recursively justify the PO value, trying to justify any critical value on a gate output by critical values on the gate inputs

Line Justification – 3 Input AND gate

By Primitive Cubes

<i>A</i>	<i>B</i>	<i>C</i>	<i>Z</i>
1	1	1	1
0	<i>x</i>	<i>x</i>	0
<i>x</i>	0	<i>x</i>	0
<i>x</i>	<i>x</i>	0	0


(a)

By Critical Cubes


<i>A</i>	<i>B</i>	<i>C</i>	<i>Z</i>
1	1	1	1
0	1	1	0
1	0	1	0
1	1	0	0

(b)

Critical-path TG - Example

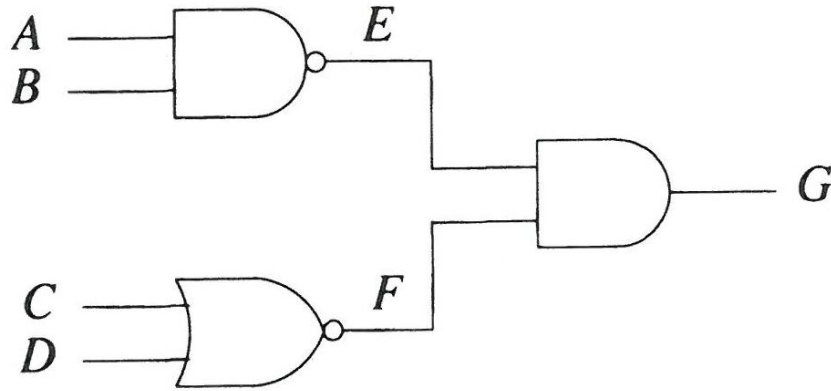





(a)

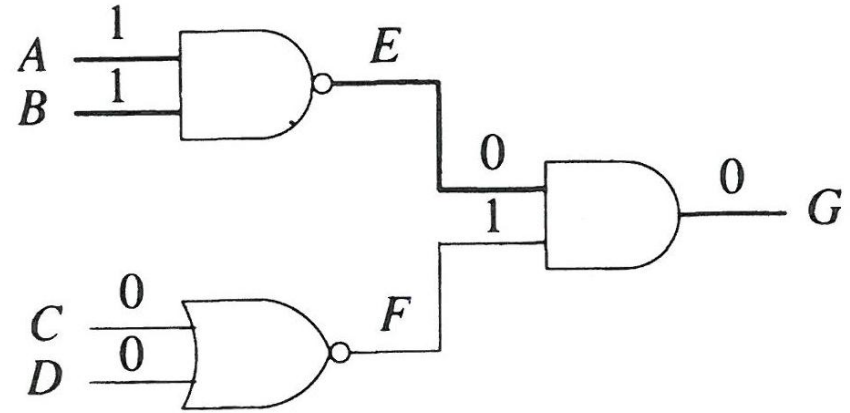

(b)

What SSFs can be detected by this input vector?

Critical-path TG – Example ...contd.

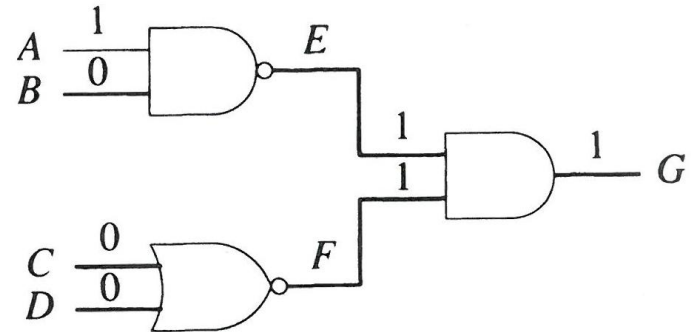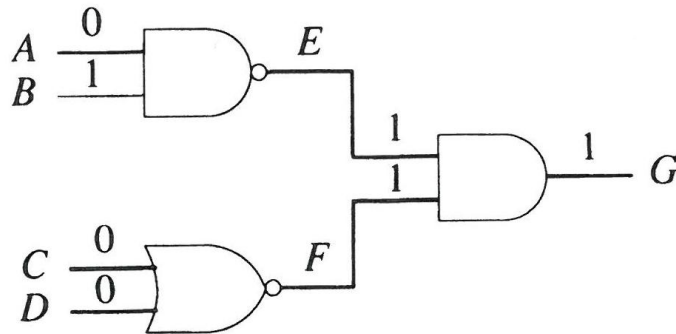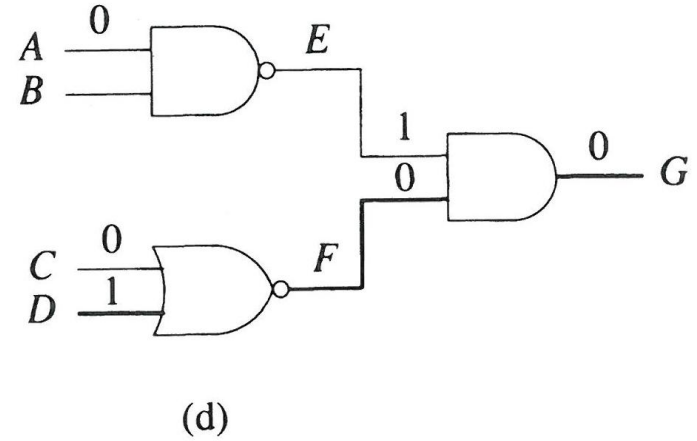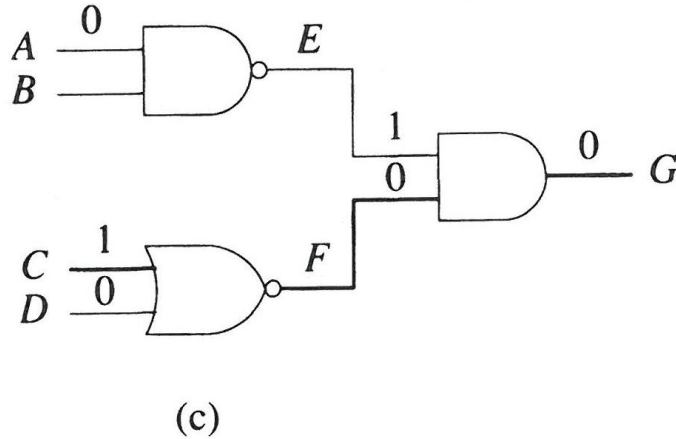

```

CPTGFF()
begin
  while (Critical ≠ ∅)
    begin
      remove one entry (l, val) from Critical
      set l to val
      mark l as critical
      if l is a gate output then
        begin
          c = controlling value of l
          i = inversion of l
          inval = val ⊕ i
          if (inval =  $\bar{c}$ )
            then for every input j of l
              add (j,  $\bar{c}$ ) to Critical
            else
              begin
                for every input j of l
                  begin
                    add (j, c) to Critical
                    for every input k of l other than j
                      Justify (k,  $\bar{c}$ )
                      CPTGFF()
                    end
                  end
                return
              end
            end
          end
        end
      /* Critical = ∅ */
      record new test
      return
    end
  end
end

```

- Critical Path TG Fanout Free
- To generate complete test set for a FF circuit whose PO is Z,

add (Z, 0) to *Critical*
 CPTGFF()
 add (Z, 1) to *Critical*
 CPTGFF()

Decision Tree

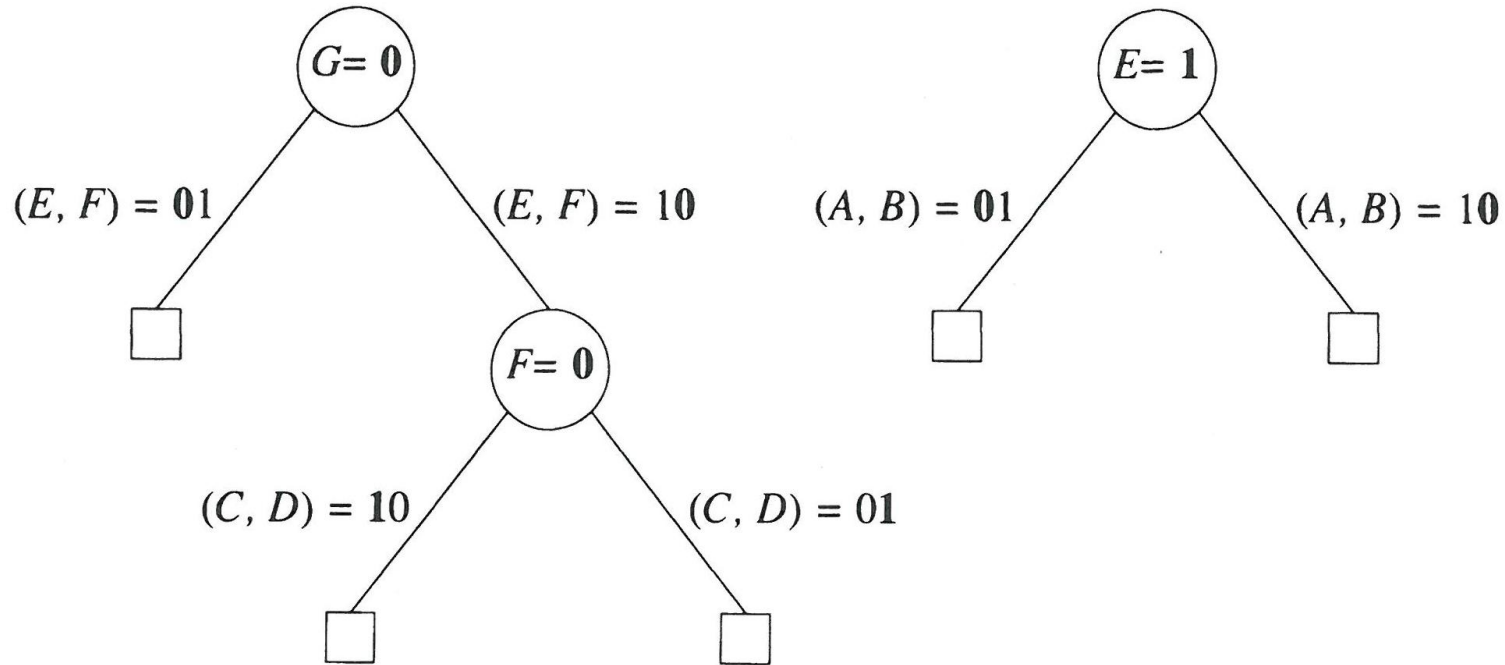



Figure 6.47 Decision trees for Example 6.12

The number of terminal nodes equals the number of tests generated.

ATG for SSFs in Sequential Circuits

- TG using Iterative Array Model
 - Extends TG methods of combinational circuits to sequential circuits
- Transform Synchronous sequential circuit into an iterative combinational array.
 - Unroll the circuit for k times.
 - One cell in the array \rightarrow *time frame*
- Assume all FFs are driven by a fault-free clock line.
- An input vector for the array is a sequence of k input vectors for the synchronous circuit.

Synchronous State m/c model

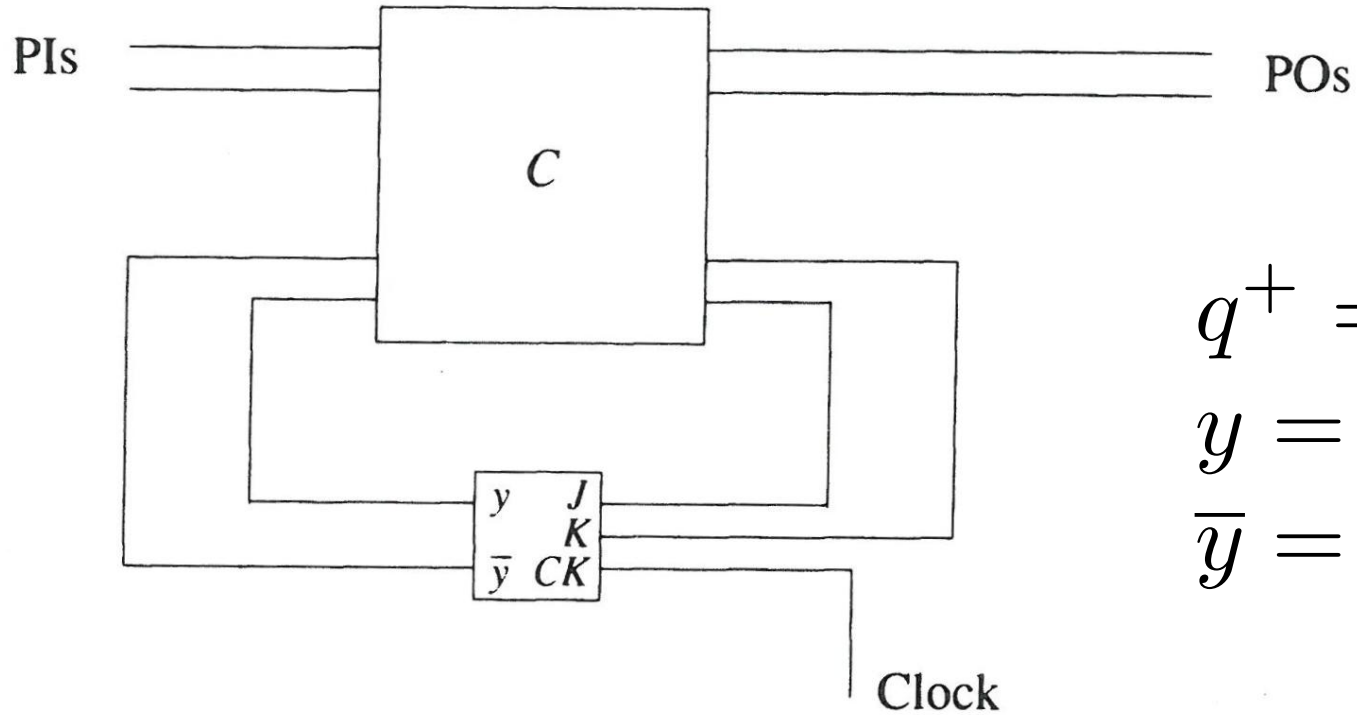


$$q^+ = J\bar{q} + \bar{K}q$$

$$y = q$$

$$\bar{y} = \bar{q}$$

Model for one time frame

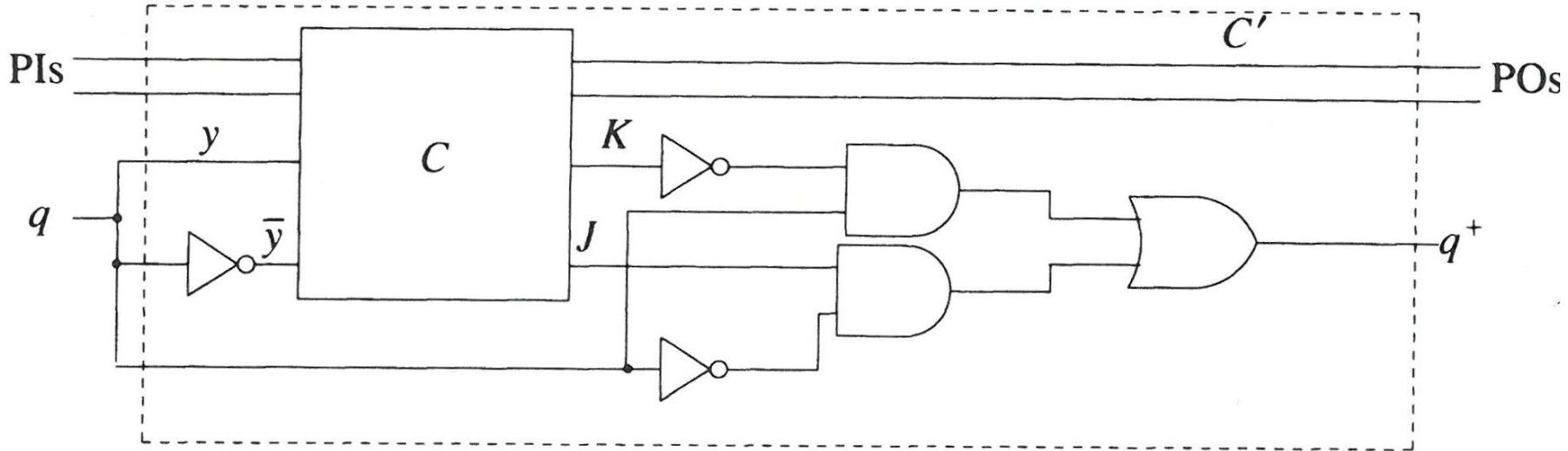

- Since the circuit is same for every frame, we do not have to generate n copies
- However, we should separately maintain signal values of each time frame

Some observations

- C' is a combinational circuit, so any combinational TG algorithm (D, PODEM, CPTG, etc.) can be applied
- A test vector t for C' , may specify PI and q values
 - q values must be justified in previous timeframe
- t may not propagate an error to a PO but to a q+ variable
 - Error must be propagated to next time frame
- In general, search process
 - May span multiple time frames
 - Going backward and forward in time

Fault Propagation

- Target fault can be present in every time frame!
 - Error value (D or D') may propagate onto the faulty line itself

Value propagated onto line l	Fault of line l	Resulting value of line l
D	$s-a-0$	D
D	$s-a-1$	1
\overline{D}	$s-a-0$	0
\overline{D}	$s-a-1$	\overline{D}

Figure 6.73 Result of a fault effect propagating to a faulty line


TG from a Known Initial State

```
r = 1
repeat
  begin
    build model with r time frames
    ignore the POs in the first r - 1 frames
    ignore the  $q^+$  outputs in the last frame
     $q(1)$  = given initial state
    if (test generation is successful) then return SUCCESS
    /* no solution with r frames */
    r = r + 1
  end
until r =  $f_{\max}$ 
return FAILURE
```

Maximum Unroll factor

Once circuit is unrolled, we can use any of the test generation algorithm we studied for combinational circuits, such as D-alg(), PODEM, etc.


Iterative Array Model

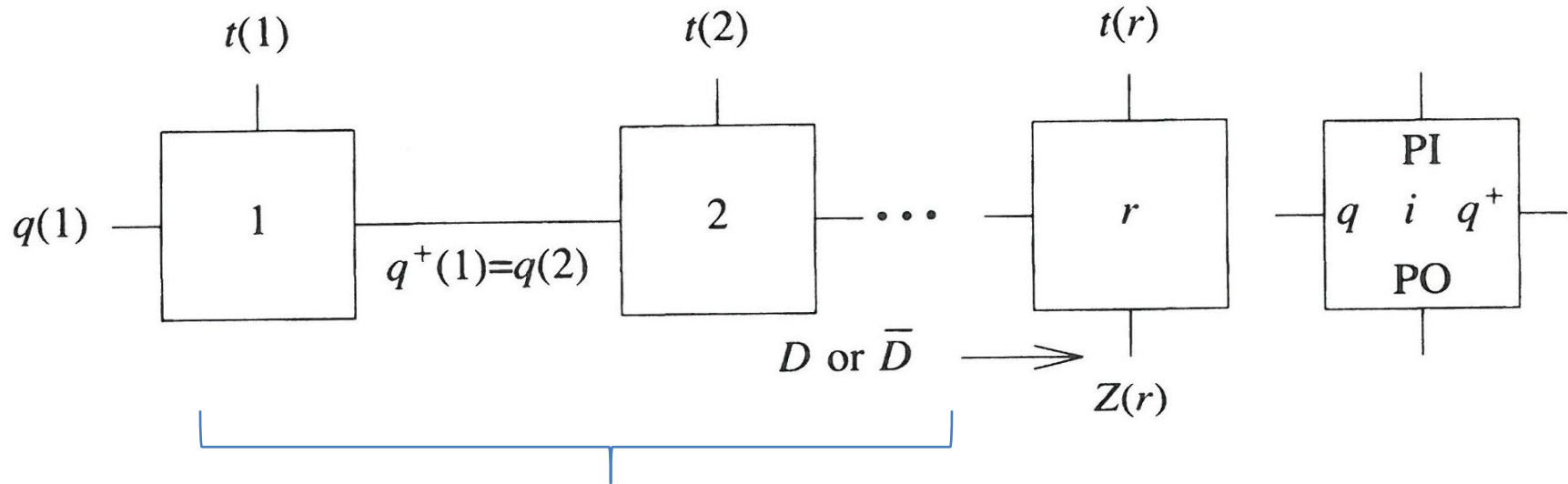


Ignore POs in
r-1 slices

Example

→ Assume $q_1 = a_2 = 0$

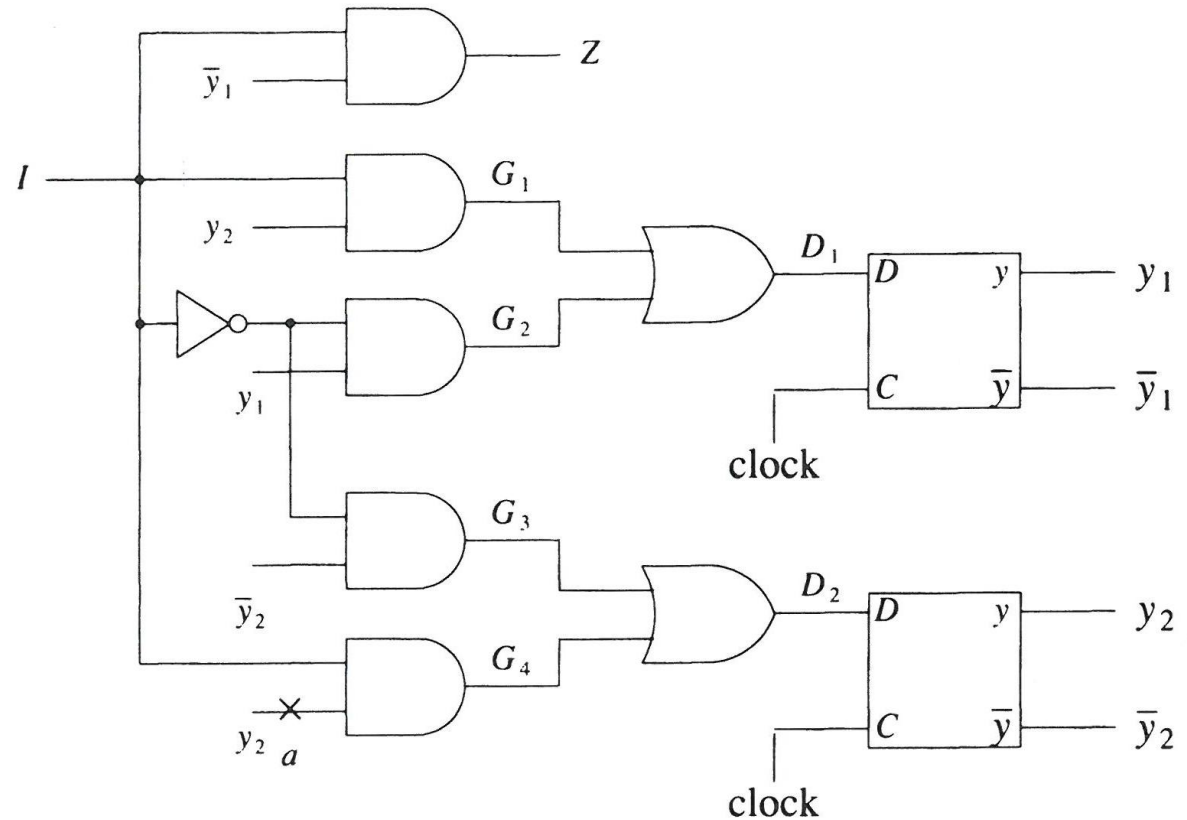


Time Frame

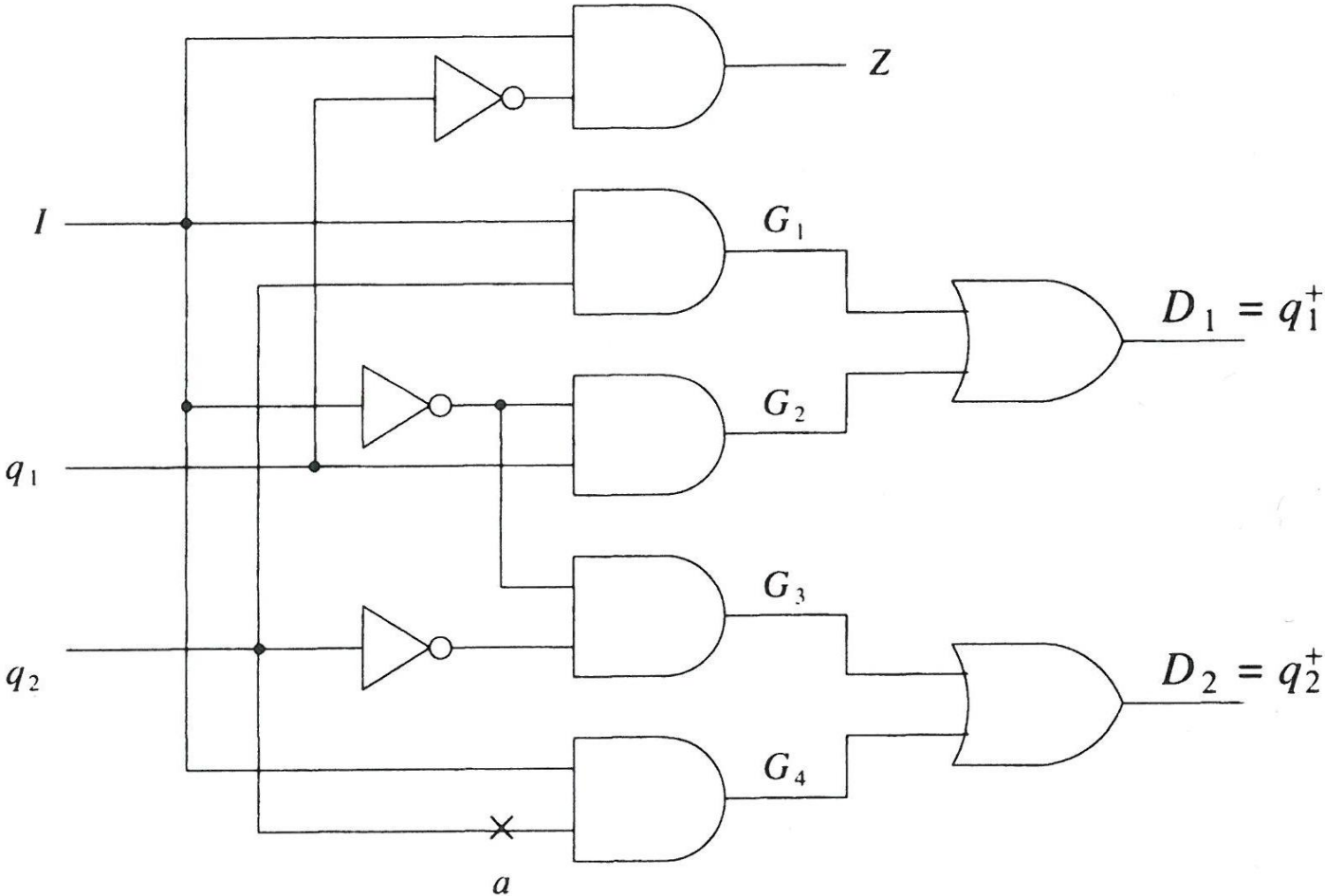


Time Frame 1

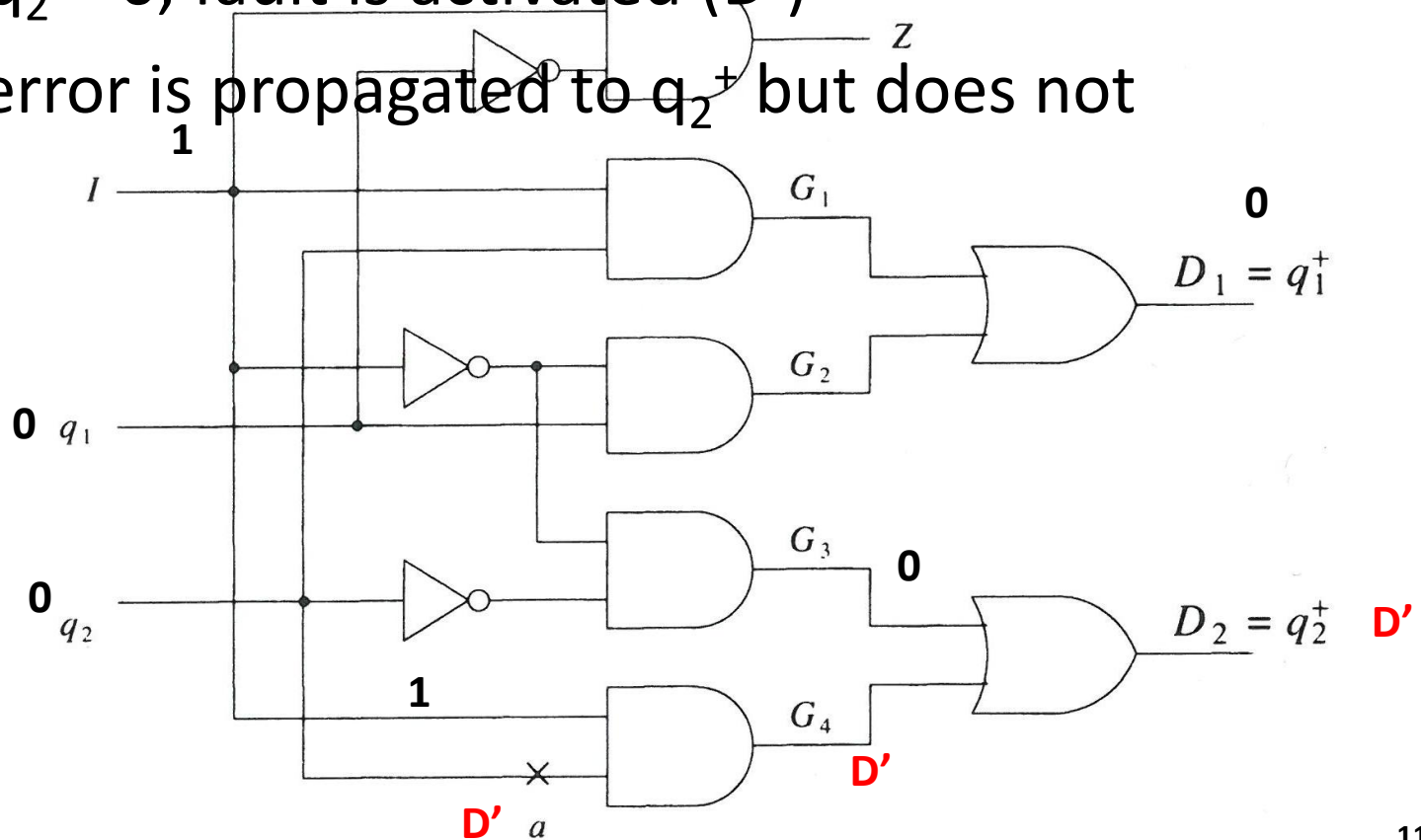
- With $q_1 = q_2 = 0$, fault is activated (D')
- With $I=1$, error is propagated to q_2^+ but does not reach Z



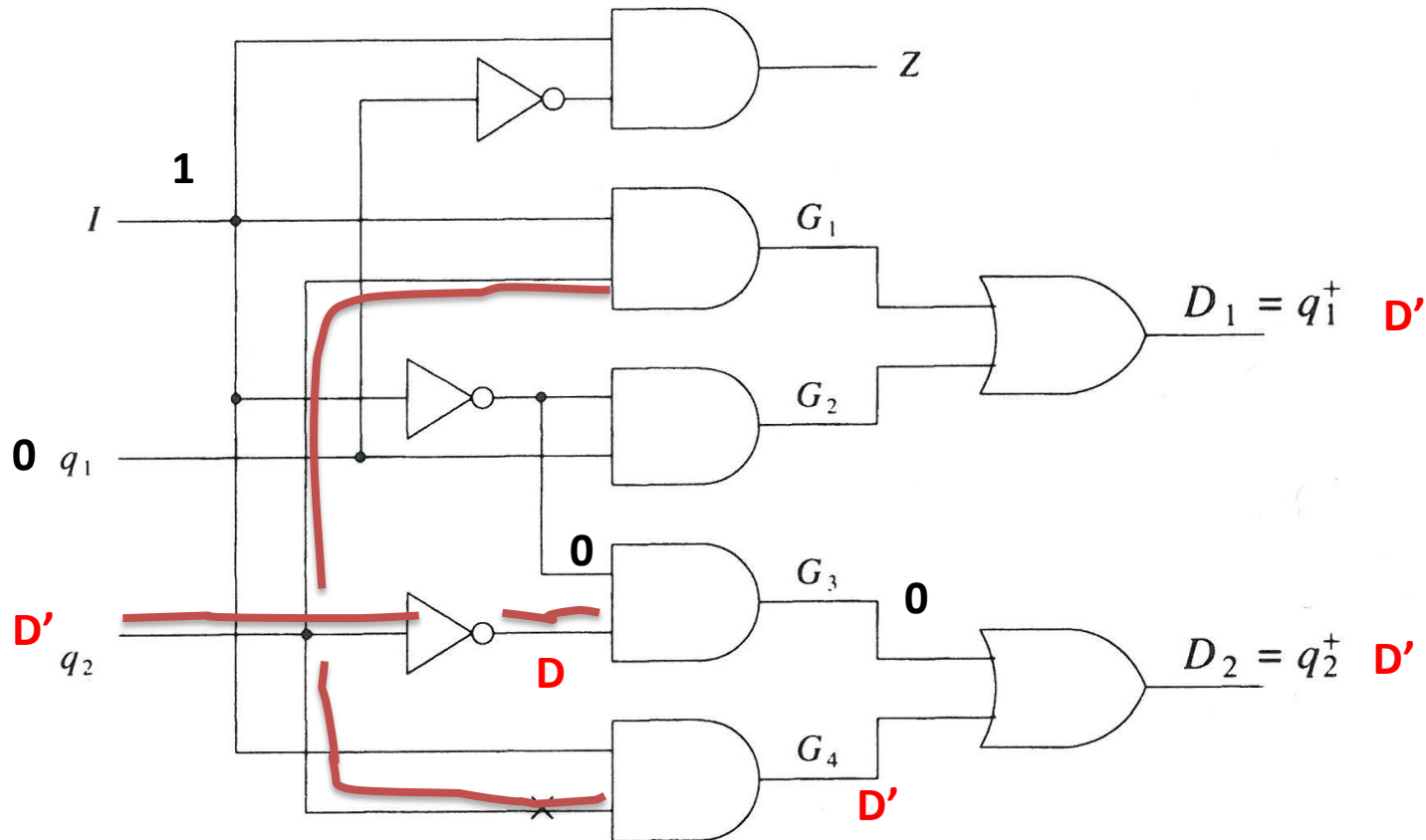- D-frontier = {G1, G3, G4}
- If G1 or G4 is chosen, then $I = 1$ gives $q_1^+ = D'$ and $q_2^+ = D'$
- If G3 is selected with $I = 0$ gives $q_1^+ = 0$ and $q_2^+ = D$



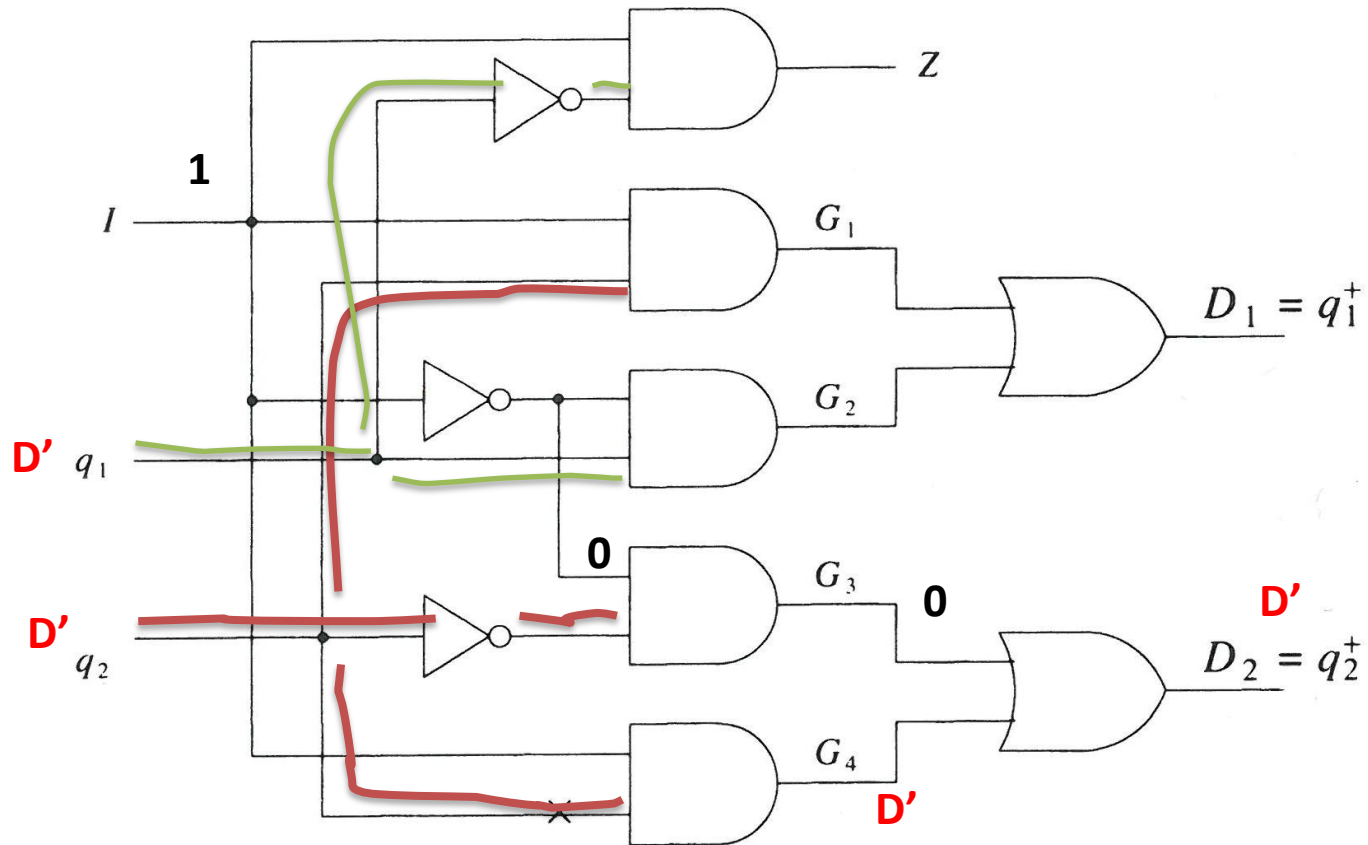- D-frontier = {Z, G1, G2, G3, G4}
- With $l=1$, we get $Z = D$, error propagated to a PO!
- Desired test sequence is $l = (1, 1, 1)$




Generation of Self-initializing Test Sequences



```
r = 1
p = 0
repeat
  begin
    build model with  $p + r$  time frames
    ignore the POs in the first  $p + r - 1$  frames
    ignore the  $q^+$  outputs in the last frame
    if (test generation is successful and every  $q$  input in the first frame has
      value  $x$ ) then return SUCCESS
    increment  $r$  or  $p$ 
  end
until ( $r+p=f_{\max}$ )
return FAILURE
```

Generation of Self-initializing Test Sequences

(a)


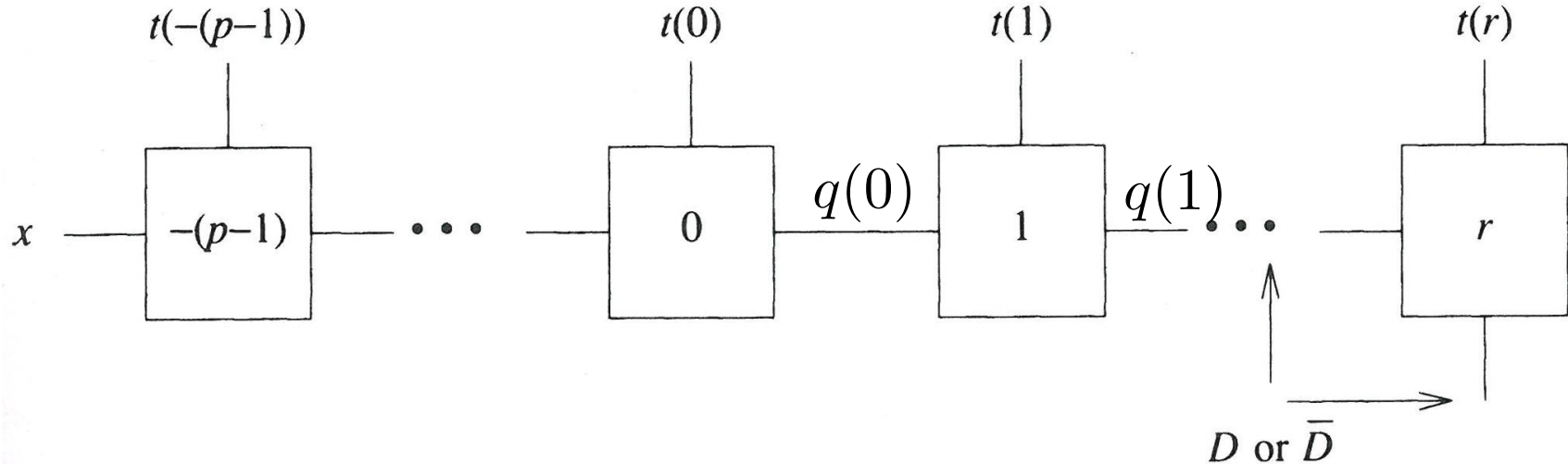


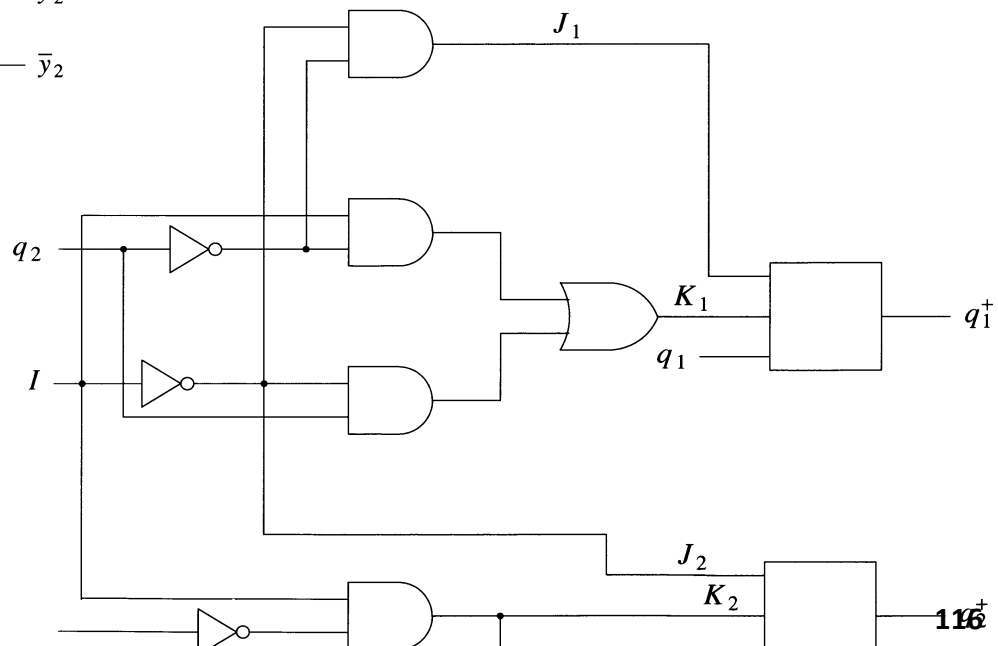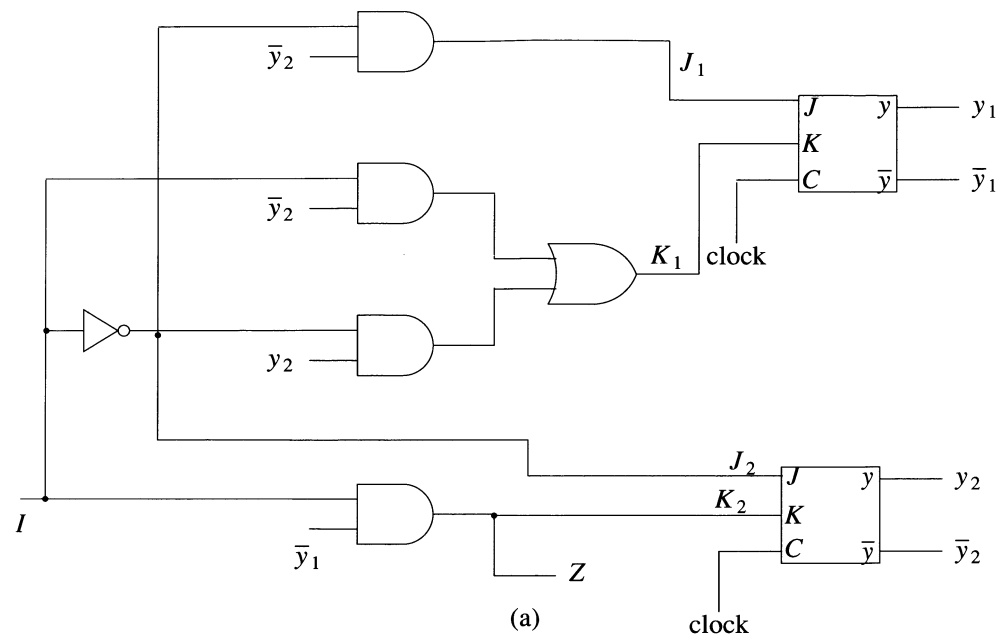1. Activate fault in frame 1, and propagate it to PO using r frames.
2. If $q(0)$ is not all x , justify $q(0)$ by backward propagation of p frames.



$$q^+ = J\bar{q} + \bar{K}q \quad \rightarrow$$

Example: Iterative Array: Detect Z s-a-0

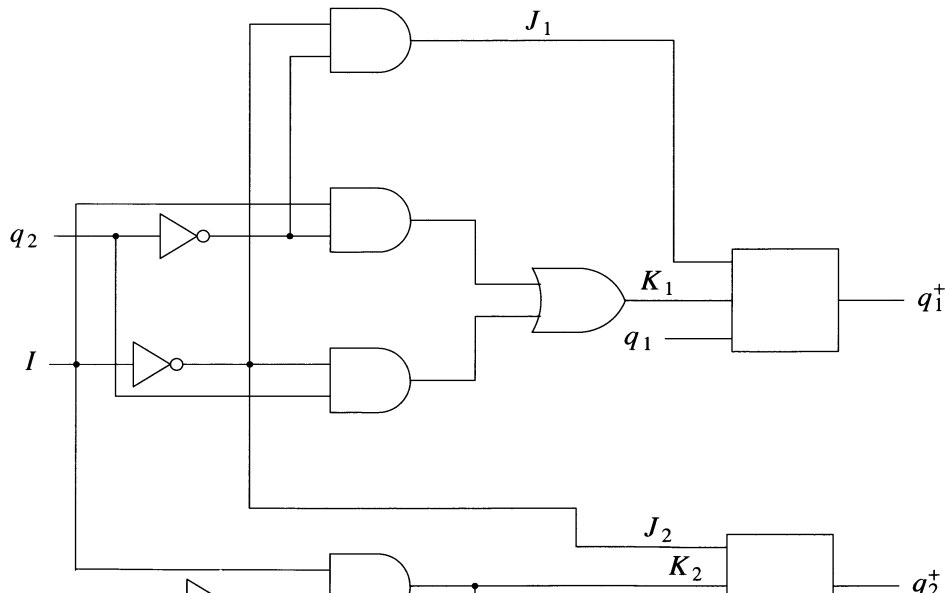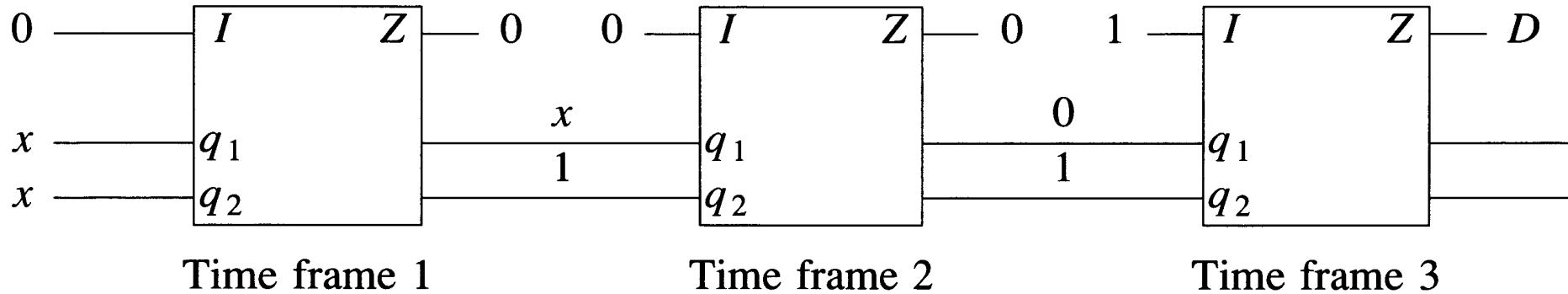

$$q^+ = J\bar{q} + \overline{K}q$$

Example: Iterative Array: Detect Z s-a-0

