

# **CIS 4930 Digital System Testing**


## **Built-In Self Test (BIST)**

Dr Hao Zheng  
Comp. Sci. & Eng.  
U of South Florida


# Introduction
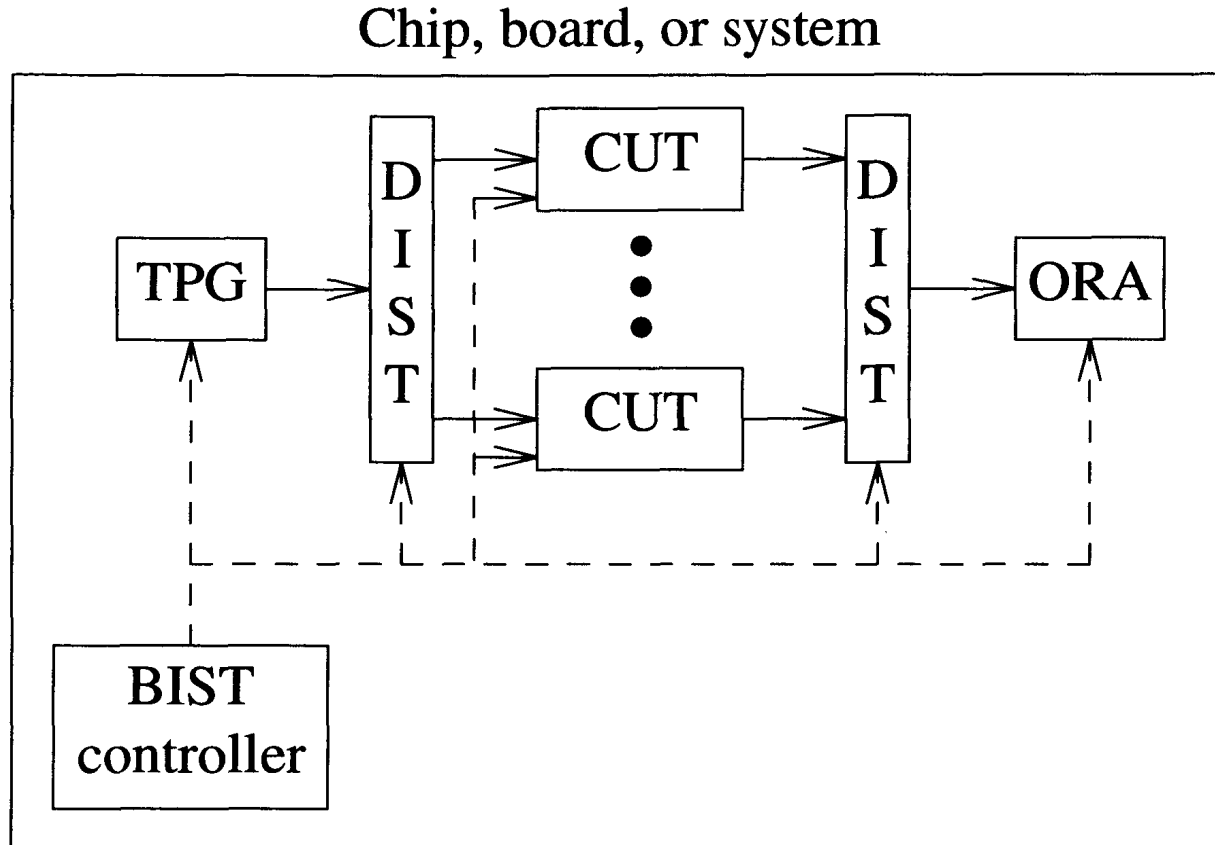
# Built-In Self-Test (BIST)

- BIST is the capability of a circuit (chip, board, or system) to test itself



# Forms of Built-In Self-Test (BIST)

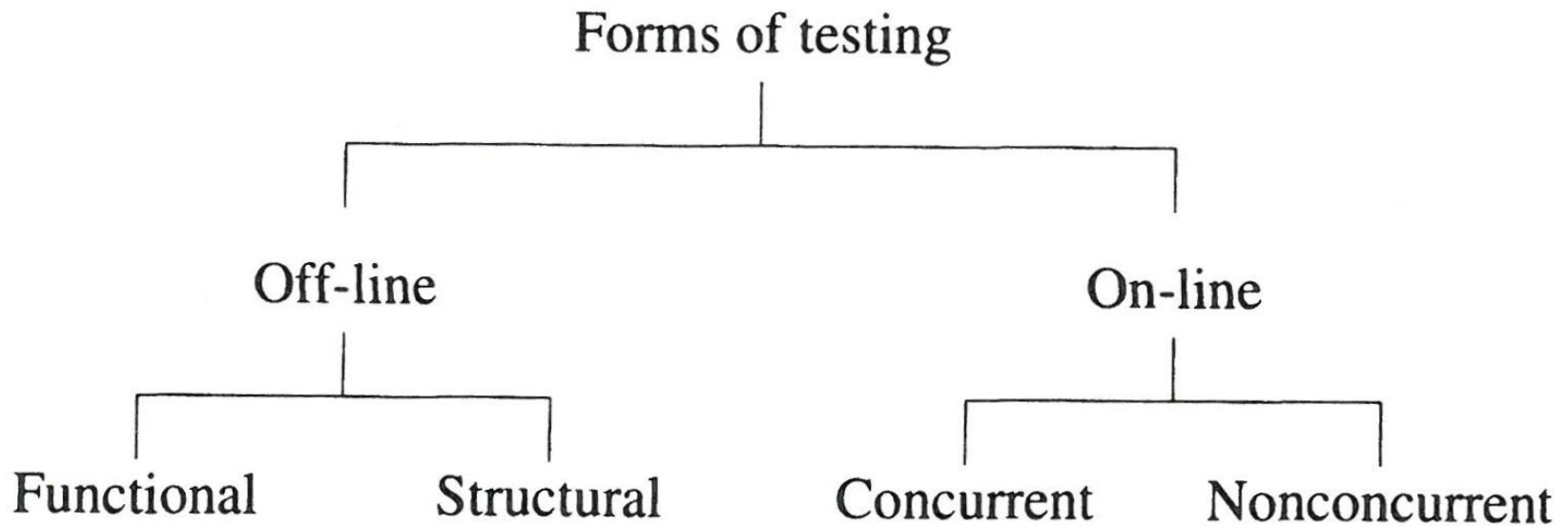

**Figure 11.1** Forms of testing

# On-line BIST

- Testing occurs during normal functional operating conditions
  - Circuit Under Test (CUT) is *not* put in test mode
- **Concurrent online BIST**
  - Testing occurs *simultaneously with normal functional operation*
- **Non-concurrent online BIST**
  - Testing while system is in **idle state**
  - Executing diagnostic software
  - Test process can be interrupted so that normal operation can resume

# Off-line BIST

- Testing a system when the it is not carrying out its normal functions
- Systems, boards, and chips can be tested
- Applicable at the manufacturing, field, depot, and operational stages
- Usually employs test-pattern generators (TPGs) and output response analyzers (ORAs)
- Errors cannot be detected in real time

# Off-line BIST – cont'd

- **Functional off-line BIST**
  - Test based on functional description
  - Employs a functional fault model
- **Structural off-line BIST**
  - Explicit structural fault model may be used
  - Fault coverage based on **structural fault detection**
  - Usually tests are generated and responses are compressed

Our discussion is primarily on **Structural Off-line BIST**

# Glossary of key BIST Architectures

BILBO — built-in logic block observer (register)

LFSR — linear feedback shift register

MISR — multiple-input signature register

ORA — (generic) output response analyzer

PRPG — pseudorandom pattern generator, often referred to as a pseudorandom number generator

SISR — single-input signature register

SRSG — shift-register sequence generator; also a single-output PRPG

TPG — (generic) test-pattern generator



# Hardcore

- Parts of circuit that must be operational (correct) to execute a self-test
- At a minimum it consists of Power, Ground, and Clock Distribution
- Easy to detect, but hard to diagnose
  - Faults may be in CUT or hardcore
- Usually tested by external test equipment
- Designer attempts to minimize complexity of hardware

# Levels of Test

- **Production Test**

- Newly manufactured components
- Performed at Chip, Board, System levels
- Reduces the need for expensive ATE (Automated Test Equipment)

- **Field Testing**

- Eliminates the need for expensive special test equipment.
- Improve maintainability,
- Reduce life-cycle costs.

# Test-Pattern Generation for BIST


# Test Pattern Generation for BIST

Assume CUT =  $n$ -input,  $m$ -output combinational circuit

- **Exhaustive Testing**
  - Exhaustive test-pattern generators – expensive
- **Pseudo-random Testing**
  - Weighted test generator
  - Adaptive test generator
- **Pseudo-exhaustive testing (cf. 8.3)**
  - Syndrome driver counter
  - Constant-weight counter
  - Combined LFSR and shift register
  - Combined LFSR and XOR gates
  - Condensed LFSR
  - Cyclic LFSR




# XOR Gates in Feedback

 

S0	0	1	1
S1	0	0	1
S2	1	0	0
S3	1	1	0
S4 = S0	0	1	1
⋮			
⋮			

Cycles through  
4 states


# XOR Gates in Feedback

 

S0	0	1	1
S1	0	0	1
S2	1	0	0
S3	1	1	0
S4 = S0	0	1	1
⋮			
⋮			

Cycles through  
4 states

# XOR Gates in Feedback

 


S0	0	1	1
S1	0	0	1
S2	1	0	0
S3	1	1	0
S4 = S0	0	1	1
⋮			
⋮			

Cycles through  
4 states




# XOR Gates in Feedback

 

S0	0	1	1
S1	0	0	1
S2	1	0	0
S3	1	1	0
S4 = S0	0	1	1
⋮			
⋮			

Cycles through  
4 states


# XOR Gates in Feedback

 

S0	0	1	1
S1	0	0	1
S2	1	0	0
S3	1	1	0
S4 = S0	0	1	1
⋮			
⋮			

Cycles through  
4 states

# Maximal Length LFSR

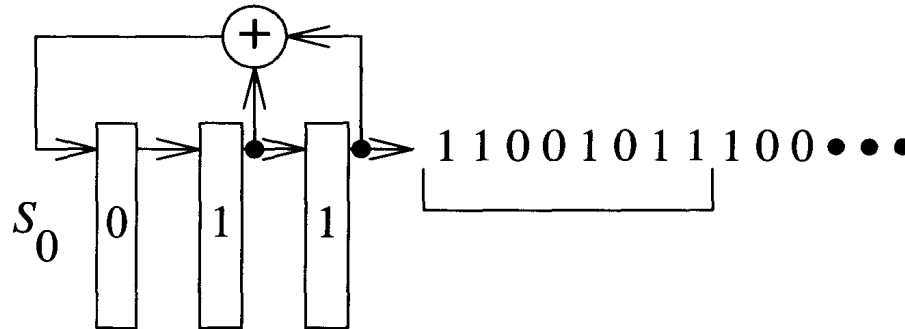

$s_1$	0	0	1
$s_2$	1	0	0
$s_3$	0	1	0
$s_4$	1	0	1
$s_5$	1	1	0
$s_6$	1	1	1
<hr/>			
$s_7 = s_0$	0	1	1
	•		
	•		
	•		

Generates a cyclic sequence of length  $2^n - 1$

All-0 initial state leads to a sequence of length 1.

# Exhaustive Testing

- Test the  $n$ -input comb. circuit with  $2^n$  inputs
- Binary counter can be used as TPG.
- Autonomous LFSR can also be used.
- Guarantees that all detectable faults that *do not* introduce sequential behavior will be detected
  - i.e. no bridging faults.
- Depending on clock rate,  $n > 22$  is impractical
- Not used for sequential circuits

# Pseudo-Random Testing

- Many characteristics of random patterns
- Generated deterministically => Repeatable
- With or without replacement
- **With replacement** = patterns can repeat
- **Without replacement** = unique patterns (autonomous LFSR can be a source)
- Applicable to both comb. and seq. circuits

# Bias in Pattern Generation

- Autonomous LFSR: 0's and 1's balanced in the output
- Sometimes we want a bias (say more 1's than 0's)
- Example: 4-input AND gate
  - Probability of an input set to 0 is  $15/16$
  - With random inputs, hard to test other input  
s-a-0 or s-a-1 fault

# Weighted & Adaptive Test Generation

- **Weighted Test Generator**
  - Distribution of 0s and 1s -> not uniform
  - Can be constructed by LFSR + a comb. Circuit
  - When testing a circuit using WTG, preprocessing is carried out to determine weights
  - Therefore, each part of circuit can be tested with different distributions
- **Adaptive Test Generator**
  - Uses a WTG
  - Results of fault simulation used to modify weights
  - Efficient in terms of test length
  - Requires complex TPG hardware

# Pseudo-Exhaustive Testing

- Achieves benefits of exhaustive testing *but with far fewer test patterns*
- Relies on circuit segmentation
- A segment = subcircuit of the CUT
- Attempts testing each segment exhaustively
- Segments need not be disjoint
- Forms of Segmentation
  1. Logical Segmentation
    - a. Cone Segmentation
    - b. Sensitized Path Segmentation
  2. Physical Segmentation



# Cone Segmentation

- Cone segmentation of a  $m$  output circuit is logically segmented into  $m$  cones
- Cone = all logic associated with one output
- Each cone tested exhaustively
- All cones tested concurrently


 


Figure 11.3 A (4,2)-CUT

# Sensitized Path Segmentation


 
- Example:
  - C partitioned into  $C_1$  and  $C_2$
  - Set inputs to B such that  $D=1$  and apply  $2^{n_1}$  patterns to test  $C_1$
  - Similarly test  $C_2$
  - Need  $2^{n_1} + 2^{n_2} + 1$  patterns instead of  $2^{n_1 + n_2}$



# Physical Segmentation

- In large circuits, pseudo-exhaustive testing leads to large test sets
- Can employ physical segmentation
  - Partitioning: Circuit is divided into sub-circuits
  - Bypass Storage Cell
    - Normal mode: acts as a wire
    - Test mode: part of an LFSR


# Physical Segmentation by Partitioning

 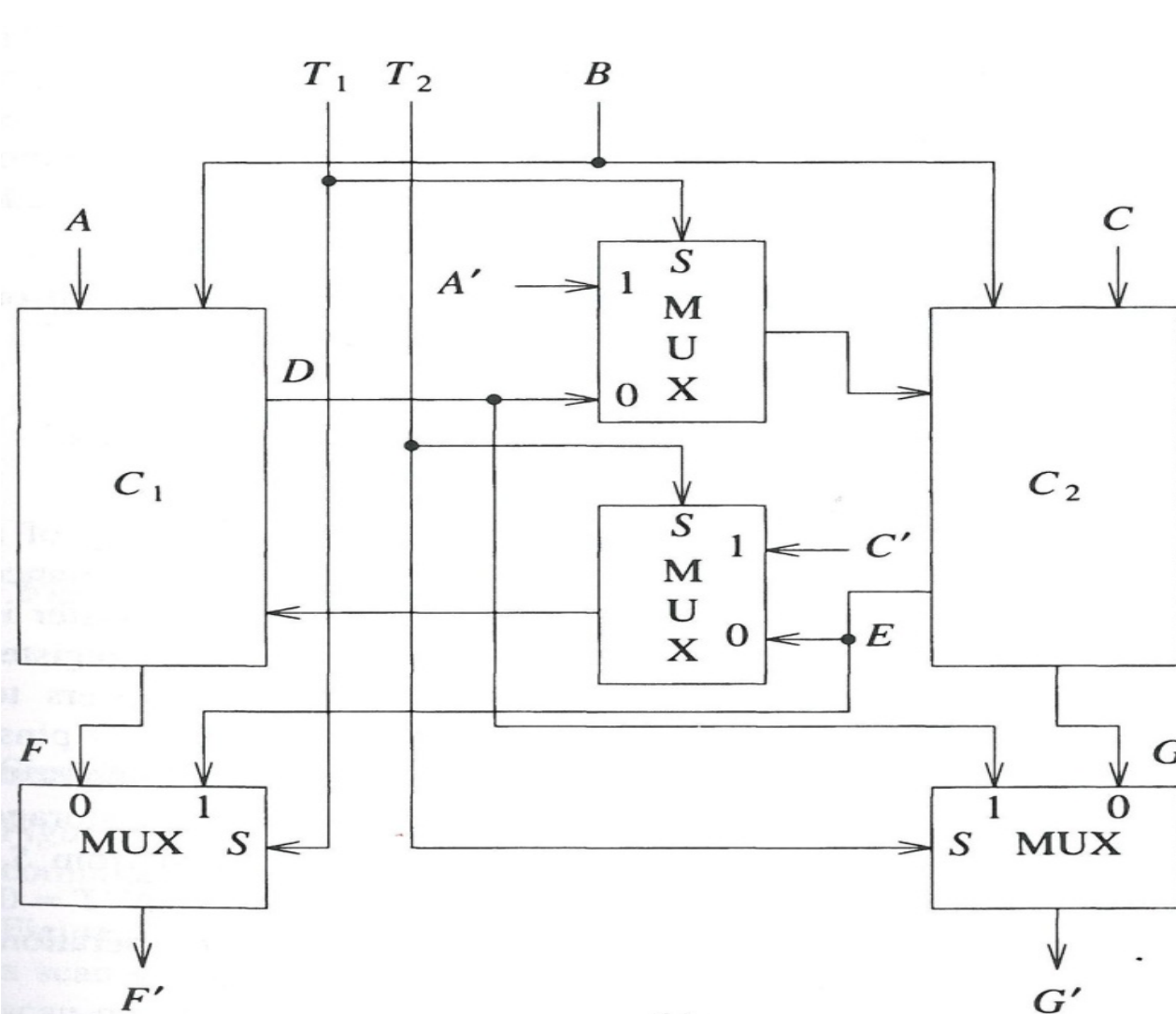



$T_1$	$T_2$	Mode
0	0	normal
0	1	test $C_1$
1	0	test $C_2$
 
# Physical Segmentation by Storage Cells


- Let us say we want to segment the following such that no signal is a function of more than 4 variables



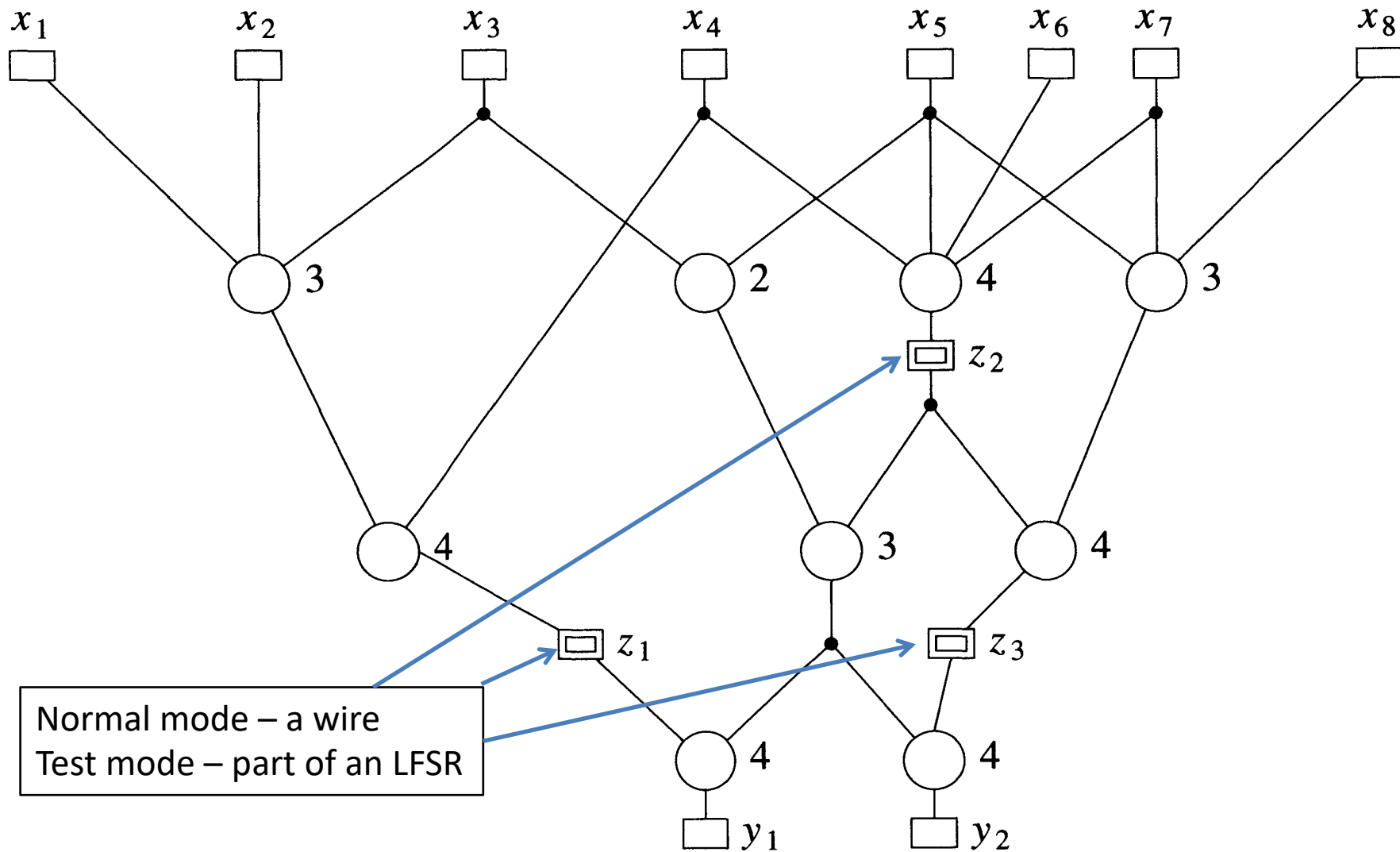

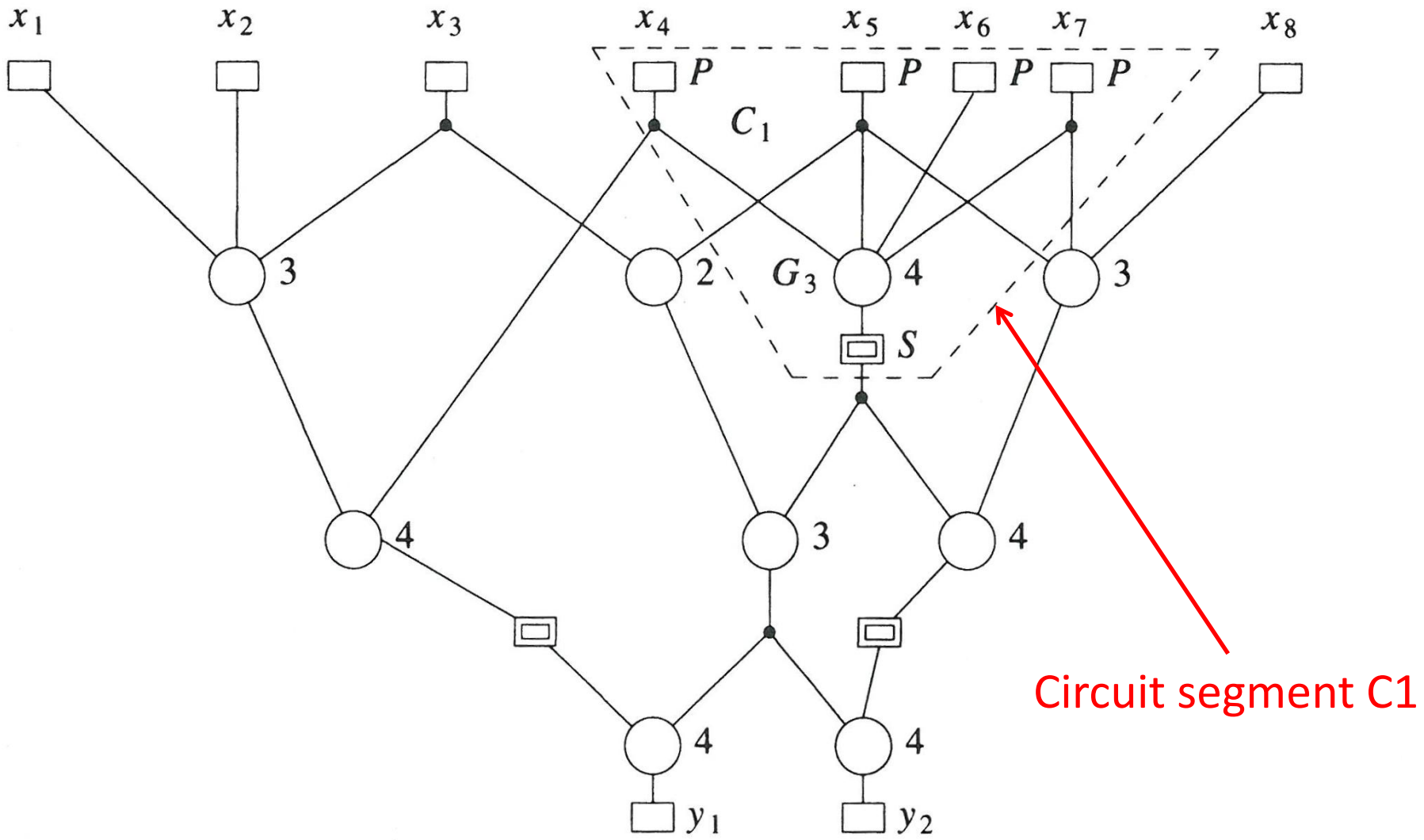


(a)

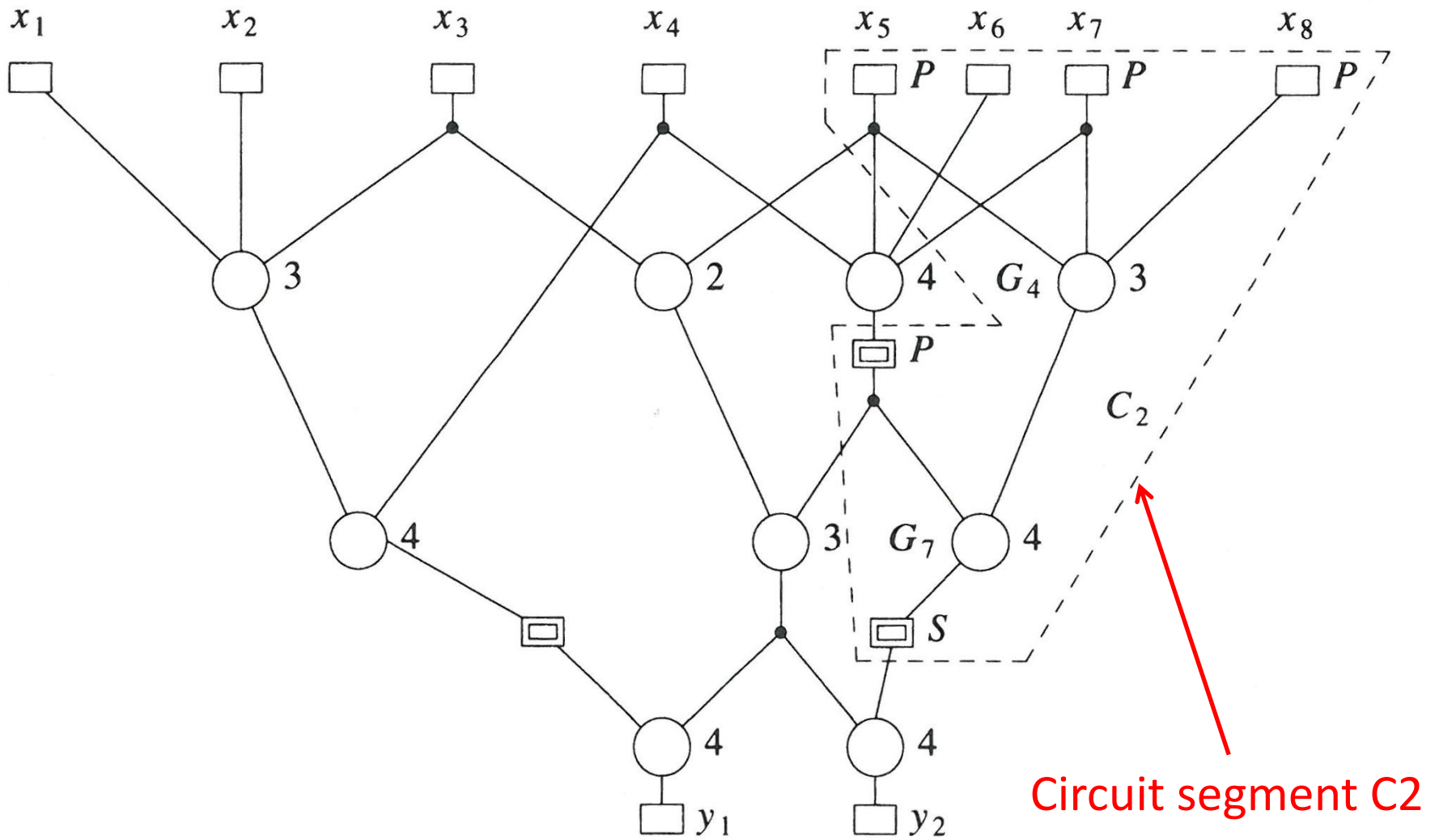


(b)

Circuit segment C2



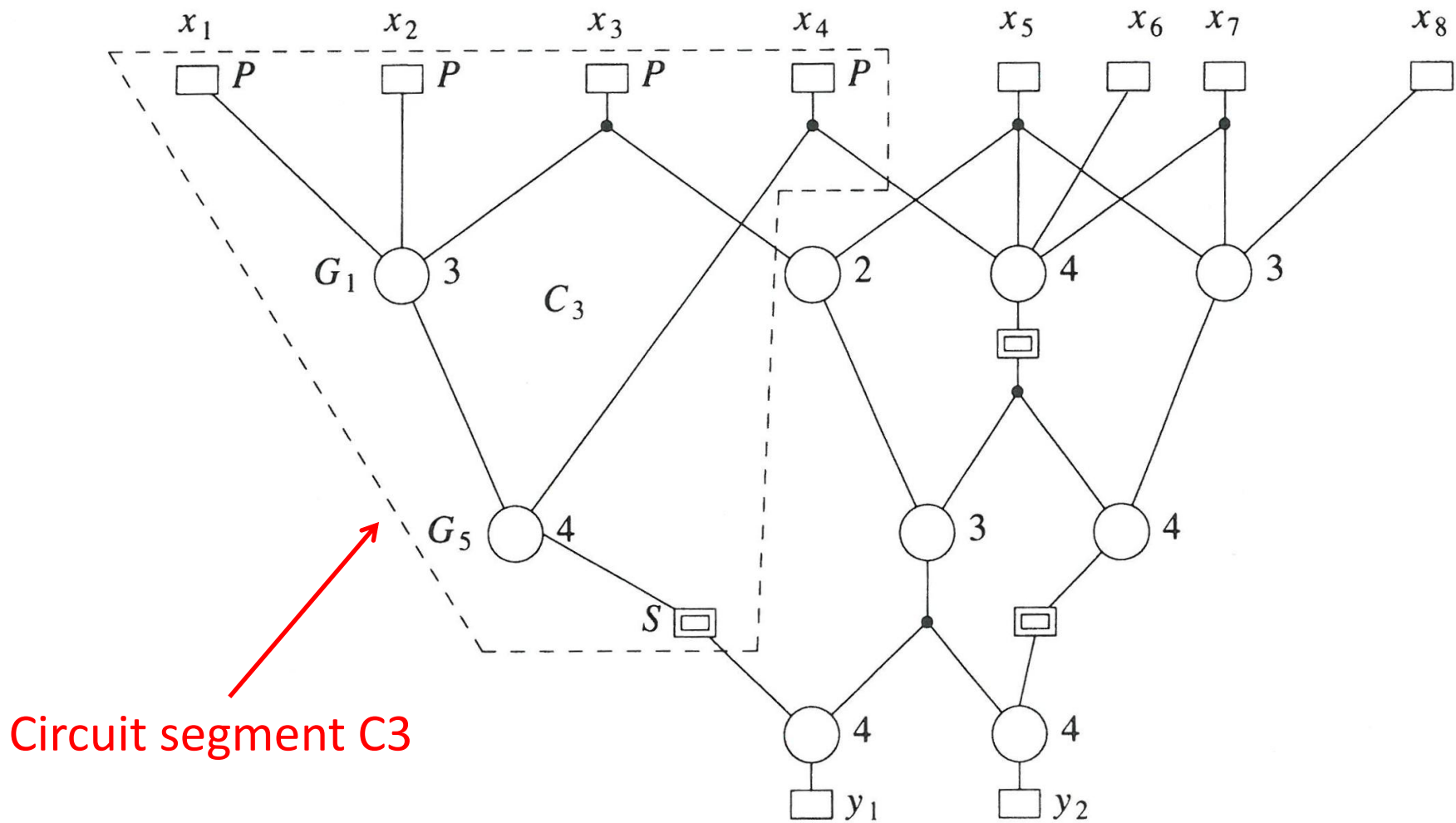


(c)

 

Circuit segment C3

(d)


# Identification of Test Signal Inputs

 

- $f$  and  $g$  are functions of only two inputs each
- To exhaustively test the multiple function  $(f, g)$ , we need 8 vectors
- Since no output is function of both  $x$  and  $z$ , same test data can be applied to both these lines
  - 2 test signals
  - 4 test vectors are sufficient
 
# Maximal-Test-Concurrency (MTC) circuit

- A circuit is said to be a *maximal-test-concurrency* (MTC) circuit, if the minimal number of required test signals is equal to the maximum number of inputs upon which any output depends.



# Non-MTC circuit

- All three signals are required, can still be tested exhaustively by just four test patterns

 


Figure 11.6 A nonmaximal-test-concurrency circuit with verification test input

# TPG – Syndrome-Driver Counter

- If  $(n-p)$  input share test signals with  $p$  other inputs, at most  $2^p$  tests are required.
  - $n$ : # of inputs
- $n = 4, p = 3, w=2$ 
  - $w = \#$  of inputs of a segment
- At most 8 tests are needed.
- 0000 & 1111 are not needed

 


Figure 11.3 A (4,2)-CUT

# TPG – Constant-Weight Counter

- A  $(n, w)$  circuit can be tested by a counter implementing by  $w$ -out-of- $K$
- Complexity of the counter can be high for large  $w$

1100

1010

1001


0110

0101

0011

# TPG – Combined LFSR/SR

- $(n, w)$  circuit
- Lower cost
- May generate more tests
- # of tests near minimal when  $w \ll n/2$

 


**Figure 11.12** A 4-stage LFSR/SR for a (4,2)-CUT



# TPG – Condensed LFSR

- $(n, w)$  circuit
- Can produce efficient test set when  $w \geq n/2$
- But produce more test than combined LFSR/SR
- What patterns does it generate?

 

**Figure 11.15** A condensed LFSR for a (4,2)-CUT

# Generic Off-line BIST Architectures


- Off-line BIST Architectures
  1. Centralized or Distributed
  2. Embedded or Separate
- BIST architecture elements:
  1. Test pattern generators
  2. Output response analyzers
  3. Circuit under test
  4. Distribution system (DIST) for transmitting data from TPGs to CUTs and from CUTs to ORAs
  5. BIST Controller

# BIST Controller

During testing BIST Controller can carry out one or more functions:


1. **Single-step** the CUTs through some test sequence
2. **Inhibit** system clocks and control test clocks
3. **Communicate** with other test controllers
4. **Control** the operation of self-test (seeding of registers, number of test patterns processed, etc.)

# Centralized and BIST Architecture

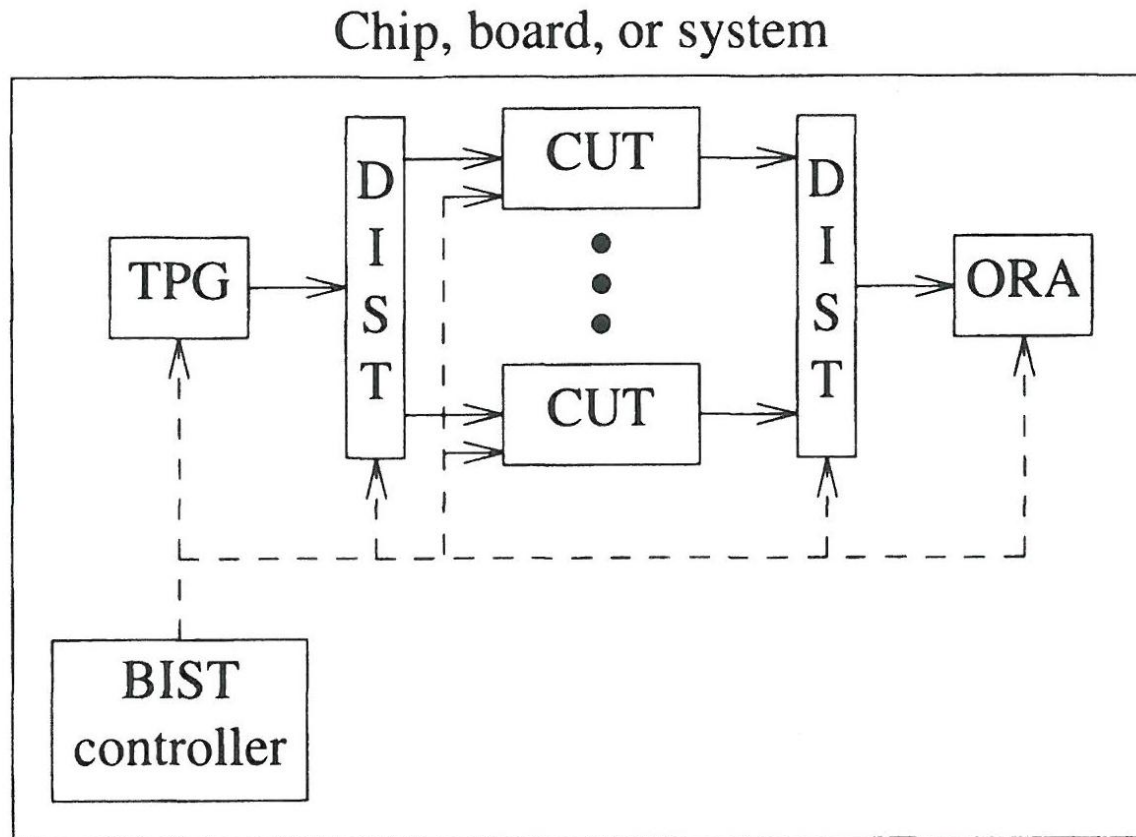

**Figure 11.18** Generic form of centralized and separate BIST architecture


# Distributed and Separate BIST

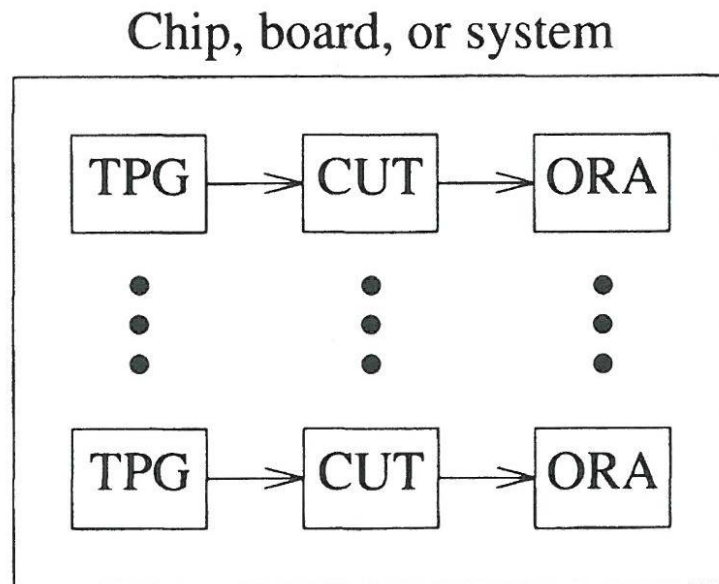

**Figure 11.19** Generic form of distributed and separate BIST architecture

# Distributed and Embedded BIST

- TPG and ORA configured from within CUT
- Complex design to control

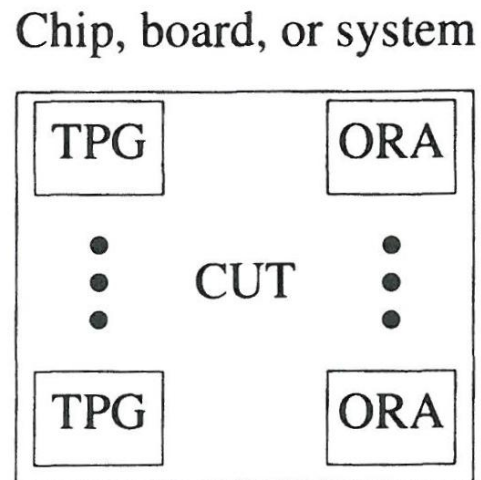

**Figure 11.20** Generic form of distributed and embedded BIST architecture


# BIST Architecture

When choosing BIST architecture, following factors need to be considered:

1. Degree of test parallelism
2. Fault coverage
3. Level of packaging
4. Test time
5. Physical constraints
6. Complexity of replaceable units
7. Factory and field test-and-repair strategy
8. Performance degradation

# Some Example BIST Architectures

## 1. Centralized and Separate Board-Level BIST

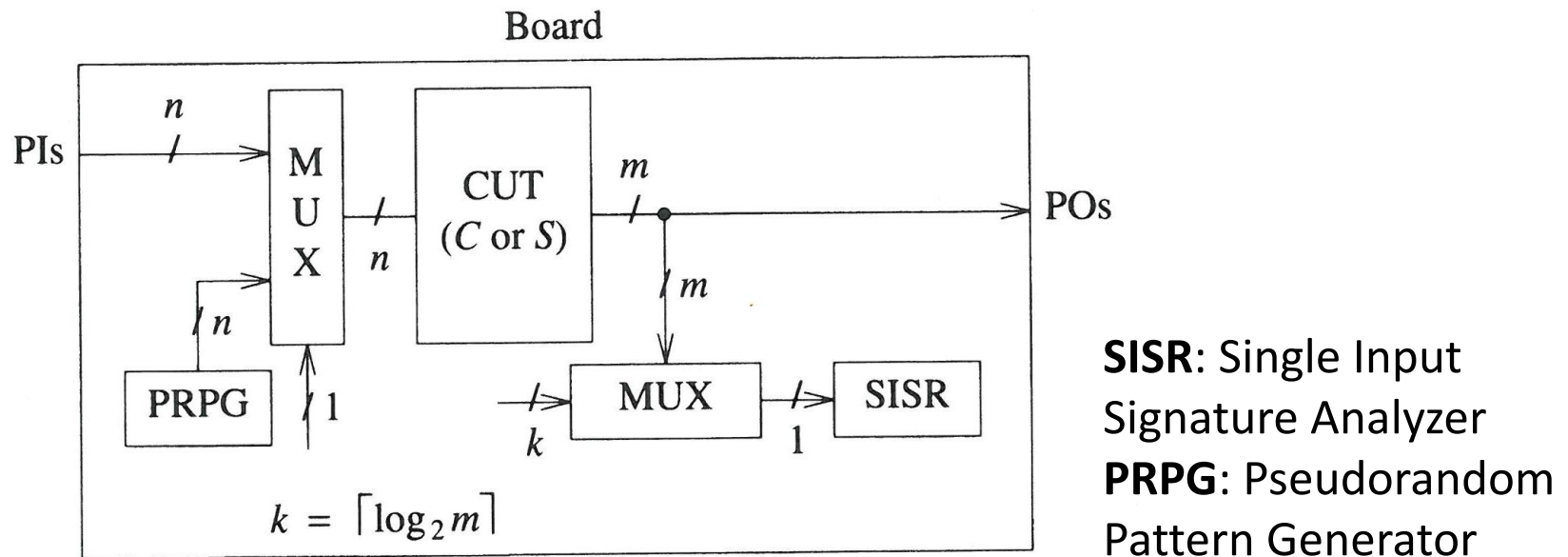


**Figure 11.21** A centralized and separate BIST architecture (CSBL)

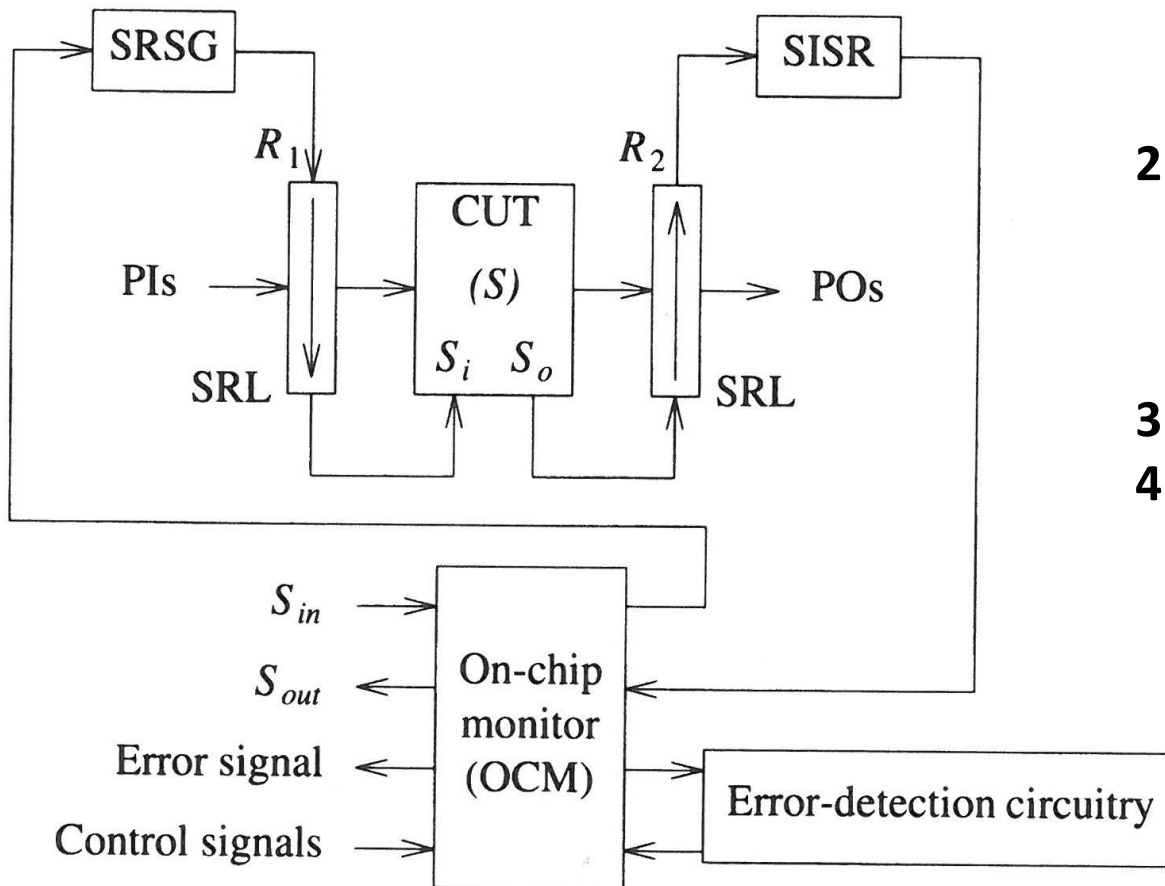

# Some Example BIST Architectures

## 2. LSSD On-Chip Self-Test (LOCST)



### Test Process

- 1. Initialize**  
Scan path loaded with seed via  $S_{in}$
- 2. Activate Self-test mode**
  - a) Disable sys clks on R1 and R2
  - b) Enable LFSR operation
- 3. Execute Self-test**
- 4. Check Result**  
Compare final value of SISR with known good signature

**LSSD:** Level Sensitive Scan Design

**SRSG:** Shift Register Sequence Generator

Figure 11.25 The LOCST architecture

# Some Example BIST Architectures

## 3. Random Test Data (RTD) BIST


- Previous archs – entire scan path be loaded with new data to apply a single test pattern to CUT; RTD overcomes this

- Test process:

a) R1, R2, and R3 set to scan mode and a seed pattern is loaded

b) Registers put to test mode and held while circuit is tested

 
c) For each clock cycle, R1 and R2 generate a new test pattern, and R2 and R3 operate as a MISR






# BIBLO Register Modes


**B1 = B2 = 1**  
**Normal Mode**

 

 
**B1 = B2 = 0**  
**Shift Register Mode**



**B1 = 1, B2 = 0**  
**LFSR Mode**

 

# BIST Design with BILBO Registers

 

(a)

- To test  $C_1$ 
  1.  $R_1$  and  $R_2$  are seeded
  2.  $R_1$  into PRPG mode,  $R_2$  into MISR mode
  3. Hold inputs to  $R_1$  to value 0 so that LFSR ( $R_1$ ) acts as a PRPG
  4. Run for N clock cycles
- If  $C_1$  is not too large,  $C_1$  can be tested exhaustively (except for all-zero pattern)
- At the end of test session,  $R_2$  scanned out and signature checked
- Need two test sessions, one for  $C_1$  and other for  $C_2$

# Summary

- Built-In Self Test – can be offline or online
- Needs test pattern generators (TPGs) and output response analyzers (ORAs)
- Linear Feedback Shift Registers (LFSRs) can be used as both as a TPG and as an ORA
- Offline BIST architectures can be centralized or distributed, embedded or separate