

System-on-Chip Design

RTL Modeling

Dr. Hao Zheng
Comp. Sci & Eng.
U of South Florida

Outline

- Data Types for logic circuits
- Modeling Combinational Logic
- Modeling Synchronous Logic

Data Types for Modeling Logic Designs

Logic and Bounded Integer Types

- Logic types

```
sc_bit var; //Values: '0', '1'  
sc_logic var; //Values: '0', '1', 'X', 'Z'  
sc_bv<length> var; //bit vector  
sc_lv<length> var; //logic vector
```

- Bounded integer types

```
sc_int<length> var; //signed int (<= 64bit)  
sc_uint<length> var; //unsigned int (<= 64bit)  
sc_bigint<length> var; //signed int  
sc_biguint<length> var; //unsigned int
```

sc_logic

'0', SC_LOGIC_0	false
'1', SC_LOGIC_1	true
'X', 'x', SC_LOGIC_X	unknown
'Z', 'z', SC_LOGIC_Z	high-impedance

Data Operations

Operation	Type sc_bit sc_bc sc_lv	sc_bc sc_lv	sc_int, sc_uint sc_bigint, sc_biguint
Bitwise	~ & ^	~ & ^ << >>	~ & ^ << >>
Arithmetic			+ - * / %
Logical			
Equality	== !=	== !=	== !=
Relational			> < <= >=
Assignment	= &= = ^=	= &= = ^=	= += -= *= /= %= &= = ^=
Increment Decrement			++ --
Arithmetic if			
Concatenation	,	,	,
Bitselect		[x]	[x]
Partselect		range()	range()

Examples

```
sc_logic x;  
x = '1';  
x = 'Z';
```

```
sc_bit a;  
sc_logic b, c;  
a == b;  
b != c;  
b == '1';
```

```
sc_lv<4> val;  
val = "110X";
```

```
sc_int<16> x, y, z;
```

```
z = x & y; //bitwise-or of x and y  
z = x >> 4; //x right shift by 4  
x = x + y;
```

```
sc_uint<8> ui1, ui2;  
sc_int<16> i1, i2;  
ui1 = i2; // type conversion and  
i1 = ui2; // possible truncation
```

Examples

```
sc_lv<8> ctrl_bus;  
sc_lv<4> mult;
```

```
ctrl_bus[5] = '0';  
ctrl_bus.range(0,3) = ctrl_bus.range(7,4);  
mult = ctrl_bus.range(2,5);
```


Vector and Ranges

```
// Bit select or range() cannot be  
// applied to a port or a signal
```

```
sc_in<sc_uint<4> > data;  
sc_signal<sc_bv<6> > counter;  
sc_uint<4> temp;  
sc_uint<6> cnt_temp;  
bool mode, preset;
```

```
mode = data[2]; // not allowed
```

```
temp = data.read();  
mode = temp[2];
```

Arithmetic Operations

All fixed precision integer type calculations occur on a 64-bit representation and appropriate truncation occurs depending on the target result size

Arithmetic Operations

```
sc_uint<4> write_addr;  
sc_int<5> read_addr;
```

```
read_addr = write_addr + read_addr;
```

- E.g.:
 - write_addr is zero-extended to 64-bit
 - read_addr is sign-extended to 64-bit
 - + is performed on 64-bit data
 - result is truncated to 5-bit result and assigned back to read_addr

Arithmetic Operations

```
// Arithmetic operations cannot be  
// applied to bit/logic vectors.
```

```
sc_in<sc_bv<4> > pha1;  
sc_signal<sc_bv<6> > pha2;  
sc_uint<4> uint_pha1;  
sc_uint<6> int_pha2;
```

```
uint_pha1 = pha1;  
uint_pha2 = pha2 - uint_pha1;  
pha2 = uint_pha2;
```

Modeling Combinational Logic

Combinational Circuit Modeling

- Logic is described in member functions.
- `SC_METHOD` is used to implement those functions.
- Every `SC_METHOD` processes must have a sensitivity list that includes all input signals that a combinational logic reads.
- Every signal/variable must be assigned in every branch of a if/switch statement.

Ports and Signals

- Declaration

```
sc_in<port_type> port_name;
```

```
sc_out<port_type> port_name;
```

```
sc_inout<port_type> port_name;
```

```
sc_signal<signal_type> signal_name;
```

- Operations

read()

returns value of signal or port

write()

assigns value to signal or port

event()

returns true or false if event on signal or port

default_event()

any change of value

value_changed_event()

any change of value

posedge()

returns true if 0 -> 1 transition

negedge()

returns true if 1 -> 0 transition

Specialized Ports and Signals

```
sc_in<T> port_name;
```

```
sc_out<T> port_name;
```

```
sc_inout<T> port_name;
```

```
sc_signal<T> signal_name;
```

where T is bool or sc_logic, there are additional member functions available.

```
posedge_event() returns a sc_event
```

```
negedge_event() returns a sc_event
```

```
posedge() returns bool
```

```
negedge() returns bool
```


Reading and Writing Ports and Signals

```
#include "systemc.h"
```


logic operators are not allowed for ports.

```
SC_MODULE(xor_gates) {  
    sc_in<sc_uint<4> > a, b;  
    sc_out<sc_uint<4> > c;
```

```
void prc_xor_gates() { c = a ^ b; }
```

```
SC_CTOR(xor_gates) {  
    SC_METHOD(prc_xor_gates);  
    sensitive << a << b;  
}
```

```
}
```

 

A Compiler error may occur! Arithmetic ops cannot be applied to ports/signals directly.

Reading and Writing Ports and Signals

```
#include "systemc.h"
```

```
SC_MODULE(xor_gates) {  
    sc_in<sc_uint<4> > a, b;  
    sc_out<sc_uint<4> > c;
```

```
void prc_xor_gates() {  
    c = a.read() ^ b.read();  
}
```

```
SC_CTOR(xor_gates) {  
    SC_METHOD(prc_xor_gates);  
    sensitive << a << b;  
}};
```

Reading and Writing Ports and Signals

```
#include "systemc.h"

SC_MODULE(xor_gates) {
    sc_in<sc_uint<4> > a, b;
    sc_out<sc_uint<4> > c;

    void prc_xor_gates() {
        c.write(a.read() ^ b.read());
    }

    SC_CTOR(xor_gates) {
        SC_METHOD(prc_xor_gates);
        sensitive << a << b;
    }
};
```

SystemC Half Adder

```
// File half_adder.cpp
#include "systemc.h"

SC_MODULE(half_adder) {
    sc_in<bool> a, b;
    sc_out<bool> sum, carry;

    void prc_half_adder() { ... }

    SC_CTOR(half_adder) {
        SC_METHOD(prc_half_adder);
        sensitive << a << b;
    }
};
```

SystemC Decoder 2/4

```
// decode.h
#include "systemc.h"

SC_MODULE(decoder2by4) {
    sc_in<bool> enable;
    sc_in<sc_uint<2> > select;
    sc_out<sc_uint<4> > z;

    void prc_decoder2by4() { ... }


    SC_CTOR(decoder2by4) {
        SC_METHOD(prc_half_adder);
        sensitive(enable, select);
    }
};
```

SystemC Decoder 2/4

```
// decode.cpp
#include "decode.h"
void decoder2by4::prc_decoder2by4()
{
    if (enable) {
        switch(select.read()) {
            case 0: z=0xE; break;
            case 1: z=0xD; break;
            case 2: z=0xB; break;
            case 3: z=0x7; break;
        }
    }
    else
        z=0xF;
}
```

Switch statements are synthesized to multiplexers.

Hierarchy: Building a full adder

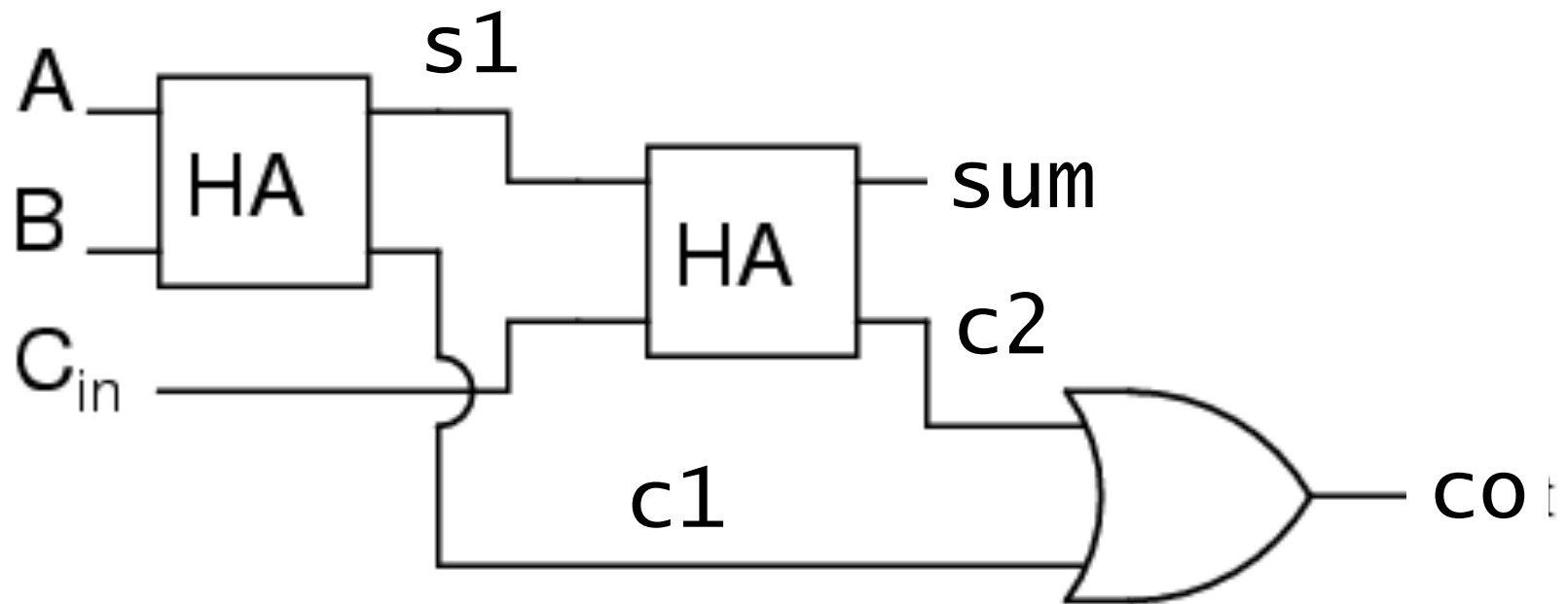

Hierarchy: Building a full adder

```
#include "systemc.h"
```

```
SC_MODULE(full_adder) {  
    sc_in<bool> a,b,cin;  
    sc_out<bool> sum, co;  
    sc_signal<bool> c1, s1, c2;  
    half_adder *ha1_ptr, *ha2_ptr;
```

```
    void prc_or() { co = c1 | c2; }
```

```
    SC_CTOR(full_adder) { ... }
```

```
    ~full_adder() { ... }
```

```
};
```


Hierarchy: Building a full adder

```
SC_CTOR(full_adder) {
    ha1_ptr = new half_adder("ha1");
    ha1_ptr->a(a);
    ha1_ptr->b(b);
    ha1_ptr->sum(s1);
    ha1_ptr->carry(c1);

    ha2_ptr = new half_adder("ha2");
    (*ha2_ptr)(s1, cin, sum, co);

    SC_METHOD(prc_or);
    sensitive << c1 << c2;
}
```

A Behavioral Model of a Full Adder

```
// File: fa.h
#include "systemc.h"

SC_MODULE(fa) {
    sc_in<sc_int<4> > a, b;
    sc_out<sc_int<4> > sum;
    sc_out<bool> cout;

    void prc_fa();

    SC_CTOR(decoder2by4) {
        SC_METHOD(prc_fa);
        sensitive(a, b);
    };
};
```

A Behavioral Model of a Full Adder

```
// File: fa.cpp
#include "fa.h"

void fa::prc_fa() {
    sc_in<sc_int<5> > temp;

    temp = a.read() + b.read();
    sum = temp.range(3,0);
    cout = temp[4];
}
```

The same circuit is synthesized if the input type is **sc_uint**.

Comparator Circuit

```
SC_MODULE(neq) {  
    sc_in<sc_int<4> > a, b;  
    sc_out<bool> z;  
  
    void prc_neq() { z = (a != b); }  
  
    SC_CTOR(neq) {  
        SC_METHOD(prc_neq);  
        sensitive << a << b;  
    }  
}
```

Different comparison circuits are synthesized for different relational operators used..

Loops for Synthesis

- C++ loops: for, do-while, while
- SystemC RTL supports only for loops
 - For loop iteration must be a compile time constant

```
// File: demux.h
#include "systemc.h"

SC_MODULE(demux) {
    sc_in<sc_uint<2> > a;
    sc_out<sc_uint<4> > z;

    void prc_demux();

    SC_CTOR(demux) {
        SC_METHOD(prc_demux);    sensitive << a;
    }
};
```

Loops: An Example

```
// File: demux.cpp
#include "demux.h"

void demux::prc_demux() {
    sc_uint<3> j;
    sc_uint<4> temp;

    for(j=0; j<4; j++)
        if(a==j)    temp[j] = 1;
        else        temp[j] = 0;

    z = temp;
}
```

Loops are typically unrolled during synthesis.

Methods

```
// File: odd1s.h  
#include "systemc.h"
```

```
SC_MODULE(odd1s) {  
    sc_in<sc_uint<6> > din;  
    sc_out<bool> is_odd;
```

```
    bool isOdd(sc_uint<SIZE> abus);  
    void prc_odd1s();
```

```
    SC_CTOR(odd1s) {  
        SC_METHOD(prc_odd1s); sensitive << data_in;  
    }  
};
```

Methods other than SC_METHOD processes can also be used

Methods

```
// File: odd1s.cpp
#include "odd1s.h"

void odd1s::prc_odd1s() {
    is_odd = isOdd(din);
}

bool odd1s::isOdd(sc_uint<6> abus) {
    bool result;

    for(int i=0; i<6; i++)
        result = result ^ abus[i];

    return(result); }

```

During synthesis, the code in `prc_odd1s()` is inlined into `is_odd()`

Multiple Processes

```
// File: mult_proc.h
#include "systemc.h"

SC_MODULE(mult_proc) {
    sc_in<bool> in;
    sc_out<bool> out;

    sc_signal<bool> c1, c2;

    void mult_proc1();
    void mult_proc2();
    void mult_proc3();


    SC_CTOR(mult_proc) {
        SC_METHOD(mult_proc1); sensitive << in;
        SC_METHOD(mult_proc2); sensitive << c1;
        SC_METHOD(mult_proc3); sensitive << c2;
    }
};
```

Combinational circuit can also be modeled with multiple processes.

Inter-process communications are done via signals.

Verification

Testbench (sc_main(...))

 

Verifying the Functionality: Driver

```
// File driver.h
#include "systemc.h"

SC_MODULE(driver) {
    sc_out<bool> d_a, d_b, d_cin;

    // Generate input stimulus
    void prc_driver();

    SC_CTOR(driver) {
        SC_THREAD(prc_driver);
    }
};
```

Verifying the Functionality: Driver

```
// File: driver.cpp
#include "driver.h"

void driver::prc_driver(){
    sc_uint<3> pattern;
    pattern=0;

    while(1) {
        d_a=pattern[0];
        d_b=pattern[1];
        d_cin=pattern[2];
        wait(5, SC_NS);
        pattern++;
    }
}
```

pattern defines values for
inputs of DUT

Verifying the Functionality: Monitor

```
// File monitor.h
#include "systemc.h"

SC_MODULE(monitor) {
    sc_in<bool> m_a, m_b, m_cin, m_sum, m_cout;

    void prc_monitor();

    SC_CTOR(monitor) {
        SC_THREAD(prc_monitor);
        sensitive << m_a, m_b, m_cin, m_sum, m_cout;
    }
};
```

Verifying the Functionality: Monitor

```
// File: monitor.cpp
#include "monitor.h"

void monitor::prc_monitor(){
    cout << "At time " <<
    sc_time_stamp() << "::";
    cout << "(a, b, carry_in): ";
    cout << m_a << m_b << m_cin;
    cout << "(sum, carry_out): ";
    cout << m_sum << m_cout << endl;
}
```

Observe inputs and outputs of DUT, and check if outputs are correct wrt inputs.

Verifying the Functionality: Main

```
#include "driver.h"
#include "monitor.h"
#include "full_adder.h"

int sc_main(int argc, char * argv[]) {
    sc_signal<bool> t_a, t_b, t_cin, t_sum, t_cout;

    full_adder f1("FullAdderWithHalfAdders");
    f1(t_a, t_b, t_cin, t_sum, t_cout);

    driver d1("GenWaveforms");
    d1.d_a(t_a);
    d1.d_b(t_b);
    d1.d_cin(t_cin);

    monitor m1("MonitorWaveforms");
    m1(t_a, t_b, t_cin, t_sum, t_cout);

    sc_start(100, SC_NS);
    return(0); }
}
```

Modeling Sequential Logic

Edge Detection

- Positive or negative edges can be detected on signals or ports of `bool` type.
 - `signal_name.posedge()`: return true or false
 - `signal_name.posedge()`: return true or false
 - `signal_name.posedge_event()`
 - ✦ return an 0 -> 1 event
 - `signal_name.negedge_event()`
 - ✦ return an 1 -> 0 event

Modeling Synchronous Logic: Flip-flops

```
// File: dff.h
#include "systemc.h"

SC_MODULE(dff) {
    sc_in<bool> clk, reset, d;
    sc_out<bool> q;

    void prc_dff();

    SC_CTOR(dff) {
        SC_METHOD(prc_dff);
        sensitive_pos << clk; // edge sensitivity
        // sensitive_neg << clk;
    };
};
```

Modeling Synchronous Logic: Flip-flops

```
// File: dff.h  
#include "systemc.h"
```

Output ports and signals can be synthesized to FFs.

```
SC_MODULE(dff) {  
    sc_in<bool> clk, reset, d;  
    sc_out<bool> q;  
  
    void prc_dff();  
  
    SC_CTOR(dff) {  
        SC_METHOD(prc_dff);  
        sensitive << clk.posedge_event();  
        // sensitive << clk.negedge_event();  
    }  
};
```

Modeling Synchronous Logic: Flip-flops

```
// File: dff.cpp version 1  
#include "dff.h"
```

```
void dff::prc_dff(){  
    q = d;  
}
```

```
// File: dff.cpp version 2  
// FF w synchronous reset  
#include "dff.h"
```

```
void dff::prc_dff(){  
    if (!reset.read()) q = false;  
    else                q = d;  
}
```

Registers

```
#include "systemc.h"
const int WIDTH = 4;

SC_MODULE(reg) {
    sc_in<bool> clock;
    sc_in<sc_uint<WIDTH> > cstate;
    sc_out<sc_uint<WIDTH> > nstate;

    void prc_reg() { nstate = cstate; }

    SC_CTOR(dff) {
        SC_METHOD(prc_dff);
        sensitive_neg << clock;
    };
};
```

Sequence Detector: “101”

```
// File: sdet.h
#include "systemc.h"
```

```
SC_MODULE(sdet) {
    sc_in<bool> clk, data;
    sc_out<bool> sfound;
    sc_signal<bool> first, second, third;

    void prc_sdet();
    void prc_out();

    SC_CTOR(sdet) {
        SC_METHOD(prc_sdet);
        sensitive_pos << clk;
        SC_METHOD(prc_out);
        sensitive << first << second << third;
    }
};
```

A model contain multiple processes,
some for combinational logic, some
for sequential logic

Sequence Detector: “101”

```
// File: sdet.cpp
#include "sdet.h"

// A shift register
void sdet::prc_sdet(){
    first = data;
    second = first;
    third = second;
}

// match the shift reg to string pattern
void sdet::prc_out(){
    sfound = first & (!second) & third;
}
```

Counter: Up-down, Async Negative Clear

```
// File: cnt4.h
#include "systemc.h"
const int CSIZE = 4;

SC_MODULE(sdet) {
    sc_in<bool> mclk, clear, updown;
    sc_out<sc_uint<CSIZE> > dout;

    void prc_cnt4();

    SC_CTOR(cnt4) {
        SC_METHOD(prc_cnt4);
        sensitive_pos << mclk;
        sensitive_neg << clear;
    };
};
```


Counter: Up-down, Async Negative Clear

```
// File: cnt4.cpp
#include "cnt4.h"

void sdet::prc_cnt4(){
    if(!clear)
        data_out = 0;
    else
        if(updown)
            dout=dout.read()+1;
        else
            dout=dout.read()-1;
}
```

Template for Sequential Process with Asynchronous Reset

```
void my_module::my_process () {
    if (a)                // Positive value used, since positive
                        // edge specified.
        <asynchronous behavior>
    else if (b)
        <asynchronous behavior>
    else if (! d)        // Logical-not used, since negative
                        // edge specified.
        <asynchronous behavior>
    else if (! e)
        <asynchronous behavior>
    else if (! f)
        <asynchronous behavior>
    else                // Rising clock edge.
        <clocked behavior>
}
```

Multiple Clocks



```
#include "systemc.h"

SC_MODULE(multiclock) {
    sc_in<bool> clk1, clk2;
    sc_out<sc_uint<CSIZE> > ...;
    sc_signal<bool> ...;

    void prc_clk1() {}
    void prc_clk2() {}

    SC_CTOR(multiclock) {
        SC_METHOD(prc_clk1);
        sensitive_pos << clk1;
        SC_METHOD(prc_clk2);
        sensitive_neg << clk2;
    };
};
```

Multiple Drivers and Resolved Logic

  

	0	1	Z	X
0	0	X	0	X
1	X	1	1	X
Z	0	1	Z	X
X	X	X	X	X

Multiple Drivers

```
#include "systemc.h"
const BUS_SIZE = 4;

SC_MODULE(bus) {
    sc_in<bool> a_rdy, b_rdy;
    sc_in<sc_uint<BUS_SIZE> > a_bus, b_bus;
    sc_out_rv<BUS_SIZE> z_bus; //resolved type

    void prc_a_bus();
    void prc_b_bus();

    SC_CTOR(bus) {
        SC_METHOD(prc_a_bus);
        sensitive << a_rdy << a_bus;
        SC_METHOD(prc_b_bus);
        sensitive << b_rdy << b_bus;
    };
};
```

Multiple Drivers

```
void bus::prc_a_bus() {  
    if (a_rdy)  
        z_bus = a_bus.read();  
    else  
        z_bus = "ZZZZ";  
}
```

```
void bus::prc_b_bus() {  
    if (b_rdy)  
        z_bus = b_bus.read();  
    else  
        z_bus = "ZZZZ";  
}
```

`sc_signal_rv<n>`: resolved signal vector type

Variables or Signals

- Local variables declared within SC_METHOD processes do not have memory.
- Assignment to variables happens instantly.
- Assignment to signals happens after a *delta* delay.

Shift Register

```
#include "systemc.h"
```

```
SC_MODULE(Shifter) {  
    sc_in<bool> clk, din;  
    sc_out<bool> dout;  
    bool q; //may cause dout to carry wrong value
```

```
    void prc_reg1() { q = din; }  
    void prc_reg2() { dout = q; }
```

```
    SC_CTOR(Shifter) {  
        q = 0;  
        SC_METHOD(prc_reg1);  
        sensitive_pos << clk;  
        SC_METHOD(prc_reg2);  
        sensitive_pos << clk;  
    }  
};
```


Shift Register (1)

```
#include "systemc.h"
```

```
SC_MODULE(shifter) {  
    sc_in<bool> clk, din;  
    sc_out<bool> dout;  
    sc_signal<bool> q;
```

```
    void prc_reg1() { q = din; }  
    void prc_reg2() { dout = q; }
```

```
    SC_CTOR(shifter) {  
        q = 0;  
        SC_METHOD(prc_reg1);  
        sensitive_pos << clk;  
        SC_METHOD(prc_reg2);  
        sensitive_pos << clk;  
    }  
};
```

Shift Register (2)


```
#include "systemc.h"
```

```
SC_MODULE(Shifter) {  
    sc_in<bool> clk, din;  
    sc_out<bool> dout;  
    sc_signal<bool> q;
```


```
    void prc_shift() { q = din; dout = q;}
```

```
    SC_CTOR(Shifter) {  
        q = 0;  
        SC_METHOD(prc_reg1);  
        sensitive_pos << clk;  
        SC_METHOD(prc_reg2);  
        sensitive_pos << clk;  
    }  
};
```

Finite State Machines

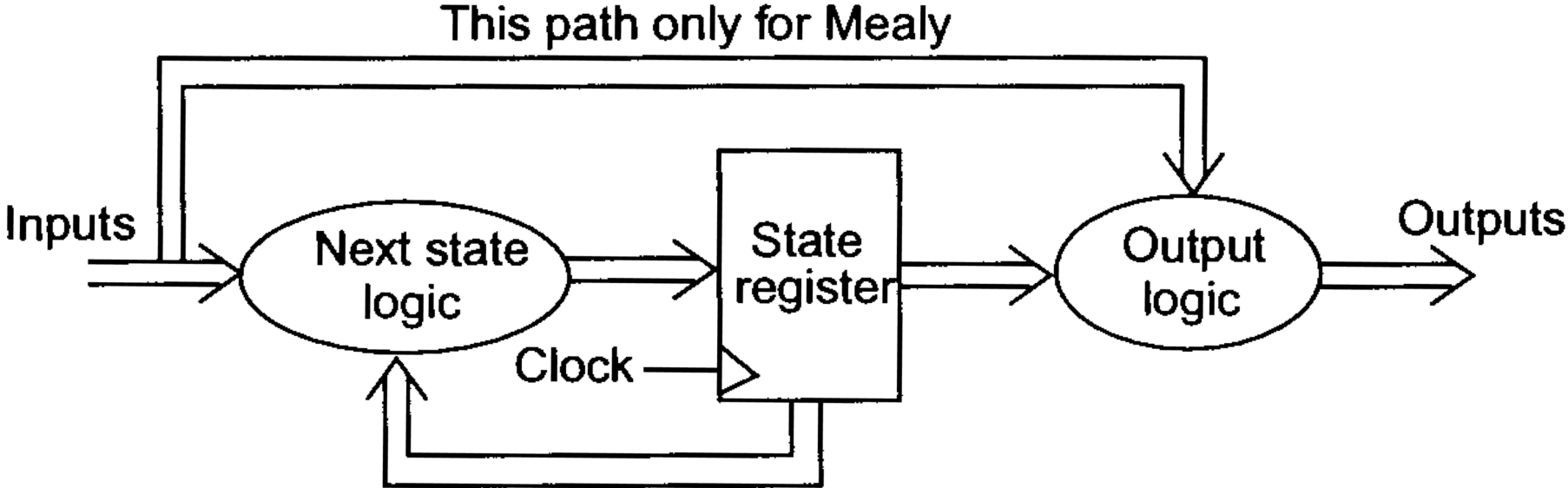

Modeling Moore FSM

 

Modeling Moore FSM

```
#include "systemc.h"
```

```
SC_MODULE(moore) {  
    sc_in<bool> clk, reset, a;  
    sc_out<bool> z;
```

```
    enum state_type {s0, s1, s2, s3 };  
    sc_signal<state_type> moore_state;
```

```
    void prc_moore();
```

```
    SC_CTOR(moore) {  
        SC_METHOD(prc_moore);  
        sensitive_pos << clk;  
    };
```

Modeling Moore FSM

```
void moore::prc_moore() {
    if (reset) {
        moore_state = s0;
        z = 1;
    }
    else
        switch (moore_state) {
            case s0:
                z = 1;
                moore_state = a ? s0 : s2;
                break;
            case s1:
                ...
            case s2:
                ...
            case s3:
                ...
        }
}
```

A extra FF is derived for z

Modeling Moore FSM

```
#include "systemc.h"
```

```
SC_MODULE(moore) {  
    sc_in<bool> clk, reset, a;  
    sc_out<bool> z;
```

```
    enum state_type {s0, s1, s2, s3 };  
    sc_signal<state_type> moore_state;
```

```
    void prc_states();  
    void prc_output();
```

```
    SC_CTOR(moore) {  
        SC_METHOD(prc_states); sensitive_pos << clk;  
        SC_METHOD(prc_output); sensitive << moore_state;  
    };
```


Separate state transition logic from output logic to avoid introducing FFs for output signals.

Modeling Moore FSM

```
void moore::prc_states() {
    if (reset)
        moore_state = s0;
    else
        switch (moore_state) {
            case s0:
                moore_state = a ? s0 : s2;
                break;
                //Other cases
                ...
        }
}
```

```
void moore::prc_output() {
    switch (moore_state) {
        case s0: z = 1; break;
        case s1: z = 0; break;
        case s2: z = 1; break;
        case s3: z = 0; break;
    }
}
```


Modeling Mealy FSM

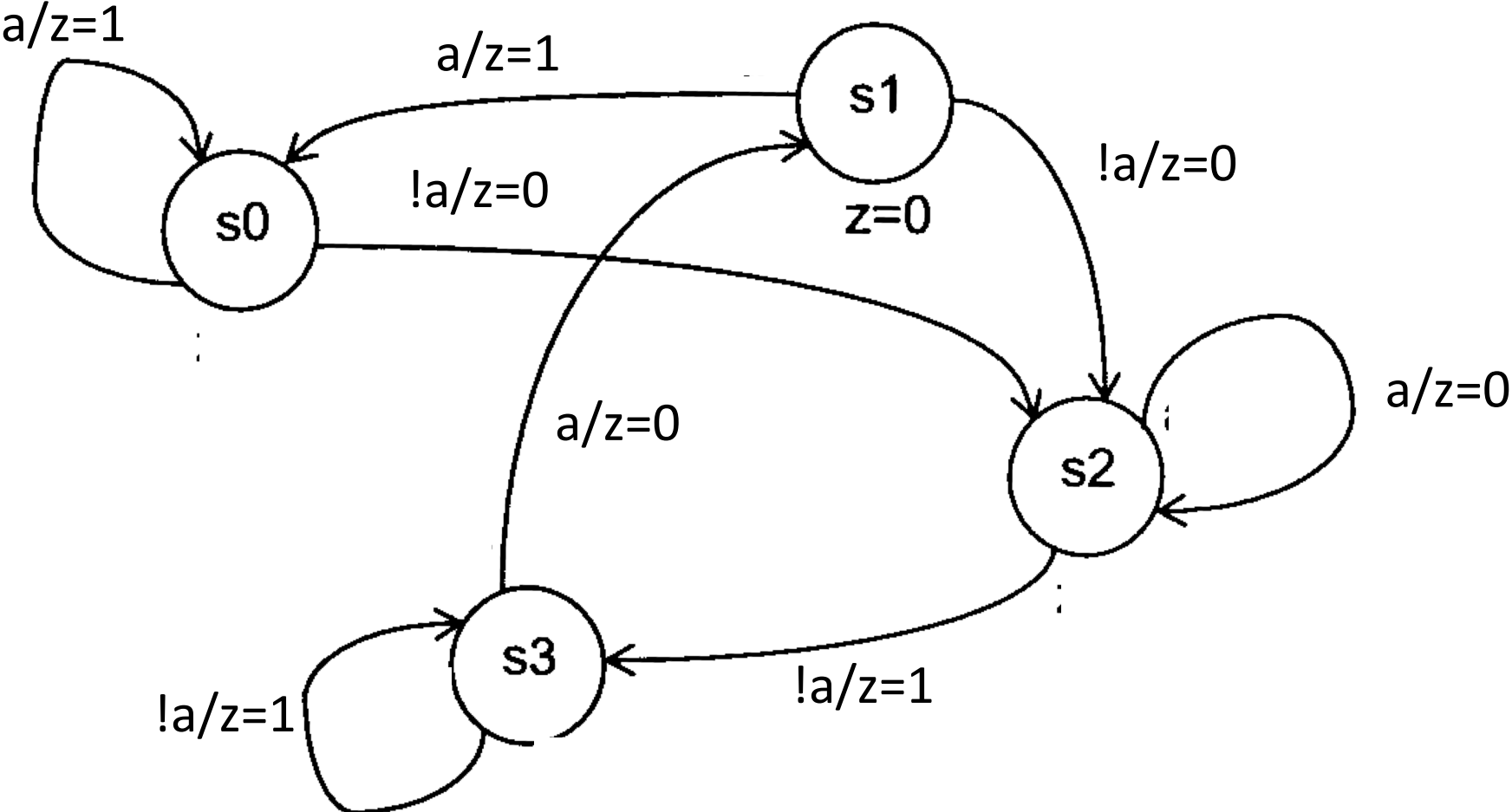

Modeling Mealy FSM

```
#include "systemc.h"

SC_MODULE(mealy) {
    sc_in<bool> clk, reset, a;
    sc_out<bool> z;

    enum state_type {s0, s1, s2, s3 };
    sc_signal<state_type> cstate, nstate;

    void prc_state();
    void prc_output();

    SC_CTOR(mealy) {
        SC_METHOD(prc_state);
        sensitive_pos << clk;
        SC_METHOD(prc_output);
        sensitive << cstate << a;
    }
};
```


Mealy FSM

```
void mealy::prc_state() {  
    if (reset)  
        cstate = s0;  
    else  
        cstate = nstate;  
}
```

```
void mealy::prc_output() {  
    z = 1;  
    switch (cstate) {  
        case s0: if (!a) { z = 0; nstate = s2; }  
                else    { z = 1; nstate = s0; }  
                break;  
        case s1: ... break;  
        case s2: ... break;  
        case s3: ... break;  
    }}  
}
```

Verification and Testbench

Testbench (sc_main(...))

 


Clock Signal

```
sc_clock clock_name ("name", period, duty_cycle, start_time, positive_first ) ;  
name:      name           type: char *  
period:    clock period  type: variable of type sc_time or constant of type uint64  
duty_cycle:      clock duty cycle           type: double default value: 0.5  
start_time:      time of first edge           type: variable of type sc_time or  
constant of type uint64  
  
default value: 0  
positive_first:      first edge positive           type: bool    default value: true
```

Clock Signal
 
```
sc_clock clk1("clock1", 20, 0.5, 2, true);
```



```
// To bind a clock object to port  
mod.port(clk1.signal());
```

Tracing

Simulation results can be saved in 3 formats:

- VCD – use `sc_create_vcd_trace_file(name);`
- WIF – use `sc_create_wif_trace_file(name);`
- ISDB – use `sc_create_isdb_trace_file(name);`

Create a trace file:

```
sc_trace file *tfile =  
    sc_create_vcd_trace_file("myvcddump");
```

Trace a signal:

```
sc_trace(tfile, sig1, "sig_name");
```

Tracing

Create a trace file:

```
sc_trace file *tfile =  
    sc_create_vcd_trace_file("myvcddump");
```

Trace a signal:

```
sc_trace(tfile, sig1, "sig_name");
```

After simulation finishes,

```
sc_clock_vcd_trace_file(tfile);
```